

EECS 16B Designing Information Devices and Systems II

Summer 2020

Note 1

1 Introduction to RC circuits and Differential Equations

Let us motivate this note by understanding the speed of digital computers. We can understand computers as a set of blocks that perform digital logic operations one after the another. We learned about these logical blocks earlier in the form of ‘AND’ and ‘OR’ gates. One of the most basic logical blocks is an inverter (or a ‘NOT’ gate). An inverter takes a boolean input and outputs the logical inverse: a 0 (low) maps to a 1 (high) and a 1 (high) maps to a 0 (low). The speed of the computers is related to how quickly these logical blocks can change their state and thus perform logic (for example, how quickly an inverter can output a 0 after its input changes to a 1).

One of the most basic circuits that we can use to analyze this change is an oscillator, a basic device that oscillates between zero and one. In fact such oscillators are quite common and are used as clocks in all the devices you regularly use! We can analyze the speed and behavior of such oscillators as a basic model to understand the more complex behavior of computers and their speed.

One way to create oscillators is by connecting together an odd prime number of inverters in a loop. Simply connecting an inverter in a loop will misbehave¹. This type of oscillator is called a ring oscillator. By examining the signal in this oscillator after any inverter we can see that the signal must indeed oscillate between 0 and 1. We can create these inverters physically by using transistors as shown below:

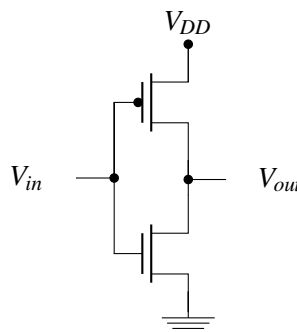


Figure 1: CMOS Inverter

Until now transistors have been modeled as switches that change state based on the voltage applied at their gates. In the switch model of transistors each inverter switches instantaneously. If each inverter switched instantaneously then connecting them in a loop would lead to inconsistent behavior! However, since we can implement this circuit in the real world there is clearly some aspect that we are missing. When such inconsistencies arise in our model, this can be a symptom of failing to properly understand real world behavior.

¹If we simply have one inverter connected in a loop we will not have the switching behavior of the oscillator that we desire (depending on if the capacitor is appropriately sized). Since the circuit is fighting between high and low at the output it can stabilize at an intermediate value. In order to allow for oscillations we need to chain more inverters in a loop. In fact to prevent undesired behavior, we usually chain together a prime number of inverters. The reason why is related to properties of modulo arithmetic you will learn in CS70 together with properties of signals studied in EE120.

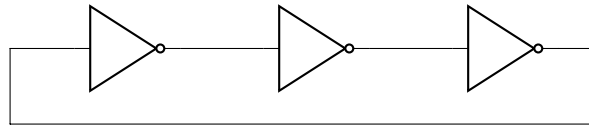


Figure 2: Ring oscillator with 3 inverters

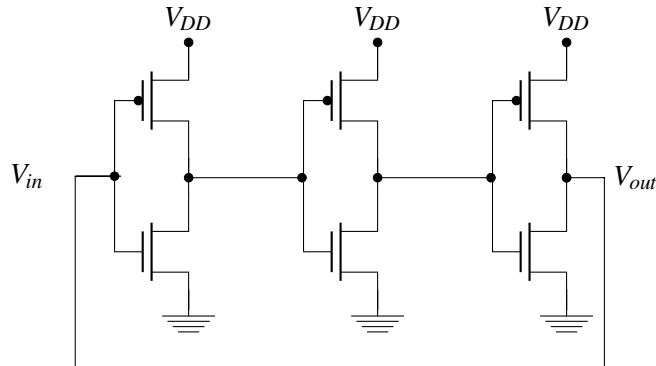


Figure 3: Ring oscillators with 3 CMOS inverters

In such cases, the usual approach is to approach the problem with a more detailed model. In this case, the oscillating behavior that we see is actually possible as there is a slight delay between the input and output of the inverters. You can think of these inverters in terms of relays or mechanical switches that are turned on and off by springs. The slight delay while the spring moves the switch from on to off and vice versa is what enables the oscillatory behavior that we see.

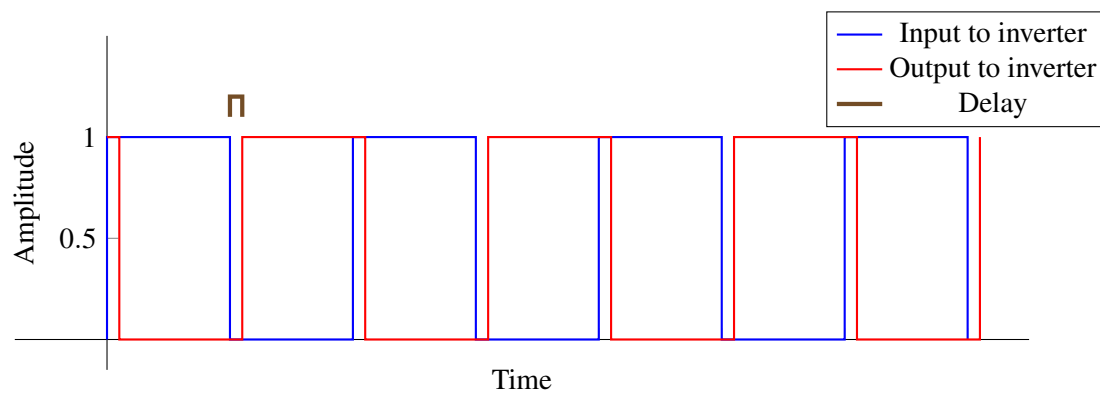


Figure 4: Delay in inverter output for simplified model.

Resistor-Capacitor Model for Transistors

Since our simple switch model is not enough to understand this delayed behavior, we adopt a more detailed model for transistors. We model transistors as having some resistance and some characteristic capacitance from their gates. Note: When dealing with these circuits in real-world integrated circuits, we also must deal with the capacitance of the wires.

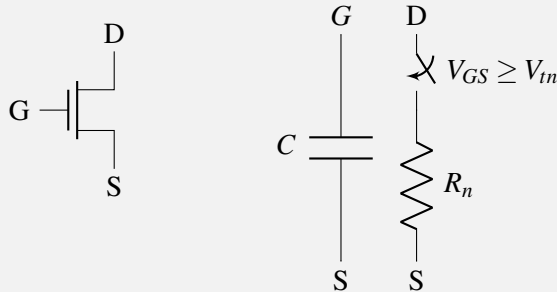


Figure 5: NMOS Transistor Resistor-switch model

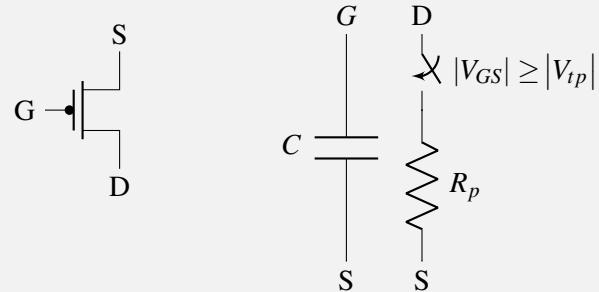


Figure 6: PMOS Transistor Resistor-switch model

This model for inverters can be used to redraw and analyze our oscillator made out of inverters from Figure 3

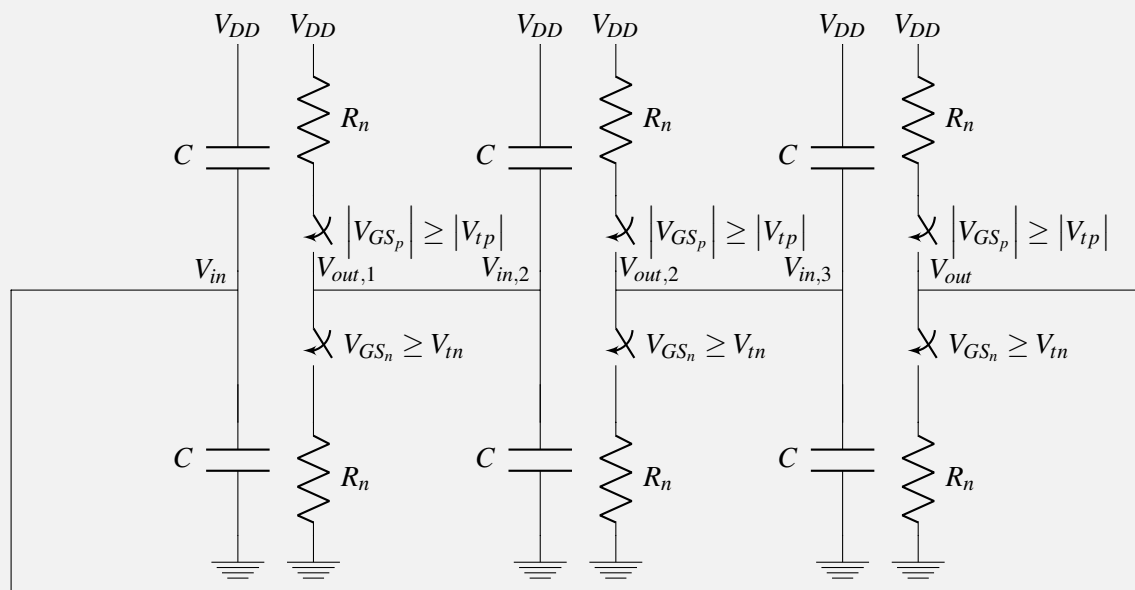


Figure 7: Ring oscillator with detailed transistor model.

With this model we can see that each inverter drives some capacitance. This means that each inverter is pushing or draining charge from capacitors to cause the output to flip to a '1' or a '0'.

To get an idea of how fast it takes for the inverter to change signals, let us examine the case of the first inverter in the oscillator where the output started at 1 (high) switching to zero.

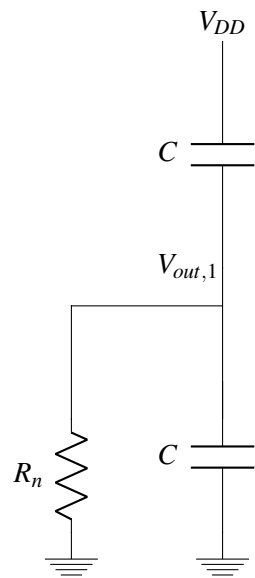


Figure 8: Inverter output at 0

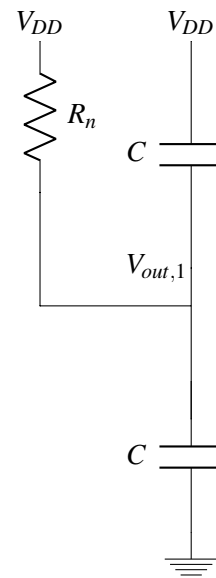


Figure 9: Inverter output at 1

If we condense the circuit down we see that switching the signal involves discharging the capacitor through a resistor. Similarly, if we look at an inverter going from outputting a 0 to a 1 we get a capacitor charging through a resistor. We will show that this behavior is true later in the note. In the next section we will analyze this with an intuitive approach.

2 Intuitive approach to RC circuits

Before going into the example above, let us intuitively examine a circuit with a single resistor and capacitor and examine the voltage on a discharging capacitor over time.

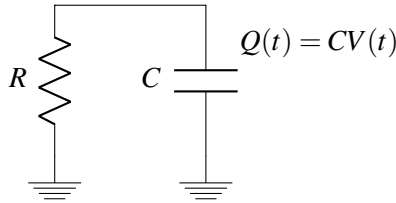


Figure 10: Capacitor discharging through circuit

Let us start out by writing the equations we know from EE16A:

$$V = IR \quad (1)$$

$$Q = CV \quad (2)$$

Here since we are dealing with voltage and current changing over time we will use $V(t)$ and $I(t)$ in place of V and I to denote this time dependence.

We know that the voltage on the capacitor starts out high at some value we will call V_{DD} . This voltage $V(t)$ is the result of some charge $Q(t)$ on the capacitor. When we discharge the capacitor, the charge leaves the capacitor as a current through the resistor and sinks into ground. From Ohm's law, the current through the resistor is $I(t) = \frac{V(t)}{R}$. As charge leaves the capacitor, $V(t)$ decreases and as a result the current $I(t)$ also decreases. Therefore as the voltage drops, charge will leave the capacitor at a decreased rate due to the decrease in current. Thus the voltage drop will be a curve falling sharply first and then decreasing at some rate with the decrease in voltage.

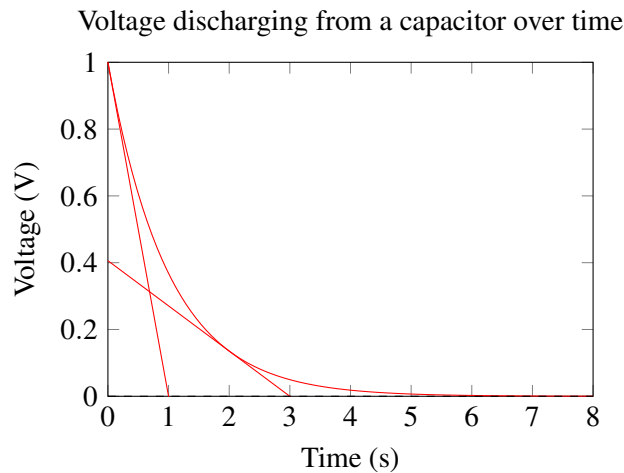


Figure 11: Voltage on capacitor discharging through resistor with RC constant = 1

Now the question arises, what exactly is this curve? Does it have a formula? In the following sections we will use a mathematical approach to solve for $V(t)$ exactly and validate our intuition.

3 Mathematical approach to RC circuits

To begin solving for $v(t)$ let us begin with the following approach that should be a familiar pattern from EE16A:

- Establish variables for various parts of the circuit
- Utilize KCL (Kirchoff's current law) to establish current equations
- Establish remaining equations (branch equations) with the elements of the circuit

Let us start by establishing variables for the circuit ²:

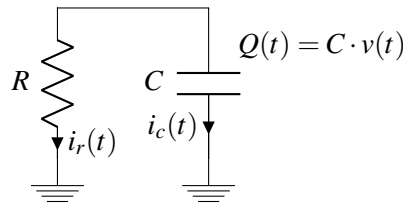


Figure 12: Capacitor discharging through circuit

Let $v(t)$ be the voltage across the capacitor, $Q(t)$ be the charge on the capacitor, $i_c(t)$ be the current flowing through the capacitor to ground, $i_r(t)$ be the current flowing through the resistor to ground, C be the capacitance of the capacitor and R be the resistance of the resistor.

To establish current equations we can focus on the node between the capacitor and resistor. Here we relate the currents to get the equation:

$$i_c(t) = -i_r(t)$$

For the remaining equations let us start by looking at the equation $Q(t) = Cv(t)$. This charge, $Q(t)$, starts to leave the capacitor as current through the capacitor which in turn lowers the voltage on the capacitor. Since current is the change in charge over time we differentiate the formula for charge given above to get:

$$i_c(t) = \frac{d}{dt}Q(t) = C \frac{d}{dt}v(t)$$

This gives us the following equations:

$$i_c(t) = C \frac{d}{dt}v(t), i_r(t) = \frac{v(t)}{R} \quad (3)$$

$$i_c(t) = -i_r(t) \quad (4)$$

Simplifying the above equations by substitution we get:

$$\frac{d}{dt}v(t) = -\frac{1}{RC}v(t) \quad (5)$$


²You might wonder why we switch between uppercase and lowercase letters when referring to variables. In traditional circuits literature, constant voltages and currents use uppercase letters such as V_{DD} or I_s . For voltages that vary over time, we use lowercase letters $v(t)$ or $i_r(t)$ to make a distinction between the two.

At first glance it seems like we have one equation and two unknowns: $\frac{d}{dt}v(t)$ and $v(t)$. Normally we would not be able to make much progress with such a set up. However, these two unknowns are actually related by $\frac{d}{dt}$, the derivative operator. An equation of this form, that relates the derivative of a function to something, is called a differential equation. We will learn how to solve it in the next section.

Now that we have derived an equation for a discharging capacitor we can show how our inverter output switching from 1 to 0 behaves like a discharging capacitor.

Back to the Inverter

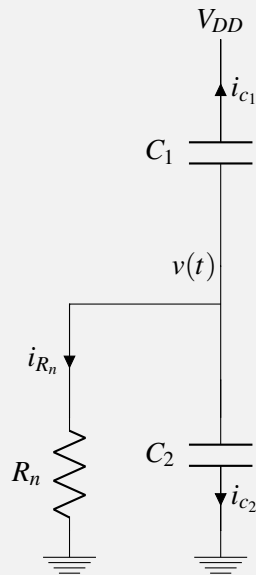In Figure 13 the inverter has just switched from outputting 1 to outputting 0. This means that the voltage $v(t)$ started at V_{DD} and decreases to 0 at steady state. We know the voltage across C_1 is $v(t) - V_{DD}$ and the voltage across C_2 is $v(t)$. Using this information we can set up a differential equation to solve for $v(t)$.



Applying KCL at the center node,

$$i_{c1} + i_{c2} = -i_{Rn}$$

From the voltage-current relationship of a capacitor,

$$i_{c1} = C_1 \frac{d}{dt}(v(t) - V_{DD}), \quad i_{c2} = C_2 \frac{d}{dt}v(t)$$

By Ohm's Law,

$$i_{Rn} = \frac{v(t)}{R_n}.$$

Figure 13: Inverter output at 0

After substituting the expressions for branch currents into KCL, it is possible to isolate $\frac{d}{dt}v(t)$.

$$\begin{aligned} C_1 \frac{d}{dt}(v(t) - V_{DD}) + C_2 \frac{d}{dt}v(t) &= -\frac{v(t)}{R_n} \\ C_1 \frac{d}{dt}v(t) + C_2 \frac{d}{dt}v(t) &= -\frac{v(t)}{R_n} \\ \frac{d}{dt}v(t) &= -\frac{v(t)}{R_n(C_1 + C_2)} \end{aligned}$$

This is exactly the same form of differential equation that we got for the discharging capacitor circuit with just a different value for capacitance! Thus we have shown that we can boil this inverter circuit down to a capacitor discharging through a resistor! (You can take a similar approach to show that an inverter that switches from 0 to 1 is akin to charging a capacitor through a resistor).

4 Differential equations

4.1 Simple scalar differential equations

Differential equations relate functions to their own derivatives. In this note we will learn to solve simple first order scalar differential equations. To begin let us start with the simple example of:

$$\frac{d}{dt}x(t) = b$$

Here b is a particular given constant. If you recall from high school calculus to find x we can integrate both sides with respect to t :

$$\int \frac{d}{dt}x(t)dt = \int b dt$$

$$x(t) = bt + k_1$$

where k_1 is any arbitrary constant.

We can check to see that this indeed satisfies $\frac{d}{dt}x(t) = b$ by calculating $\frac{d}{dt}x(t) = \frac{d}{dt}(bt + k_1) = \frac{d}{dt}(bt) + \frac{d}{dt}(k_1) = b + 0 = b$.

Recall from calculus that we resolved this ambiguous constant through definite integrals, where the bounds of integration were specified. We will further discuss solving for the unknown constants in upcoming sections. Though the example here utilized a constant, this method can be extended to differential equations of the form $\frac{d}{dt}x(t) = f(t)$ where $f(t)$ is any function that we can integrate.³

4.2 “Homogeneous” differential equations

Next we work to extend this beyond $\frac{d}{dt}x(t) = f(t)$ to the more general first order differential equations of the form $\frac{d}{dt}x(t) = ax(t) + b$ where a and b are constants (In the context of circuits you will see that b will be the effect of voltage and current sources). Let us start by setting $b = 0$ to get $\frac{d}{dt}x(t) = ax(t)$ with what are called homogeneous first order differential equations. The name isn't important and while this may feel simpler than the general form of such differential equations, this equation is exactly like $\frac{d}{dt}v(t) = \frac{-v(t)}{RC}$, the differential equation for the voltage on a discharging capacitor, where $a = -\frac{1}{RC}$.

The format of this equation should remind you of eigenvalues you saw in EE16A. There we saw $A\vec{x} = \lambda\vec{x}$. This parallels $\frac{d}{dt}x(t) = ax(t)$, where the derivative (a linear operator), akin to the linear matrix operator, acts on some function $x(t)$ to give the same function $x(t)$ times some constant a . In addition, we see that $x(t) = 0$ is a trivial solution similar to how $\vec{x} = \vec{0}$ was a trivial solution.

Thus, intuition tells us that we should look for "eigenfunctions" of the derivative operator. In other words we need a function whose derivative equals itself times some constant. It follows that the function e^{at} satisfies this property perfectly! Furthermore, recall that when we solved for eigenvectors, we found an eigenspace where any linear combination of eigenvectors corresponding to a eigenvalue constituted a valid eigenvector. Similarly, here we see that, with the information given, any multiple of e^{at} satisfies the differential equation. Hence, one solution will be in the form of $x(t) = ke^{at}$ where k can be any constant. Thus for our RC circuit, the solution should be something like $x(t) = ke^{\frac{-t}{RC}}$.

³ It is important also to realize that the only reason this “anti-derivative” approach to solving this kind of simple differential equation is valid is because you have proved the fundamental theorem of calculus in your basic calculus courses. Without that theorem, the use of integration here is nothing more than a heuristic.

So far, what we have done here is simply a form of glorified guessing. This is because while the eigenvalue/eigenvector idea above can be made rigorous, we haven't done so. We are reasoning by analogy here. Anything obtained purely by analogy is just an educated guess. So we need to check to see if this guess is even a solution to the differential equation.

Let us validate our guess $x(t) = ke^{\frac{-t}{RC}}$ by taking the derivative of $x(t)$:

$$\frac{d}{dt}ke^{\frac{-t}{RC}} = \frac{-1}{RC}ke^{\frac{-t}{RC}} \quad (6)$$

And it turns out that this worked!

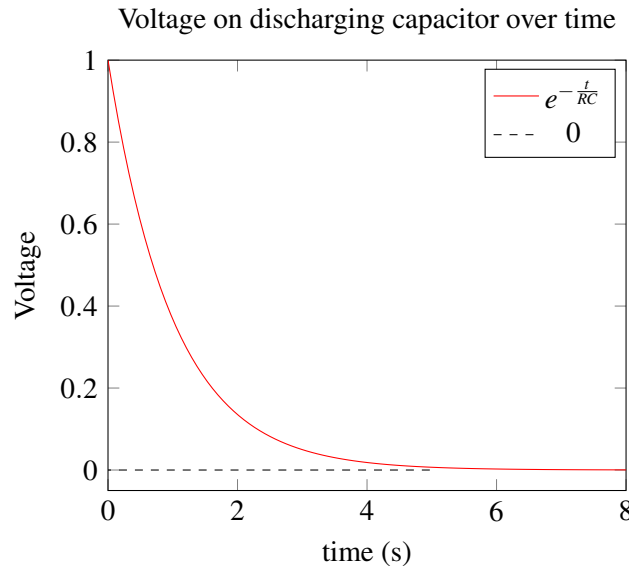


Figure 14

4.3 Uniqueness

Now that we have found a set of potential solutions, the other question that arises is whether there is a unique solution to the differential equation that we are solving. In both the cases above:

$$x = bt + k_1$$

$$\frac{d}{dt}k_2e^{at} = ak_2e^{at}$$

we had an infinite number of solutions as the constants k_1, k_2 in question could take any value and still satisfy the differential equation. Thus in order to restrict the set of solutions of these differential equations, we need more information. This information can usually be derived from the behavior of the system depending on the problem context.

Here let $x(0) = x_0$. This information is called an "initial condition" and is usually specified as the value the function takes at time $t = 0$. Although the initial condition is often specified, other points and boundary conditions can be used as well; for example we can also use steady state, i.e. $t \rightarrow \infty$, behavior to solve for the constants in question.⁴

⁴One question that may arise is whether it is valid to use times before $t = 0$ in order to compute the constant for the unique

Hence, our system is defined as follows:

$$\frac{d}{dt}x(t) = ax(t) \quad (7)$$

$$x(0) = x_0 \quad (8)$$

Revisiting the solution to the differential equation above with the initial condition we get:

$$x(t) = ke^{at} \quad (9)$$

$$x(0) = ke^0 \quad (10)$$

$$x(0) = k = x_0 \quad (11)$$

Thus we get the solution $x(t) = x_0e^{at}$. In the case of the discharging capacitor circuit, we set the initial condition $x(0) = V_{DD}$, where the capacitor was initially charged to V_{DD} . In this case solving for the constant multiplier gives us $k = V_{DD}$, yielding the solution $x(t) = V_{DD}e^{\frac{-t}{RC}}$. Finally, we have a specific solution to our problem.

Proof of uniqueness

Though we have one solution that satisfies the homogeneous differential equation and initial condition we are not yet done. We need to ensure that we have not left out any other solutions. To do so, we will prove that the solution we found is unique (Note: not all differential equations have unique solutions but we can prove the differential equation in this case does).

We start by assuming that there is another solution to the homogeneous differential equation. To argue for uniqueness we must show that the other solutions must be exactly the same as the solution that we have already found. Normally our first approach when proving equality is to manipulate both solutions to the same form, however, since we lack an expression for this hypothetical other solution, we must take another approach. We can show equality through one of two ways:

- The difference between the solutions is 0 everywhere the solution is defined
- The ratio of the solutions is always 1

Showing either of the two statements will establish the equality between the two solutions, and hence prove the uniqueness of our original solution.

Proof:

We will prove equality with the second approach⁵. We have showed one solution: $x(t) = x_0e^{at}$. Let us assume there is another solution to the homogeneous differential equation: $y(t)$ such that $\frac{d}{dt}y(t) = ay(t)$ and $y(0) = x_0$.

To do this, we define the ratio $z(t) = \frac{y(t)}{x(t)}$. If we can show $z(t) = 1$ for all $t \geq 0$, it must be that $y(t) = x(t)$ proving the uniqueness of $x(t) = x_0e^{at}$. We start by showing that $z(0) = 1$ at $t = 0$. From initial conditions we already know that $y(0) = x_0$. Plugging $t = 0$ into the equation we get $z(0) = \frac{y(0)}{x(0)} = \frac{x_0}{x_0e^0} = 1$.

solution. Though we are free to use steady state behavior, the time in the problems we establish starts at time 0. Thus in the world of our problem there is no time before 0 and so it is invalid to consider times $t < 0$ to solve for unique solutions.

⁵In general when faced with multiple approaches to solve a problem it is advantageous to try them all. As you attempt the problem, some approaches will inevitably appear easier. You can follow through with these approaches to arrive at a solution!

Now we analyze the derivative of the ratios of solutions.

$$\frac{d}{dt}z(t) = \frac{d}{dt} \frac{y(t)}{x_0 e^{at}} = \frac{1}{x_0} \frac{d}{dt} y(t) e^{-at} = \frac{-ay(t)e^{-at}}{x_0} + \frac{1}{x_0} e^{-at} \frac{d}{dt} y(t) = \frac{-aye^{-at}}{x_0} + \frac{aye^{-at}}{x_0} = 0$$

To complete the proof, there is the slightly subtle case when we are dealing with an initial condition equal to 0. We will guide you through this step of the uniqueness proof in your homework.

Thus since the derivative is always 0 and the ratio is 1 at $t = 0$ we can conclude that the ratio never moves away from 1 and that the two solutions are the same everywhere and thus are equal.

It is important to remember that this uniqueness proof is actually crucial. This is what allows us to use guess-and-check to solve differential equations with any confidence in the answer. Since essentially all so-called-methods for solving differential equations are really just ways of guessing, uniqueness is vital to being able to make progress.

4.4 Nonhomogeneous differential equations

Now that we have learned to solve homogenous differential equations (those for which the all zero solution is a potential solution) let us learn to solve nonhomogeneous differential equations where all zero is not a possible solution. These are differential equations of the form shown below. The motivating example we use here is a charging capacitor in an RC circuit. This is akin to an inverter switching from ‘0’ to ‘1’.

$$\frac{dx}{dt} = ax + b, \text{ where } b \neq 0 \quad (12)$$

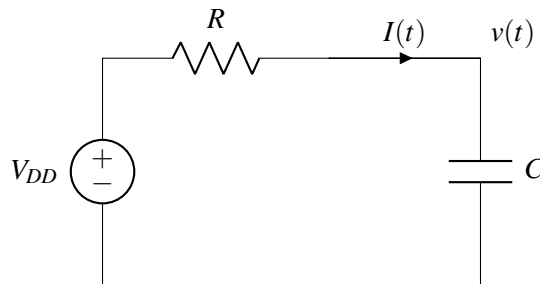


Figure 15: Capacitor charging through resistor circuit

There are many ways to solve this differential equation. We will start with Separation of Variables as a direct approach but also show Guess and Check and Change of Variables as alternate methods to build insight.

4.4.1 Separation of Variables

Given the following differential equation with initial condition $x(0) = x_0$,

$$\frac{d}{dt}x(t) = ax(t) + b, \text{ where } b \neq 0 \quad (13)$$

we can start by multiplying both sides by dt and integrating

$$\int dx = \int (ax+b)dt \quad (14)$$

$$\int \frac{dx}{ax+b} = \int dt \quad (15)$$

$$\int \ln(ax+b) = at + C \quad (16)$$

$$ax+b = Ke^{at} \quad (17)$$

We use the result from Calculus that $\int \frac{dx}{ax+b} = \frac{\ln(ax+b)}{a}$ and $K = e^C$ is another constant. Therefore, we see that the general form of our solution will be

$$x(t) = Ke^{at} - \frac{b}{a} \quad (18)$$

Lastly, if we plug in our initial condition $x(0) = x_0$, it follows that $x(0) = K - \frac{b}{a} = x_0 \implies K = x_0 + \frac{b}{a}$ and we can write the solution to our differential equation as

$$x(t) = x_0 e^{at} + \frac{b}{a}(e^{at} - 1) \quad (19)$$

4.4.2 Guess and Check

The technique used for Separation of Variables was a quick and easy way to solve for our differential equation using techniques from Calculus. Now one might ask why we didn't use a similar guess and check approach as we did for the homogenous differential equation. To answer this, we start by guessing $x(t) = x_0 e^{at}$ as a solution. If we take the derivative of $x(t)$ and check whether this is a solution, we evaluate the right-hand side first

$$ax(t) + b = ax_0 e^{at} + b$$

Whereas the left-hand side will be

$$\frac{d}{dt}x(t) = ax_0 e^{at} \neq ax(t) + b$$

So where did our guess go wrong? When evaluating $ax(t) + b$, the extra constant b seems to be causing some trouble. We can either try to add a constant to our derivative, or we can try to modify $x(t)$ to get rid of this constant. We will be taking the latter approach by creating a new, updated guess $x(t) = k_1 e^{at} + k_2$. Plugging this solution into our differential equation, we see that

$$\frac{d}{dt}x(t) = k_1 a e^{at} = ax(t) + b = k_1 a e^{at} + k_2 a + b$$

Now subtracting the $k_1 a e^{at}$ terms, a new equation $k_2 a + b = 0$ arises which tells us that $k_2 = -\frac{b}{a}$. From what it looks like, we need more information to solve for k_1 and that's where the initial condition comes in again!

$$x(t) = k_1 e^{at} - \frac{b}{a} \implies x(0) = k_1 - \frac{b}{a} = x_0$$

Solving for k_1 yields $k_1 = x_0 + \frac{b}{a}$ and we indeed end up with the same solution using Separation of Variables.

$$x(t) = x_0 e^{at} + \frac{b}{a}(e^{at} - 1) \quad (20)$$

4.4.3 Change of Variables

Our last and final approach to solving this differential equation uses a clever trick by reformulating an unknown problem in terms of a problem we know how to solve. So we formulate the above as a homogeneous differential equation that we know how to solve, and we want to do so in a way that doesn't make any assumptions.

In terms of circuits these homogeneous equations corresponded to our circuit having steady state values of 0. Here, however, the steady state value converges to some constant instead. To force this into a homogeneous differential equation we need to change variables so as to add an offset to shift the steady state value of our circuit to 0. We can accomplish this mathematically by substituting $\tilde{x}(t) = x(t) + \frac{b}{a}$ or $x(t) = \tilde{x}(t) - \frac{b}{a}$. This is simply a change of variables. We have represented our variable in a more convenient form without making any assumptions and changing the initial problem statement!⁶ With this substitution we get:

$$\frac{d}{dt}\tilde{x}(t) = a\tilde{x}(t) \quad (21)$$

This is exactly the homogeneous case we learned to solve before! Using the techniques described in the previous section we can find that $\tilde{x}(t) = ke^{at}$. We can now re-substitute to get $x(t) = ke^{at} - \frac{b}{a}$. As before we need an initial condition to solve for the constant k . Let the initial condition be $x(0) = x_0$. Plugging this in we get:

$$x_0 = ke^0 - \frac{b}{a} \implies k = x_0 + \frac{b}{a}$$

$$x(t) = (x_0 + \frac{b}{a})e^{at} - \frac{b}{a}$$

4.4.4 Quick Check

All three methods have yielded the same solution but we have yet to check the validity of our solution. To check this, let us plug our solution back into the original differential equation in (13). Since we start with $x(t) = (x_0 + \frac{b}{a})e^{at} - \frac{b}{a}$, we expect:

$$\text{LHS: } \frac{d}{dt}x(t) = \frac{d}{dt}\left((x_0 + \frac{b}{a})e^{at} - \frac{b}{a}\right) = a \cdot (x_0 + \frac{b}{a})e^{at} - 0 = a \cdot (x_0 + \frac{b}{a})e^{at} \quad (22)$$

$$\text{RHS: } a \cdot \left((x_0 + \frac{b}{a})e^{at} - \frac{b}{a}\right) + b = a \cdot (x_0 + \frac{b}{a})e^{at} - b + b = a \cdot (x_0 + \frac{b}{a})e^{at} \quad (23)$$

Hence, LHS = RHS, and $\frac{d}{dt}x(t) = ax(t) + b$ is solved by $x(t) = (x_0 + \frac{b}{a})e^{at} - \frac{b}{a}$. In fact it can be shown that it is uniquely⁷ solved by $x(t) = (x_0 + \frac{b}{a})e^{at} - \frac{b}{a}$.

⁶For example when solving $x + 2 = 7$ We can represent x as $x = \tilde{x} + 2$ or $x = \tilde{x} + 5$ if that makes the problem more convenient. With $x = \tilde{x} + 5$ we get $(\tilde{x} + 5) + 2 = 7$ Which we can solve to get $\tilde{x} = 0$ and $x = 5$. The initial problem is unchanged as x was simply a variable that we chose to represent in a more convenient manner \tilde{x} .

⁷We already proved uniqueness in the homogeneous case. This is in fact sufficient to prove uniqueness in the nonhomogeneous

4.4.5 Charging a Capacitor

With these techniques let us go back and approach the motivating example of a charging capacitor circuit. Recall that we wrote out KCL and voltage-current equations to get the nonhomogenous differential equation

$$\frac{d}{dt}v(t) = \frac{-1}{RC}v(t) + \frac{V_{DD}}{RC}$$

where $a = -\frac{1}{RC}$ and $b = \frac{V_{DD}}{RC}$.

Using the results from the previous sections, we know that the solution to our differential equation is

$$v(t) = V_{DD}(1 - e^{-\frac{t}{RC}}) \quad (24)$$

A plot of the voltage over time is shown below. Following the intuition for RC Circuits built in section 2, the capacitor is initially uncharged. The voltage source V_{DD} will charge for the capacitor and as the capacitor becomes charged, the voltage across the capacitor will increase while the voltage dropped across across the resistor will decrease. As a result, the current across the resistor decreases and this effect is shown by the decreasing rate of increase in $v(t)$ until $v(t)$ finally reaches its steady state value V_{DD} .

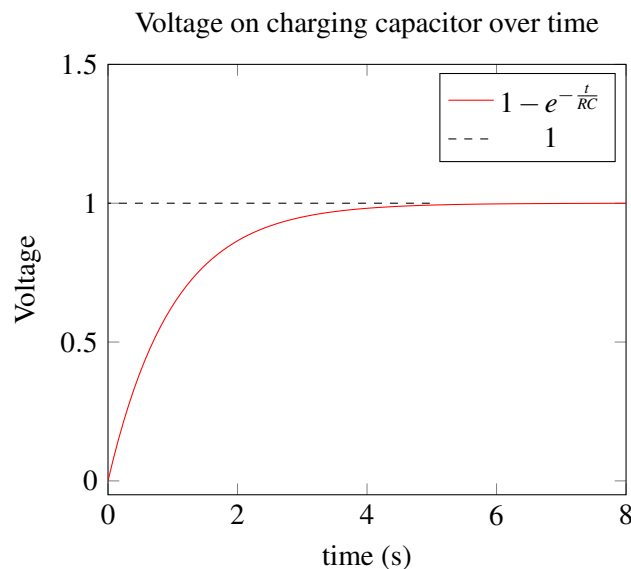


Figure 16

case, as we can simply to do a change of variables to phrase our problem as a homogeneous differential equation and prove uniqueness for this reformatted problem.

5 Nonlinear differential equations

In the above sections we only talked about linear differential equations where $\frac{d}{dt}x(t) = ax(t) + b$. However in general you may encounter differential equations like $\frac{d}{dt}x(t) = x(t)^2$ and other such nonlinear functions of $x(t)$.

In general, there are various “techniques” similar to the ones we saw for the nonhomogenous differential equation that can be used to guess or create potential solutions for such equations. At the end of the day, all of these guesses need to be checked and the appropriate uniqueness theorems proved to make sure that we have got the single true solution. Only then can this solution be used for any predictive purposes.

Without a uniqueness theorem, such solutions cannot be trusted for prediction. In the homework, you will see an example that illustrates how a seemingly innocuous differential equation can have nonunique solutions. In that homework, we will also share another heuristic technique that can be used to guess solutions to nonlinear differential equations. There are many such heuristic techniques out there, and different ones tend to work for different types of equations. You will encounter these techniques in later courses alongside the kinds of differential equations for which they tend to work.

Contributors:

- Nikhil Shinde.
- Anant Sahai.
- Aditya Arun.
- Taejin Hwang.