

EECS16A DIS 8B

email: moseswan@berkeley.edu

OH: W 10AM-12PM PT (HWP)

→ Discard

→ on queue

Logistical bits

① Circuit Review sessions

② Piazza posts

③ Scope: Norton/Thévenin

④ Karinna! Ask her questions too!

Topics / Learning objectives

① Applying superposition (how to turn off sources, labeling nuances)

② Resistor equivalence round 2

③ If time: example of a source dissipating energy/power

Playlist:

Superorganism

Everybody wants to be famous (Lucy Yang)

Waves (Tame Impala) remix

Shura - the stage

suggestions @ bit.ly/16ajukebox


EECS 16A Designing Information Devices and Systems I

Fall 2020 Discussion 8B

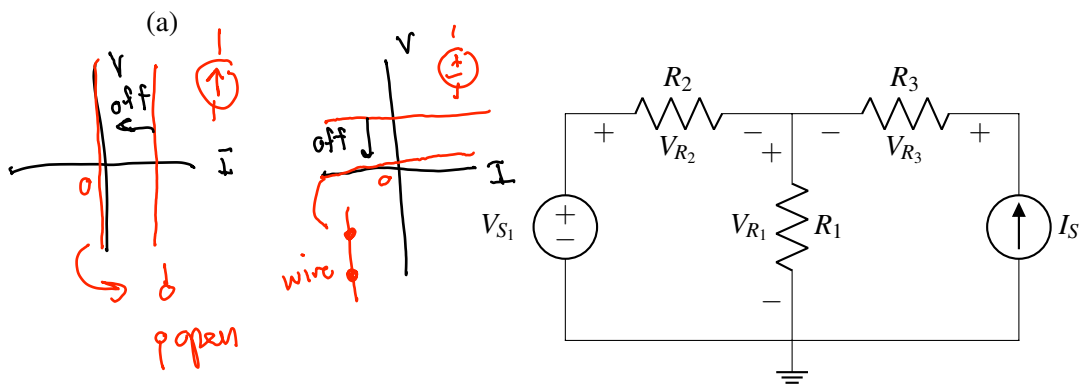1. Superposition



For the following circuits:

- Use the superposition theorem to solve for the voltages across the resistors.
- For parts (b) and (c) only, find the power dissipated/generated by all components. Is power conserved?



- (circuit)
- Redraw ch. w/ only one source on (for all sources) compute values
 - Sum values to calculate


(subckt 1)

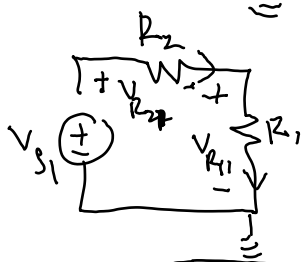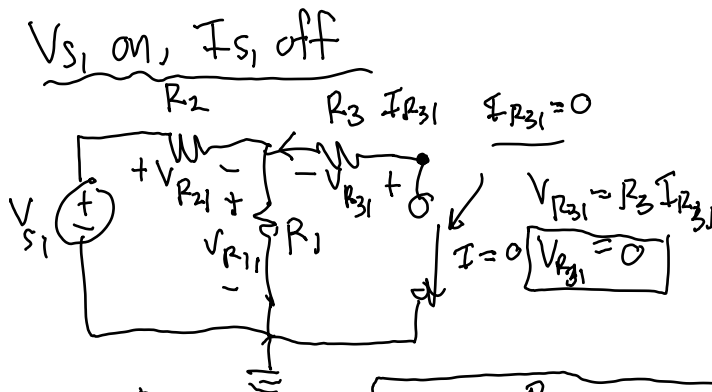

$$V_{R11} = \frac{R_1}{R_1 + R_2} V_{S1}$$

$$V_{R21} = \frac{R_2}{R_1 + R_2} V_{S1}$$
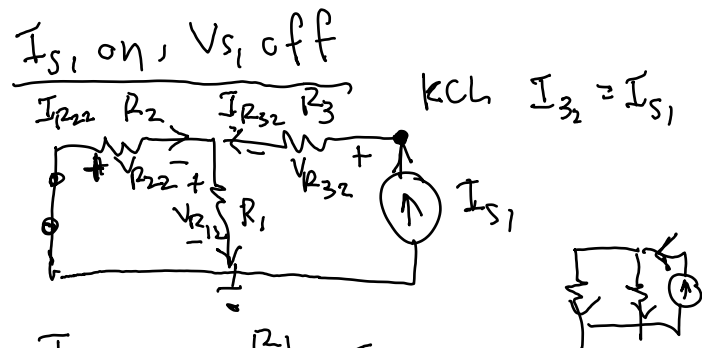
$$V_{R32} = I_{R32} \cdot R_3 = R_3 I_{S1}$$




$$I_{R22} = -\frac{R_1}{R_1 + R_2} I_{S1}$$

$$V_{R22} = R_2 I_{R22} = -\frac{R_2 R_1}{R_1 + R_2} I_{S1}$$

$$I_{R12} = \frac{R_2}{R_1 + R_2} I_{S1}$$
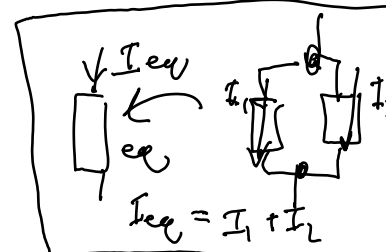
$$V_{R12} = \frac{R_1 R_2}{R_1 + R_2} I_{S1}$$



$$V_{R1} = V_{R11} + V_{R12} = \left[\frac{R_1}{R_1 + R_2} V_{S1} + \frac{R_1 R_2}{R_1 + R_2} I_{S1} \right]$$


$$V_{R2} = V_{R21} + V_{R22} = \left[\frac{R_2}{R_1 + R_2} V_{S1} - \frac{R_1 R_2}{R_1 + R_2} I_{S1} \right]$$

$$V_{R3} = V_{R31} + V_{R32} = 0 + R_3 I_{S1}$$

V_S off \rightarrow wire
 I_S off \rightarrow open


(b)

$V_{S1} = V_{S2} = V_{R1}$
 (parallel)

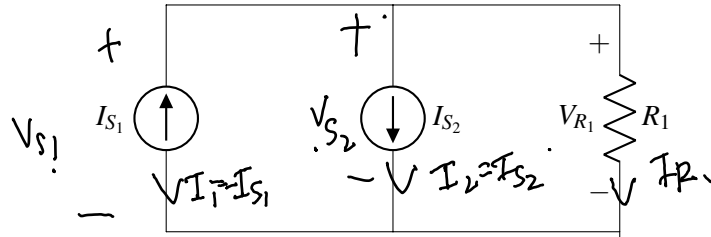

Don't calculate power in your subcircuit
~~PWR IS~~
 NOT LINEAR


I_{S1} on, I_{S2} off

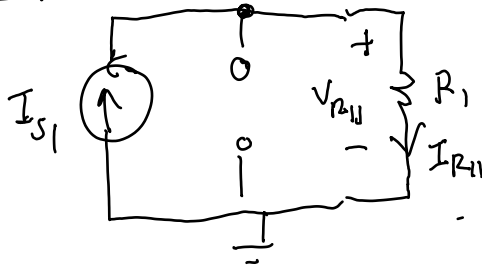

$I_{R11} = I_{S1}$ (KCL)

$V_{R11} = R_1 \cdot I_{S1}$

I_{S2} on, I_{S1} off

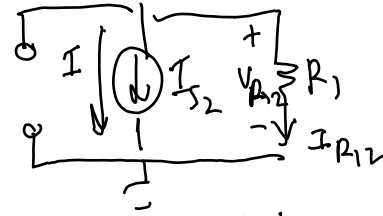

$I_{R12} = -I_{S2}$ (KCL @ top)

$V_{R12} = -R_2 \cdot I_{S2}$

By superposition:

$V_{R1} = V_{R11} + V_{R12}$
 $= R_1 \cdot I_{S1} - R_1 \cdot I_{S2}$

$I_{R1} = I_{S1} - I_{S2}$


Power

$P_{R1} = V_{R1} \cdot I_{R1} = R_1 (I_{S1} - I_{S2})^2 > 0$ (dissipating)


$P_{S1} = R_1 (I_{S1} - I_{S2}) (-I_{S1})$ ← can be positive or negative

$P_{S2} = R_1 (I_{S1} - I_{S2}) I_{S2}$ ← can be positive or negative

(c)

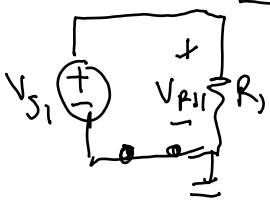


$V_{R11} = V_{S1}$

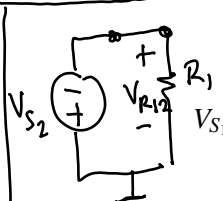

$V_{R12} = -V_{S2}$

$V_{R1} = V_{S1} - V_{S2}$

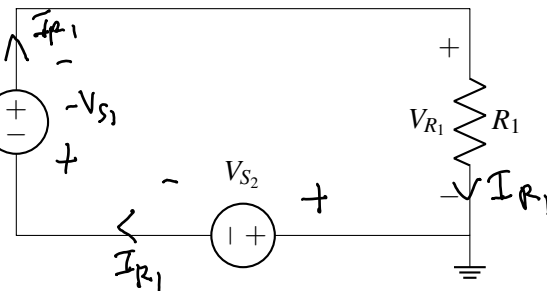$I_{R1} = \frac{V_{R1}}{R_1} = \frac{V_{S1} - V_{S2}}{R_1}$




$P_{R1} = \frac{(V_{S1} - V_{S2})^2}{R_1} > 0$

$P_{S1} = -V_{S1} \left(\frac{V_{S1} - V_{S2}}{R_1} \right)$ ← can be positive or negative

$P_{S2} = V_{S2} \left(\frac{V_{S1} - V_{S2}}{R_1} \right)$ ← can be positive or negative

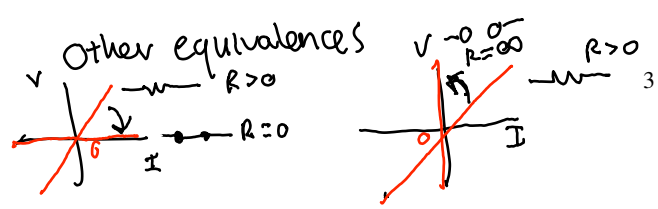$P = \frac{V^2}{R} > 0$
 $P = I^2 R > 0$
 Only for resistors!
 Resistors always dissipate! (also nonlinear)



2. (Practice) Series and Parallel Combinations


For the resistor network shown below, find an equivalent resistance between the terminals x and y using the resistor combination rules for series and parallel resistors.

Practice
 ① Choose a pair of any two resistors

② Test definitions


Note: sometimes things are neither series + parallel

③ Redraw (simplifying one at a time)




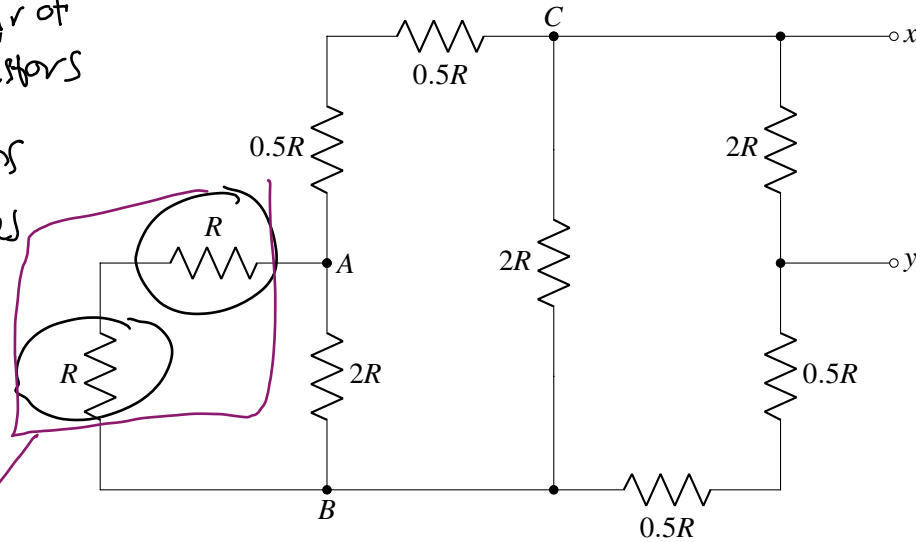


Defn of series
 Share one node
 nothing else on it

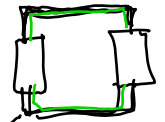Defn of parallel
 Share both pairs of nodes



$R_{eq, series} = R_1 + R_2$

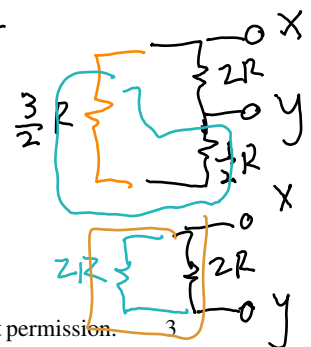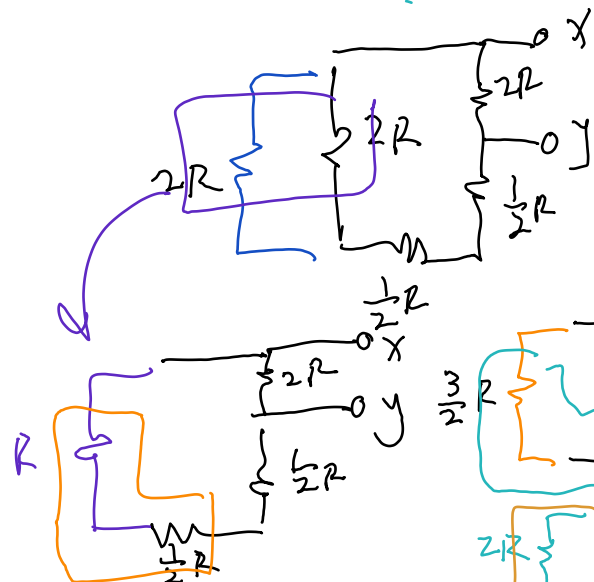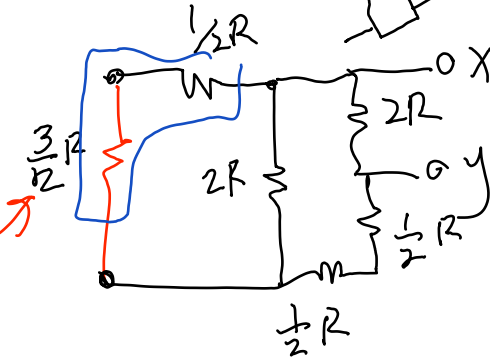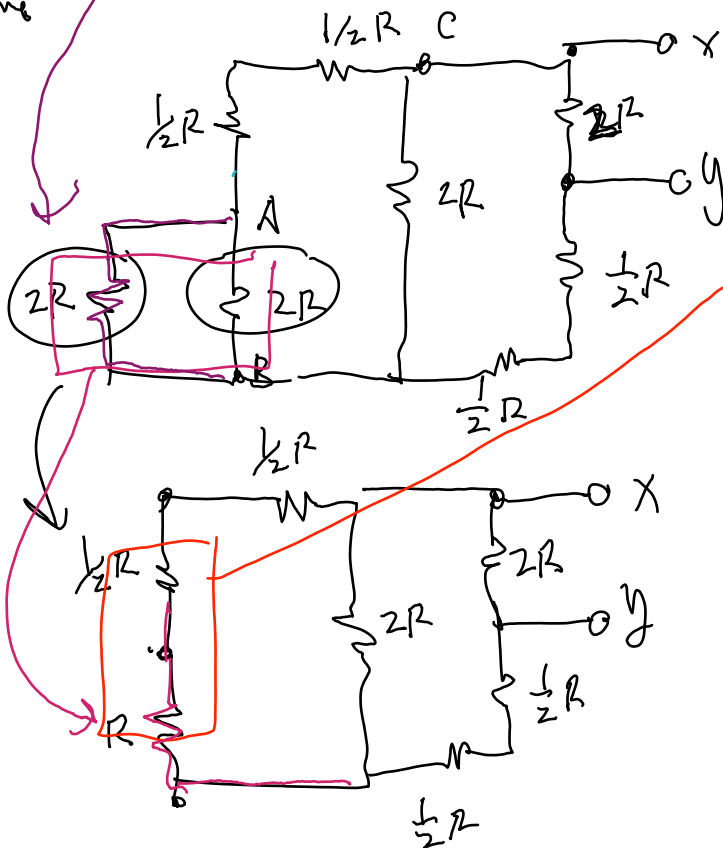


$$R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$



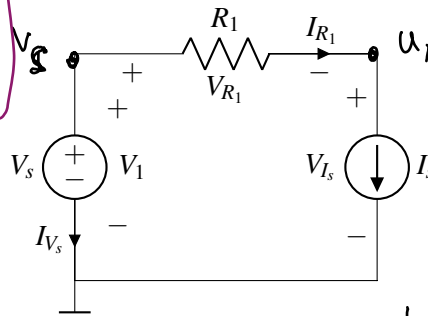3. (Practice) Passive Sign Convention and Power v 2.0

Suppose we have the following circuit and label the currents as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_S = 5\text{ V}$, $I_S = 0.5\text{ A}$ and $R_1 = 5\ \Omega$.

Voltages in parallel equal
Currents in series equal



NVA
KCL @ u_1

$$I_{R_1} = I_S$$

$$\frac{V_S - u_1}{R_1} = I_S$$

$$V_S - u_1 = R_1 I_S$$


$$V_S - R_1 I_S = u_1$$

Compute currents + voltages using NV's


Voltage source

$$\begin{aligned} V_1 &= V_S \\ I_{V_S} &= -I_{R_1} \text{ (KCL @ } V_S \text{ node)} \\ I_{V_S} &= -\frac{V_S - u_1}{R_1} \text{ (can use KCL)} \\ &= -\frac{V_S - (V_S - R_1 I_S)}{R_1} \\ &= \frac{R_1 I_S}{R_1} = I_S \end{aligned}$$

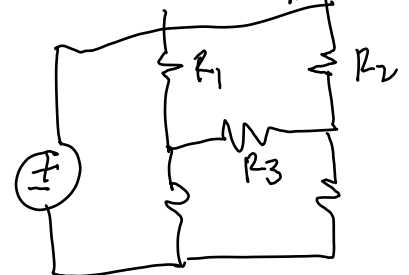Examples of neither series nor parallel
 R_1, R_2 not in parallel because of R_3



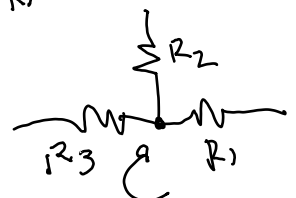R_1, R_2
 R_2, R_3
 R_3, R_1 Not in series



R_2, R_3 are not in parallel
 R_1, R_2 not in parallel

Current source

$$\begin{aligned} V_{I_S} &= u_1 - 0 \\ &= V_S - R_1 I_S \\ I_S &= I_S \end{aligned}$$

Resistor

$$\begin{aligned} V_{R_1} &= V_S - u_1 \\ &= V_S - (V_S - R_1 I_S) \\ &= R_1 I_S \text{ (know current by KCL, can use ohm's)} \\ I_{R_1} &= \frac{V_{R_1}}{R_1} = I_S \end{aligned}$$

$$P_{V_S} = V_1 I_{V_S} = V_S I_S > 0 \text{ (always supplying)}$$

$$P_{I_S} = V_{I_S} \cdot I_S = (V_S - R_1 I_S) I_S \text{ (can be supplying or dissipating)}$$

if I_S small enough dissipate
if I_S large enough supply

$$P_R = V_{R_1} \cdot I_{R_1} = R_1 I_S^2 > 0 \text{ (always dissipating)}$$