
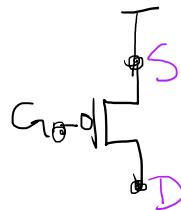
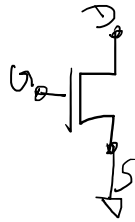
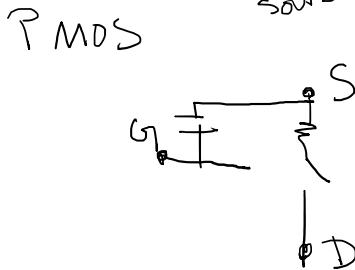


(post-lecture edits in purple)
 (useful eqns in green boxes)

Last time on EE16B...

Transistors

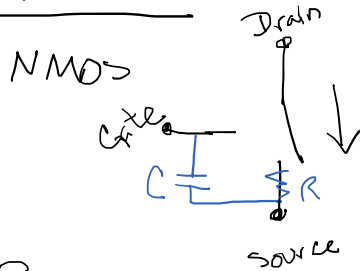

SWT closed when

$$V_G - V_S \geq V_{TH}$$



$$V_G \geq V_{TH}$$

$$V_S - V_G \geq V_{TH} = \frac{V_{DD}}{2}$$

$$\frac{V_{DD}}{2} \geq V_G$$

$$V_G \leq V_{TH}$$

Inverter

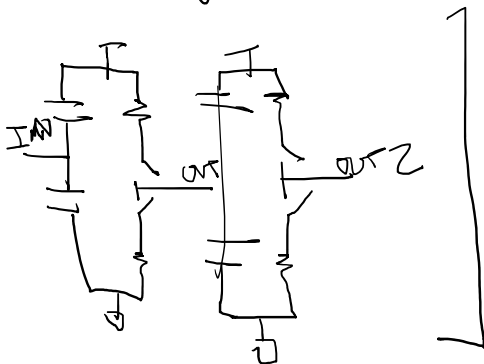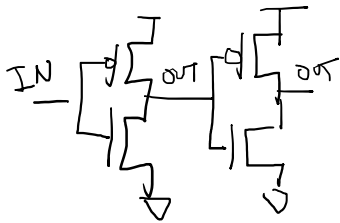

Energy / Transition


$$E = \frac{1}{2} C V_{DD}^2$$

If $I_N: V_{DD} \rightarrow 0$ @ t_0




Then PMOS open \rightarrow closed

NMOS closed \rightarrow open

OUT $0 \rightarrow VDD$ @ $t_0 + \Delta$

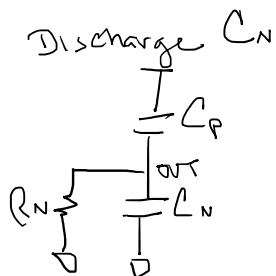

\Rightarrow

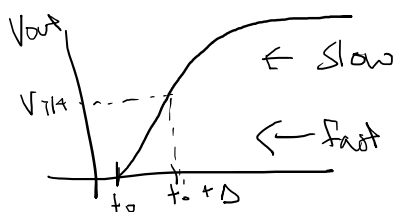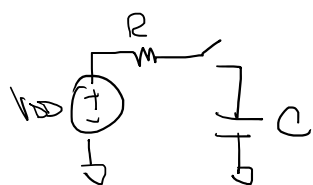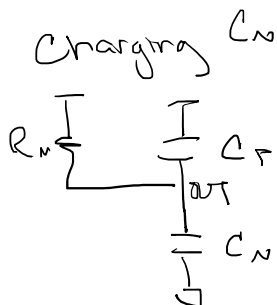

Delay

Motivation; Why care about delay?

Today

Differential Eqns

Homogeneous Eqns


Uniqueness & Existence Thm

Soln to $V_C(t)$


Transients

Time Constants

(1) (2) (3) (4)


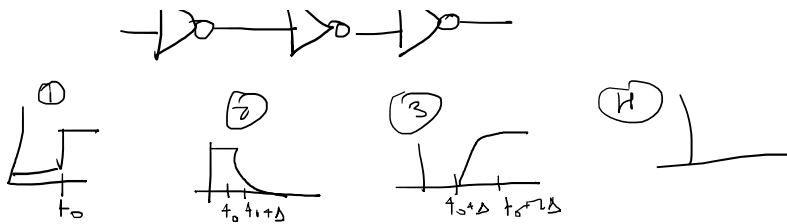


Want a fast CPU

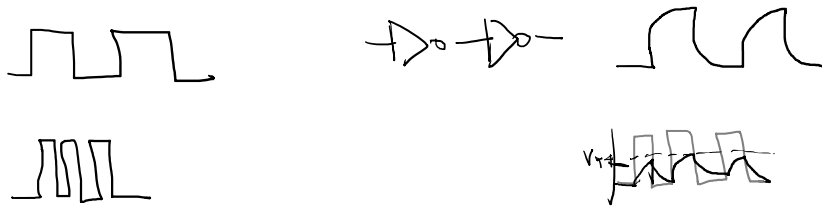


Application .Tangent

Good engineers make lemonade

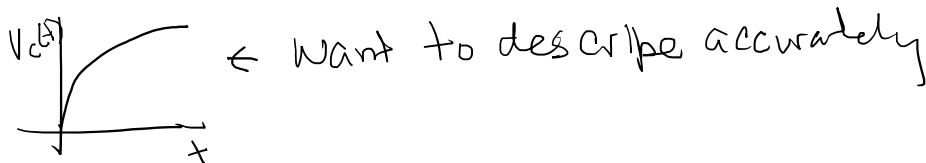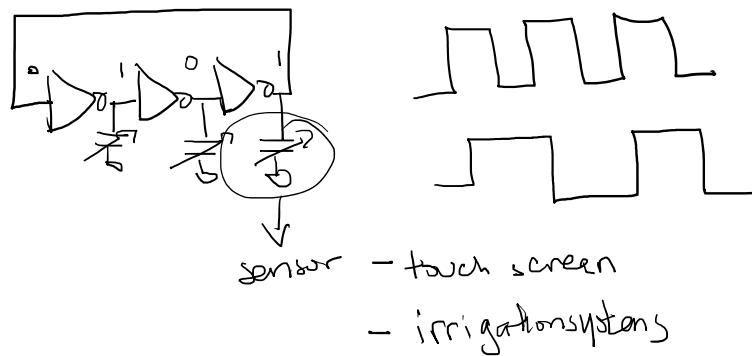


Goal I. Math model of RC circuit

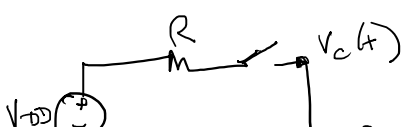

$$I_R = I_C$$

$$C \frac{d}{dt} V_C(t) = V_R(t) / R$$

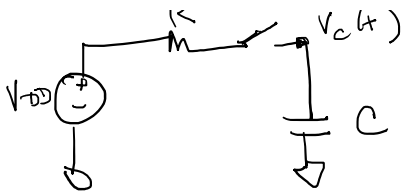

$$-R - +C$$

$$C \frac{d}{dt} V_C(t) = V_R(t)/R$$

$$\frac{d}{dt} V_C(t) = (V_{DD} - V_C(t))/RC$$

$$\frac{d}{dt} V_C(t) + \frac{1}{RC} V_C(t) = \frac{V_{DD}}{RC}$$

Diff Egn \longrightarrow

* Math Break *

Subgoal A: Solve for $V_C(t)$

Need: Diff Egn

Diff Egn warm up

$$\frac{d}{dt} x(t) = b$$

$$\int \frac{d}{dt} x(t) dt = \int b dt$$

$$x(t) = bt + k_c \quad \begin{array}{l} k_c = \text{some const} \\ \text{set by} \\ x(0) = x_0 \end{array}$$

General version

$$\frac{d}{dt} x(t) + ax(t) = b \quad \left(\frac{d}{dt} V_C(t) + \frac{1}{RC} V_C(t) = \frac{V_{DD}}{RC} \right)$$

Homogenous part

$$\frac{d}{dt} x(t) + ax(t) = 0$$

Homogenous Egn = diff egn where $x(t) = 0$ is valid

Thm :

$$x(t) = x_h(t) + x_p(t)$$

↑
general
sol'n homogenous
↑
particular
sol'n to partic

subsubgoal i: (get an idea of $x_h(t)$ to check x/A)

$$\frac{d}{dt} x(t) + a x(t) = 0$$

$$\frac{d}{dt} x(t) = -a x(t)$$

[side note: $\frac{d}{dt} f(x) = \lambda f(x)$ eigenfunction!]

Table of Basic Integrals¹

(1) $\int x^n dx = \frac{1}{n+1} x^{n+1}, n \neq -1$	(11) $\int \sec^2 x dx = \tan x$
(2) $\int \frac{1}{x} dx = \ln x $	(12) $\int \sec x \tan x dx = \sec x$
(3) $\int u dv = uv - \int v du$	(13) $\int \frac{a}{a^2 + x^2} dx = \tan^{-1} \frac{x}{a}$
(4) $\int e^x dx = e^x$	(14) $\int \frac{a}{a^2 - x^2} dx = \frac{1}{2} \ln \left \frac{x+a}{x-a} \right $
(5) $\int a^x dx = \frac{1}{\ln a} a^x$	(15) $\int \frac{1}{\sqrt{a^2 - x^2}} dx = \sin^{-1} \frac{x}{a}$
(6) $\int \ln x dx = x \ln x - x$	(16) $\int \frac{a}{x\sqrt{x^2 - a^2}} dx = \sec^{-1} \frac{x}{a}$
(7) $\int \sin x dx = -\cos x$	(17) $\int \frac{1}{\sqrt{x^2 - a^2}} dx = \cosh^{-1} \frac{x}{a}$ $= \ln(x + \sqrt{x^2 - a^2})$
(8) $\int \cos x dx = \sin x$	(18) $\int \frac{1}{\sqrt{x^2 + a^2}} dx = \sinh^{-1} \frac{x}{a}$ $= \ln(x + \sqrt{x^2 + a^2})$
(9) $\int \tan x dx = \ln \sec x $	
(10) $\int \sec x dx = \ln \sec x + \tan x $	

¹©2014. From <http://integral-table.com>, last revised June 14, 2014. This material is provided as is without warranty or representation about the accuracy, correctness or suitability of this material for any purpose. This work is licensed under the Creative Commons Attribution-NonCommercial-ShareAlike United States License.

Sol'n homogenous part

$$x(t) = C_0 e^{-at}, \quad x(0) = x_0$$

$$x(t) = x_0 e^{-at}$$

$$\frac{d}{dt} x(t) = -a x_0 e^{-at}$$

Uniqueness & Existence Thm

if a function solves a diff eqn then it is
correct & unique, as long as

(1) initial condition $x(t_0) = x_0$

(2) the soln of $x(t)$ is cont over the values
we care about, & contains that t_0

Subsubsub goal a.

Prove uniqueness thm \rightarrow HW, Note 1 Fall 19, pg 11

Have an idea of $x(t)$ what it should look like

$$x(t) = \underbrace{x_h(t)}_{x_0 e^{-at}} + x_p(t)$$

Solve $\frac{d}{dt} x(t) + ax(t) = b$ $x(0) = x_0$

$$\frac{d}{dt} x(t) = b - ax(t)$$

$$\int \frac{\frac{d}{dt} x(t)}{x(t) - b/a} = \int -a$$

$$\ln |x(t) - b/a| = -at + C, \quad C = \text{some const}$$

$$x(t) = b/a + C' e^{-at}, \quad C' = \text{some const}$$

Plug in $x(0) = x_0$


$$x(t) = b/a + (x_0 - b/a) e^{-at}$$

to check

Note 6a, pg 13

* Math Break Over! *

Solve for $v_c(t)$

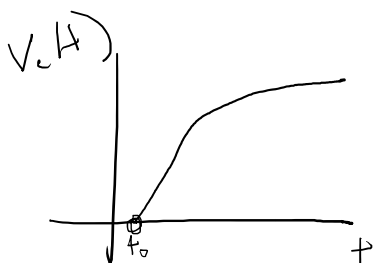

Math Form

$$\frac{d}{dt}x(t) + ax(t) = b$$

$$x(t) = b/a + (x_0 - b/a)e^{-at}$$


RC Form

$$\frac{d}{dt}V_c(t) + \frac{1}{RC}V_c(t) = \frac{V_{DD}}{RC}, \quad x(0) = x_0$$

$$V_c(t) = \frac{V_{DD}}{RC} \cdot \frac{1}{RC} + \left[0 - \frac{V_{DD}}{RC} \cdot \frac{1}{RC}\right] e^{-t/RC}$$

$$V_c(t) = V_{DD} - V_{DD} e^{-t/RC}$$

charging RC mathematical model

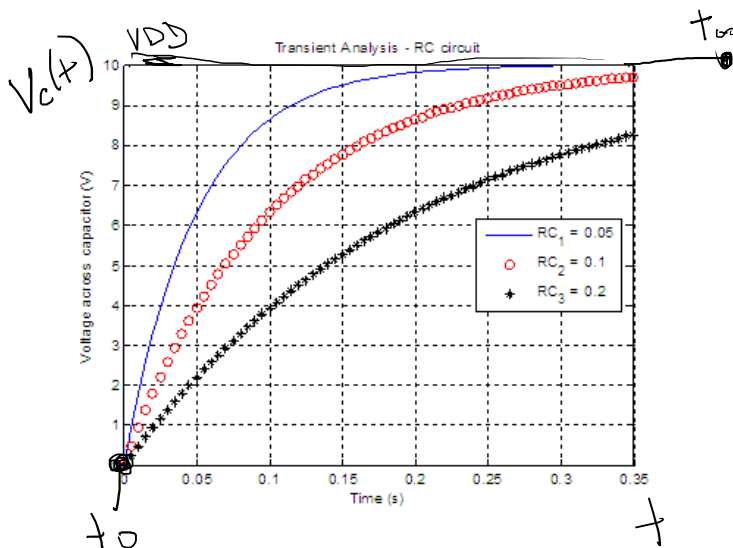

1. charges fast then slow ✓

2. $x(t_0) = 0$ ✓

$$V_c(t_0) = V_{DD} - V_{DD} e^{-t_0/RC} = V_{DD} - V_{DD}$$


3. $x(t_{\infty}) = V_{DD}$ ✓

$$V_c(t_{\infty}) = V_{DD} - V_{DD} e^{-t_{\infty}/RC} = V_{DD} - 0$$

Goal II. Explore Math Model

$$x(t) = A - Be^{-t/\tau}$$

$$\tau = RC$$

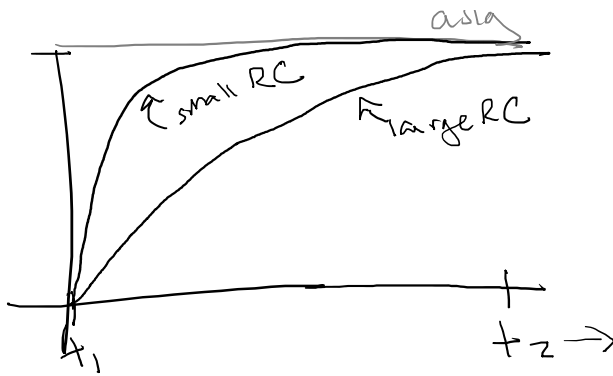



↓ + increasing

fast, not accurate: $\gamma \approx 2$ or 3

accurate, not fast: $\gamma \approx 5$ or larger

fast & accurate: RC smaller


Discharge an Inverter Output

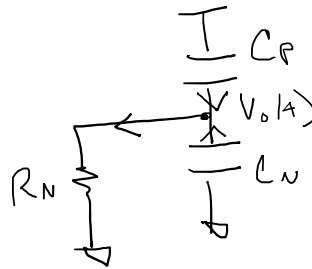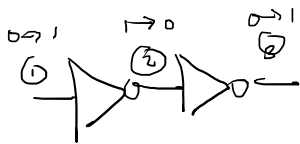

Impt Egn's

$$i_R(t) = \frac{V_o(t)}{R}$$

$$C \frac{d}{dt} V_o(t) = i_C(t)$$

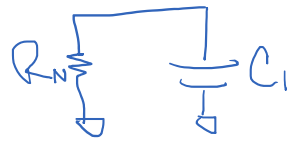

(KCL)

i_{C_P}

+

i_{C_N}

-

i_{R_N}

= 0

$$C_P \frac{d}{dt} (V_{DD} - V_o(t))$$

$$+ C_N \frac{d}{dt} (0 - V_o(t)) - \frac{(V_o(t) - 0)}{R} = 0$$

$$-C_P \frac{d}{dt} V_o(t) + -C_N \frac{d}{dt} V_o(t) - \frac{V_o(t)}{R} = 0$$

$$\frac{d}{dt} V_o(t) \underbrace{(C_N + C_P)}_{C_{II}} = -\frac{V_o(t)}{R} \quad \leftarrow \text{homogenous!}$$

$$V_o(t) = K e^{-t / R(C_N + C_P)}, \quad V_o(0) = V_{DD}$$

$$V_o(t) = V_{DD} e^{-t / R(C_N + C_P)}$$

Tomorrow : Time variant inputs through an RC



Scroll Move