

EECS16A DIS 9B

email: moseswan@berkeley.edu

OH: W 10AM-12PM (HWP)

Logistical details

- ① Don't forget MT2 next week
- ② Review sessions on Friday, Saturday

Learning Objectives

- ① How to identify floating nodes (where does charge conservation apply?)
- ② Charge sharing algorithm (finding voltages and charges in a switch-capacitor circuit)

Playlist (suggest @ Ita jukebox)



- ① Troyboi - ili
(suggested by Lucy)
- ② H.E.R. - Best Part
ft. Daniel Caesar
- ③ MONSUNE -
Outta my mind

EECS 16A Designing Information Devices and Systems I

Fall 2020 Discussion 9B

1. Capacitors and Charge Conservation

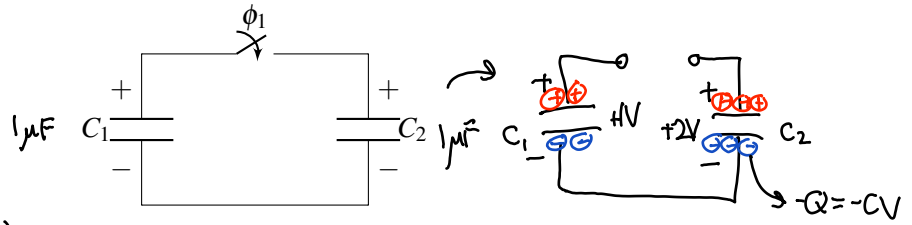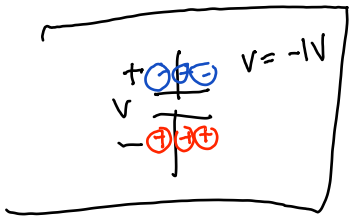
- (a) Consider the circuit below with $C_1 = C_2 = 1\ \mu\text{F}$ and an open switch. Suppose that C_1 is initially charged to $+1\ \text{V}$ and that C_2 is charged to $+2\ \text{V}$. How much charge is on C_1 and C_2 ?





$$\begin{aligned} \rightarrow Q_1 &= (1\mu\text{F})(1\text{V}) = 1\mu\text{C} \\ Q_2 &= (1\mu\text{F})(2\text{V}) = 2\mu\text{C} \end{aligned}$$

$$Q = CV$$

positive

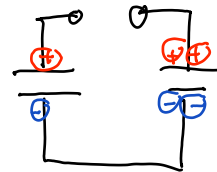

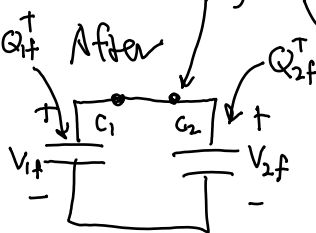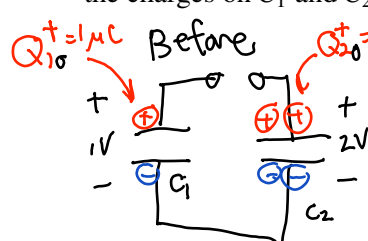(b) Now the switch is closed (i.e. the capacitors are connected together.) What are the voltages across and the charges on C_1 and C_2 ?



Charge conservation

$$Q_{1i} + Q_{2i} = Q_{1f} + Q_{2f}$$

$$\Rightarrow 1\mu\text{C} + 2\mu\text{C} = Q_{1f} + Q_{2f}$$

$V_{1f} = V_{2f}$ (why? parallel)

$$V_{1f} = \frac{Q_{1f}}{C_1} \quad (Q=CV)$$

$$V_{2f} = \frac{Q_{2f}}{C_2}$$

$$\Rightarrow \frac{Q_{1f}}{C_1} = \frac{Q_{2f}}{C_2} \quad C_1 = C_2 = 1\mu\text{F}$$

simplifies \uparrow

$$Q_{1f} = Q_{2f}$$


$$3\mu\text{C} = Q_{1f} + Q_{2f} = 2Q_{1f} \Rightarrow Q_{1f} = \frac{3\mu\text{C}}{2} = 1.5\mu\text{C}$$

$$\Rightarrow Q_{2f} = 1.5\mu\text{C}$$

$$V_{1f} = V_{2f} = \frac{1.5\mu\text{C}}{1\mu\text{F}} = 1.5\text{V}$$

Floating node

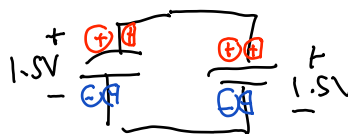- node from which charge cannot escape or enter
- connected to opens or only capacitor plates
- Charge conservation applies



Since charge cannot leave the top node, then the total charge must stay the same

$$Q_{1i} + Q_{2i} = Q_{1f} + Q_{2f}$$


$$Q_{1i} \neq Q_{1f} \quad (\text{not always})$$

$$Q_{2i} \neq Q_{2f} \quad (\text{not always})$$


$$Q_{1i} \neq Q_{2f} \quad (\text{not always})$$

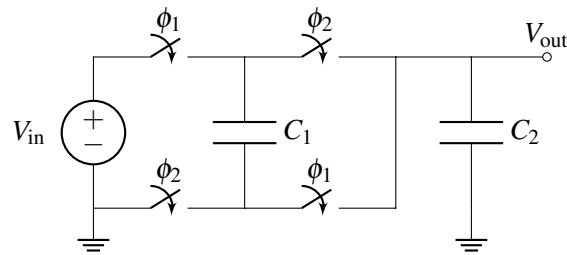2. Charge Sharing

Consider the circuit shown below. In phase ϕ_1 , the switches labeled ϕ_1 are on while the switches labeled ϕ_2 are off. In phase ϕ_2 , the switches labeled ϕ_2 are on while the switches labeled ϕ_1 are off.





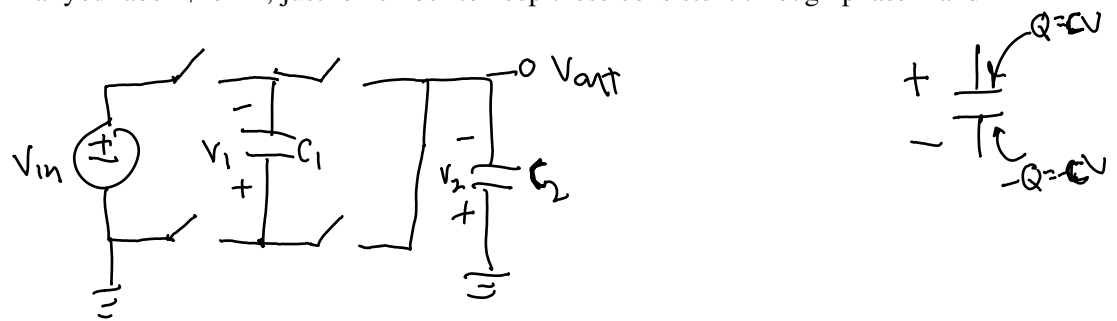- (a) Draw the polarity of the voltage (using + and - signs) across the two capacitors C_1 and C_2 . (It doesn't matter which terminal you label + or -; just remember to keep these consistent through phase 1 and 2!)





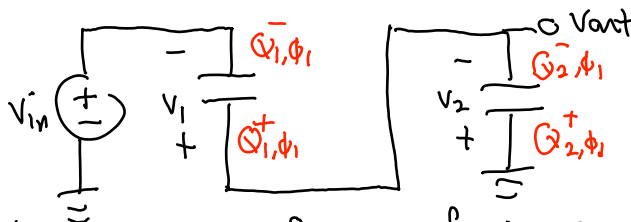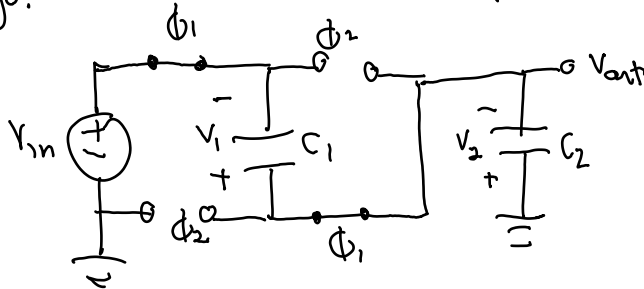(b) Redraw the circuit in phase ϕ_1 and phase ϕ_2 . Keep your polarity from part (a) in mind.

Phase ϕ_1 (ϕ_1 switches closed - shorts/wires)
 ϕ_2 switches open



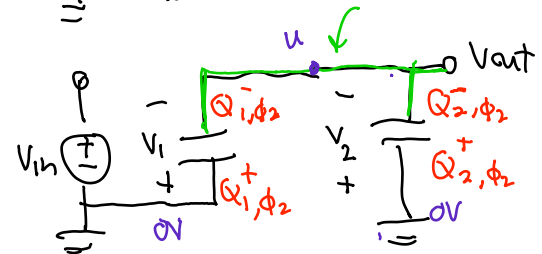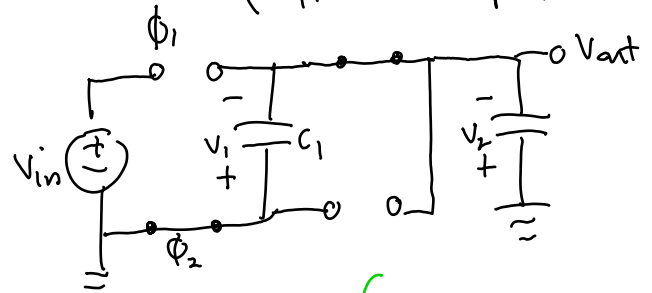Phase ϕ_2 (ϕ_2 switches closed/shorts/wires)
 ϕ_1 switches open





(c) Find V_{out} as a function of V_{in} , C_1 , and C_2 in phase ϕ_2

III Identify all floating nodes in phase ϕ_2 $Q = CV$

IV For each floating node compute charges and write conservation equations

$$Q_{1,\phi_1}^- + Q_{2,\phi_1}^- = Q_{1,\phi_2}^- + Q_{2,\phi_2}^- \quad (1)$$

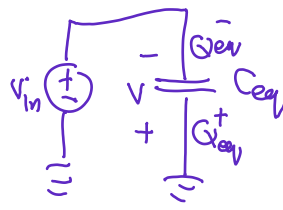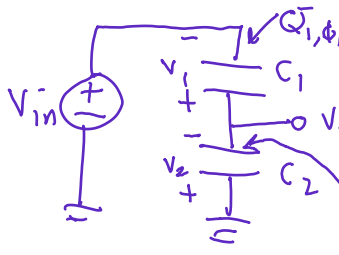charge conservation.
at floating node with
node voltage u .



$$V = -V_{in}$$

$$Q_{eq}^- = -C_{eq}V = -C_{eq}(-V_{in}) = C_{eq}V_{in}$$

$$C_{eq} = C_1 || C_2 = \frac{C_1 C_2}{C_1 + C_2}$$

☆ All capacitors are discharged in phase ϕ_1 before V_{in} charges them

$$Q_{eq}^- = Q_{1,\phi_1}^- = Q_{2,\phi_1}^- = \frac{C_1 C_2}{C_1 + C_2} V_{in} \quad (2) \quad \text{Coming from series equivalence in } \phi_1$$

$$Q_{1,\phi_2}^- = -C_1 V_1$$

$$Q_{2,\phi_2}^- = -C_2 V_2$$

$$\frac{2 C_1 C_2}{C_1 + C_2} V_{in} = Q_{1,\phi_2}^- + Q_{2,\phi_2}^-$$


$$= -C_1 (0 - u) - C_2 (0 - u) = C_1 u + C_2 u$$

☆ use node voltages
 $V_1 = V_2 = 0 - u$

$$\frac{2 C_1 C_2}{C_1 + C_2} V_{in} = u (C_1 + C_2) \Rightarrow u = \frac{2 C_1 C_2}{(C_1 + C_2)^2} V_{in} = V_{out}$$

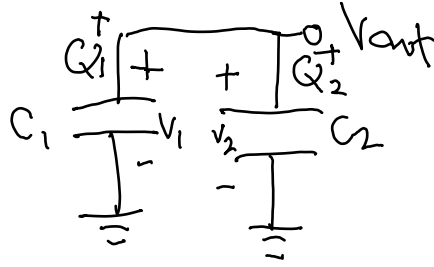(d) How will the charges be distributed in phase ϕ_2 if we assume $C_1 \gg C_2$?

$$V_{out} = \frac{2C_1C_2}{(C_1+C_2)^2} V_{in}$$



$$V_1 = V_2 = V_{out}$$

$$Q_1^+ = C_1 V_1$$

$$Q_2^+ = C_2 V_2$$

$$= \frac{2C_1^2 C_2}{(C_1+C_2)^2} V_{in}$$

$$= \frac{2C_2^2 C_1}{(C_1+C_2)^2} V_{in}$$

$$\lim_{C_1 \rightarrow \infty} Q_1^+ = \lim_{C_1 \rightarrow \infty} \frac{2C_1^2 C_2}{(C_1+C_2)^2} V_{in}$$

$$= \lim_{C_1 \rightarrow \infty} \frac{2C_2}{(1+\frac{C_2}{C_1})^2} V_{in}$$

$$= \frac{2C_2}{(1+0)^2} V_{in} = \boxed{2C_2 V_{in}}$$



$$\lim_{C_1 \rightarrow \infty} Q_2^+ = \lim_{C_1 \rightarrow \infty} \frac{2C_2^2 C_1}{(C_1+C_2)^2} V_{in}$$

$$= \lim_{C_1 \rightarrow \infty} \frac{2\frac{C_2^2}{C_1}}{(1+\frac{C_2}{C_1})^2} V_{in}$$


$$= \frac{2 \cdot 0}{(1+0)^2} V_{in} = \boxed{0}$$

Intuition for $C_1 \gg C_2 \Rightarrow$ The charge mostly goes on the larger capacitor! (C_1)


Phase ϕ_1

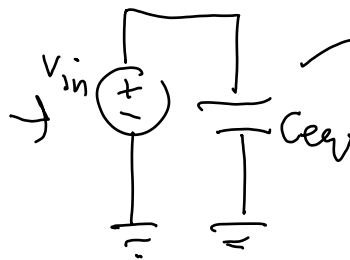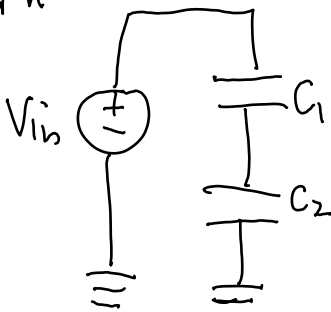


$$C_{eq} = C_1 || C_2 = \frac{C_1 C_2}{C_1 + C_2}$$

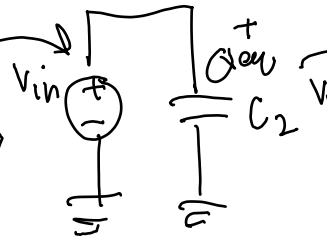
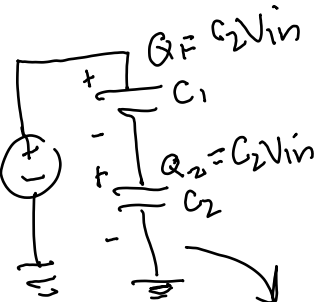
$$Q_{eq}^+ = C_{eq} V_{in} = C_2 V_{in}$$



Phase ϕ_2

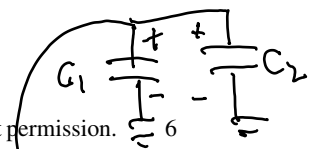

$$Q_{total} = 2C_2 V_{in}$$

($V_1 = \frac{Q_1}{C_1}$) C_1 looks like a short to C_2 .

$$\lim_{C_1 \rightarrow \infty} C_{eq} = C_2$$