


To do : Phasors!

- ① Motivation behind phasors
- ② Defining a phasor [1(a)]
- ③ Why the phasor domain is useful? [1(b), (d)]
- ④ Converting back and forth between domains [1(e), (f)]

### Complex #s

- $z = a + bj \Leftrightarrow z = |z| e^{j\theta}$
- ↳  $|z| = \sqrt{a^2 + b^2}$ ,  $\theta = \text{atan2}(b, a)$
- $z_1 \cdot z_2 = |z_1| \cdot |z_2| e^{j(\theta_1 + \theta_2)}$
- $\frac{z_1}{z_2} = \frac{|z_1|}{|z_2|} e^{j(\theta_1 - \theta_2)}$

### Phasor Motivation

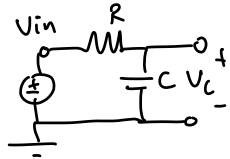Recall:   $\frac{dV_c(t)}{dt} = \frac{V_{in} - V_c}{RC} \rightarrow$  solve via change of variable

Key Assumption:  $V_{in}$  is a constant

Today: What if  $V_{in}(t)$  is a sinusoidal wave? e.g.  $V_{in}(t) = 5 \cos(2t)$

Phasor Domain: I can view the circuit in a different world

We define any time-varying  $x(t)$  [ $V_{in}(t)$ ] can be expressed as

$$x(t) = \tilde{X} e^{j\omega t} + \tilde{X}^* e^{-j\omega t} \quad (1)$$

$\uparrow$   
"phasor" of  $x(t)$

$\rightarrow \cos\theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$

Step 1 [1(a)]  $V_s(t) = 12 \sin(\omega t - \frac{\pi}{4})$


$$V_s(t) = 12 \left( \frac{e^{j(\omega t - \frac{\pi}{4})} - e^{-j(\omega t - \frac{\pi}{4})}}{2j} \right)$$

$$= 12 \left( \frac{e^{j\omega t} e^{-j\frac{\pi}{4}}}{2j} - \frac{e^{-j\omega t} e^{j\frac{\pi}{4}}}{2j} \right)$$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$\sin(\theta) = \cos(\theta - \frac{\pi}{2})$$

Convert  $j$ :  $j = e^{j\frac{\pi}{2}}$

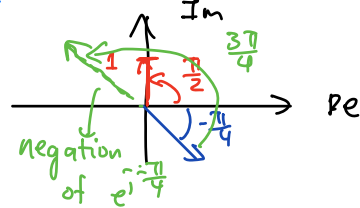

$$-e^{-j\frac{\pi}{4}} = ?? + \underline{\underline{\quad}}$$

$$= 6e^{j\omega t} e^{-j\frac{3\pi}{4}} - 6e^{-j\omega t} e^{j\frac{\pi}{4}}$$

$$= 6e^{-j\frac{3\pi}{4}} e^{j\omega t} + 6e^{j\frac{3\pi}{4}} e^{-j\omega t}$$

$$= \underline{\underline{6e^{-j\frac{3\pi}{4}}}} e^{j\omega t} + 6e^{-j\frac{3\pi}{4}} e^{-j\omega t}$$

$\tilde{X} \therefore$  phasor of  $V_s(t) = 6e^{-j\frac{3\pi}{4}}$

Alternate Way:  $V_s(t) = 12 \sin(\omega t - \frac{\pi}{4})$

$$= 12 \cos(\omega t - \frac{\pi}{4} - \frac{\pi}{2}) = 12 \cos(\omega t - \frac{3\pi}{4})$$

$$= 12 \left( \frac{e^{j(\omega t - \frac{3\pi}{4})} + e^{-j(\omega t - \frac{3\pi}{4})}}{2} \right)$$


$$= 6e^{j\omega t} e^{-j\frac{3\pi}{4}} + 6e^{-j\omega t} e^{j\frac{3\pi}{4}}$$

$\tilde{X} = 6e^{-j\frac{3\pi}{4}}$  ① polar form — magnitude  
phase


\*\*\* Conversion between time domain & phasor domain


$$V(t) = V_0 \cos(\omega t + \phi) \iff \tilde{V} = \frac{V_0}{2} e^{j\phi}$$

Step 2: Convert circuit

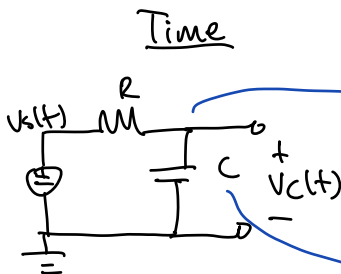

KCL, KVL, NVA hold in the phasor domain!

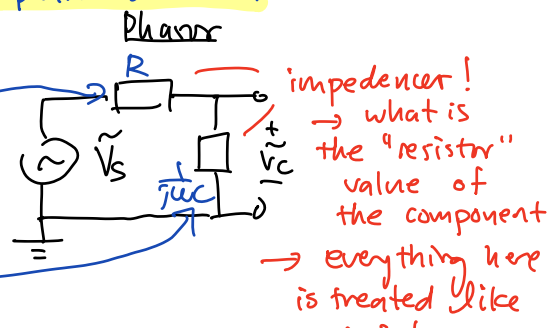

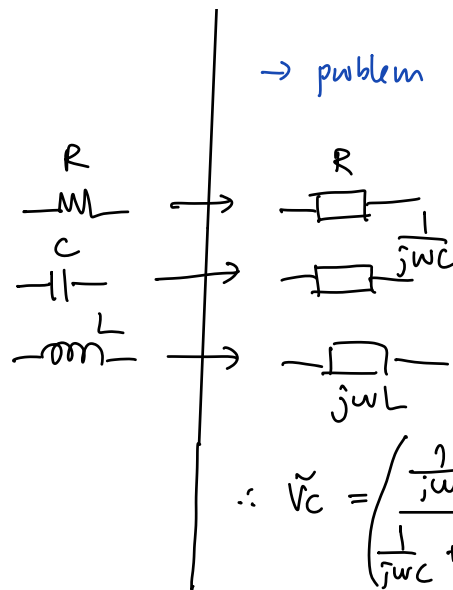


a resistor

→ problem becomes voltage divider!

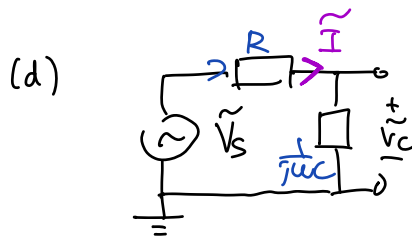(b)  $Z_R = R = \sqrt{3} \cdot 10^3 \Omega$   
 $Z_C = \frac{1}{j\omega C}$   
 $= \frac{1}{j \cdot 10^3 \cdot 10^{-6}} = -10^3 j$

$$\therefore \tilde{V}_C = \left( \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right) \tilde{V}_S$$



$$\tilde{I} = \frac{\tilde{V}_S}{Z_R + Z_C} = \frac{\tilde{V}_S}{\sqrt{3} \cdot 10^3 - 10^3 j} = \frac{6e^{-j\frac{3\pi}{4}}}{\sqrt{3} \cdot 10^3 - 10^3 j}$$

(e), (f) Convert our "solution" back to time domain

$$V(t) = V_0 \cos(\omega t + \phi) \iff \tilde{V} = \frac{V_0}{2} e^{j\phi}$$

Complex #s

•  $z = a + bj \iff z = |z| e^{j\theta}$

↳  $|z| = \sqrt{a^2 + b^2}$ ,  $\theta = \arctan 2(b, a)$

•  $z_1 \cdot z_2 = |z_1| \cdot |z_2| e^{j(\theta_1 + \theta_2)}$


•  $\frac{z_1}{z_2} = \frac{|z_1|}{|z_2|} e^{j(\theta_1 - \theta_2)}$

$z_1 = |z_1| e^{j\theta_1}$   
 $z_2 = |z_2| e^{j\theta_2}$

$$\tilde{I} = \frac{6e^{-j\frac{3\pi}{4}}}{\sqrt{3} \cdot 10^3 - 10^3 j} \text{ from (d)}$$

$$\therefore |\tilde{I}| = \left| \frac{6e^{j\frac{3\pi}{4}}}{\sqrt{3} \cdot 10^3 - 10^3 j} \right| = \frac{|6e^{j\frac{3\pi}{4}}|}{|\sqrt{3} \cdot 10^3 - 10^3 j|} = \frac{6}{\sqrt{(\sqrt{3} \cdot 10^3)^2 + (10^3)^2}} = (3 \times 10^{-3})$$
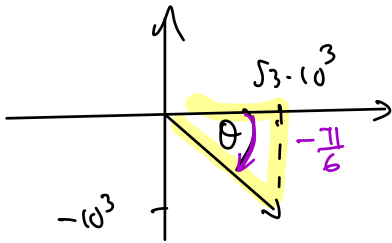
$$\begin{aligned} \therefore \angle \tilde{I} &= \angle 6e^{j\frac{3\pi}{4}} - \angle (\sqrt{3} \cdot 10^3 - 10^3 j) \\ &= -\frac{3\pi}{4} - \left( -\frac{\pi}{6} \right) = -\frac{7\pi}{12} \end{aligned}$$



$$\begin{aligned} \tan \theta &= \frac{10^3}{\sqrt{3} \cdot 10^3} \\ \theta &= \arctan\left(\frac{1}{\sqrt{3}}\right) = \frac{\pi}{6} \end{aligned}$$

$$\tilde{I} = (3 \times 10^{-3}) e^{j(-\frac{7\pi}{12})}$$



$$i(t) = 2 \cdot (3 \times 10^{-3}) \cos(\omega t - \frac{7\pi}{12})$$

$$v(t) = V_0 \cos(\omega t + \phi) \iff \tilde{V} = \frac{V_0}{2} e^{j\phi}$$

Extra time

$$\therefore \tilde{V}_C = \left( \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \right) \cdot \tilde{V}_S$$


$$\tilde{V}_C = \frac{1}{1 + j\omega RC} \cdot \tilde{V}_S$$

$$= \frac{1}{1 + \sqrt{3}j} \tilde{V}_S = \frac{1}{(1 + \sqrt{3}j)} \cdot 6e^{j\frac{3\pi}{4}}$$

convert to polar form

$$\cdot \left| \frac{1}{1 + \sqrt{3}j} \right| = \frac{|1|}{|1 + \sqrt{3}j|} = \frac{1}{2}$$
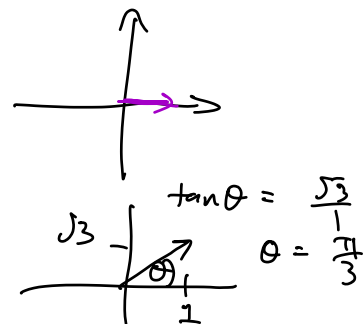
$$\begin{aligned} \cdot \angle \left( \frac{1}{1 + \sqrt{3}j} \right) &= \angle 1 - \angle (1 + \sqrt{3}j) \\ &= 0 - \frac{\pi}{3} = -\frac{\pi}{3} \end{aligned}$$



$$\tilde{V}_c = \frac{1}{2} e^{j(-\frac{\pi}{3})} \cdot 6 e^{j\frac{3\pi}{4}}$$

$$= 3 e^{j(-\frac{13\pi}{12})}$$

$$V_c(t) = 6 \cos(\omega t - \frac{13\pi}{12})$$

$$V(t) = V_0 \cos(\omega t + \phi) \iff \tilde{V} = \frac{V_0}{2} e^{j\phi}$$

$$\frac{z_1}{z_2} = \frac{(z_1 e^{j\theta_1})}{(z_2 e^{j\theta_2})} = \frac{|z_1|}{|z_2|} e^{j(\theta_1 - \theta_2)}$$