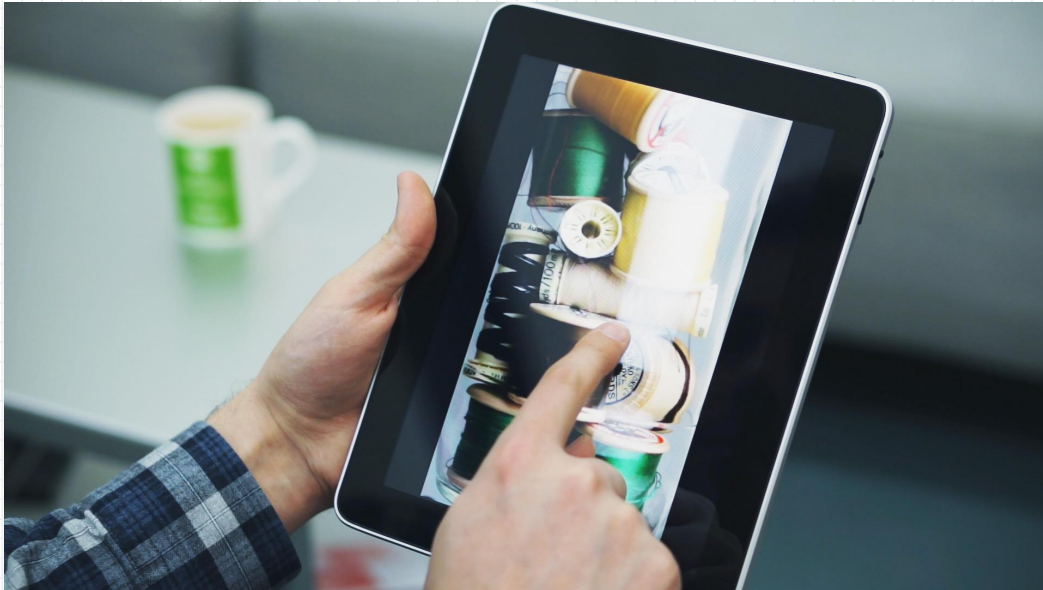


EECS16A Lab: Touchscreen 3




Capacitive Touchscreens



Electronic Systems

Most systems perform 3 tasks:

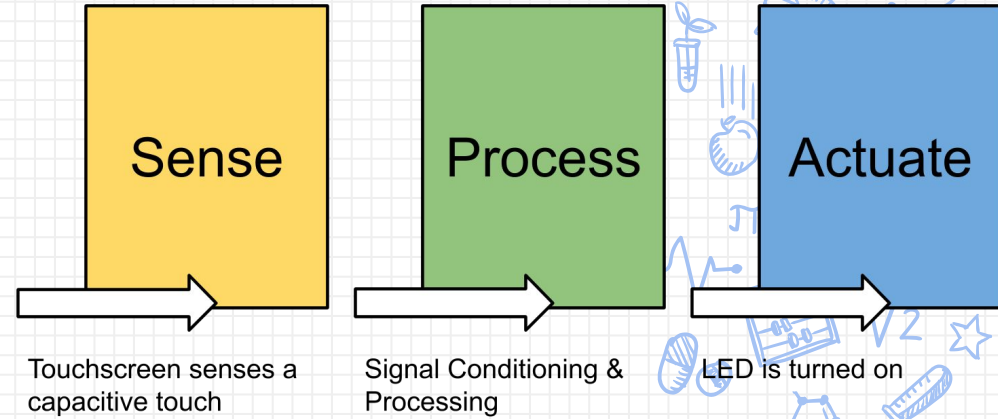- ✗ Sense (Physical to Electrical)
- ✗ Process (Signal Conditioning)
- ✗ Actuate (Electrical to Physical)



- ✗ Understand charge-sharing circuit for a capacitive touch sensor
- ✗ Understand comparators
- ✗ Build a functioning Touch Pixel

[illegible]
$$E = mc^2$$


-




- ✗ Model finger as another capacitor in parallel with our capacitive touch sensor
- ✗ How does the capacitance of what we're charging change?

- ✗ Model finger as another capacitor in parallel with our capacitive touch sensor
- ✗ How does the capacitance of what we're charging change?



Poll Time!

When you touch the screen, what will happen to C_{pixel} ?


- (A) Increase
- (B) Decrease

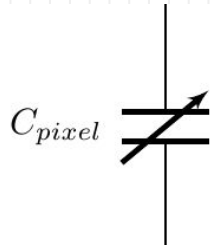


=

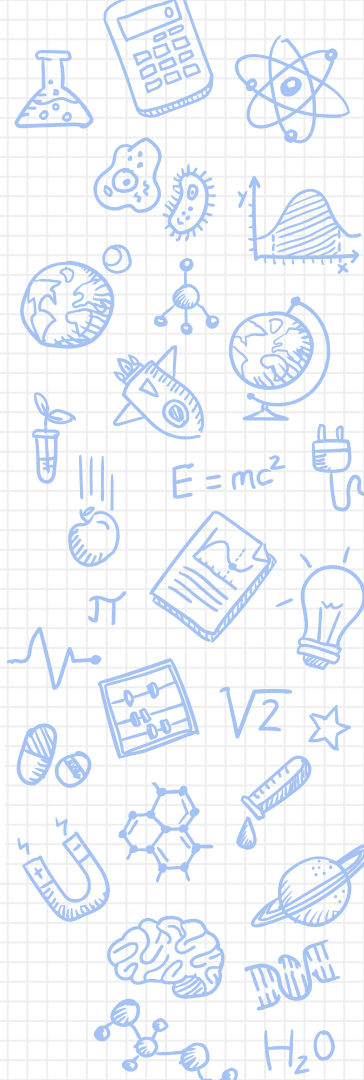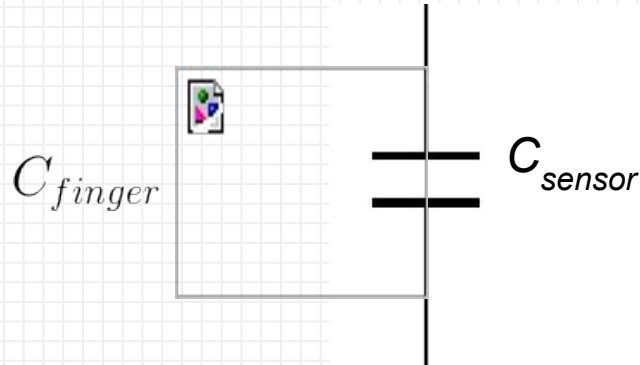


-

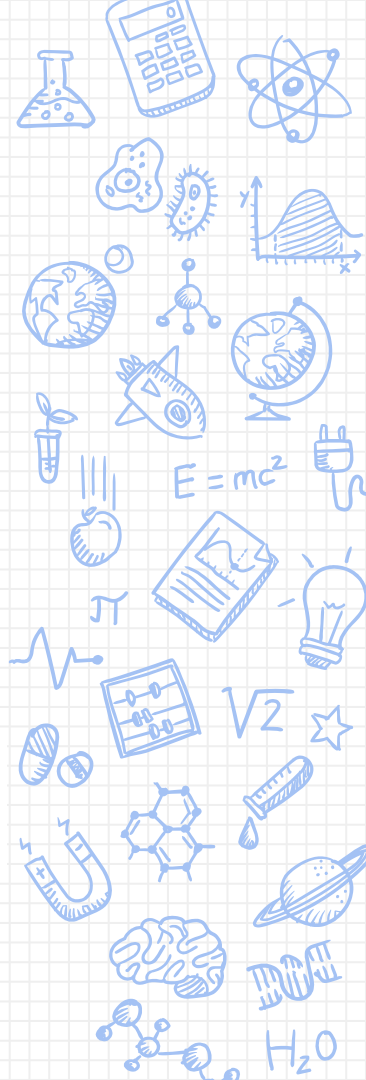

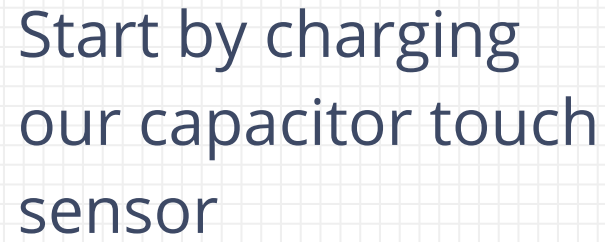


Start by charging
our capacitor touch
sensor

Measuring Capacitance

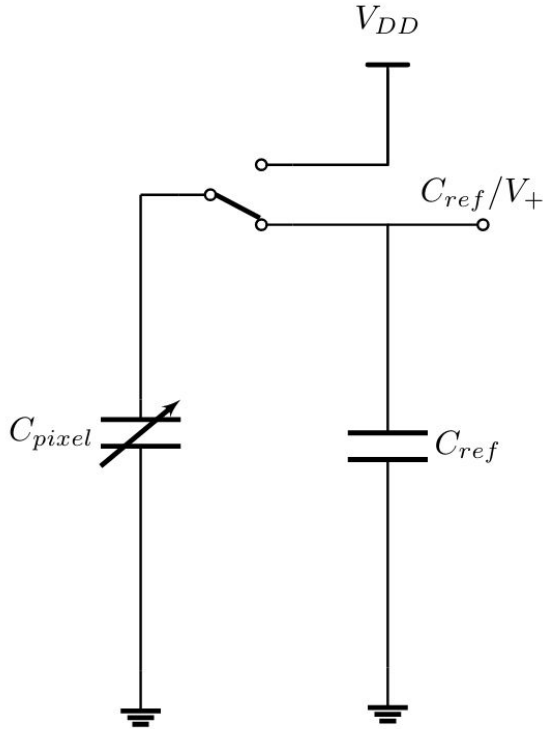


Charge-sharing
invariant: $Q = CV$

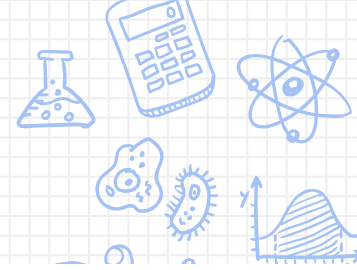

Poll Time!

When the charge is shared across C_{pixel} and C_{ref} , what will happen to the voltage at the positive plate of C_{pixel} ?

- (A) Increase
- (B) Decrease

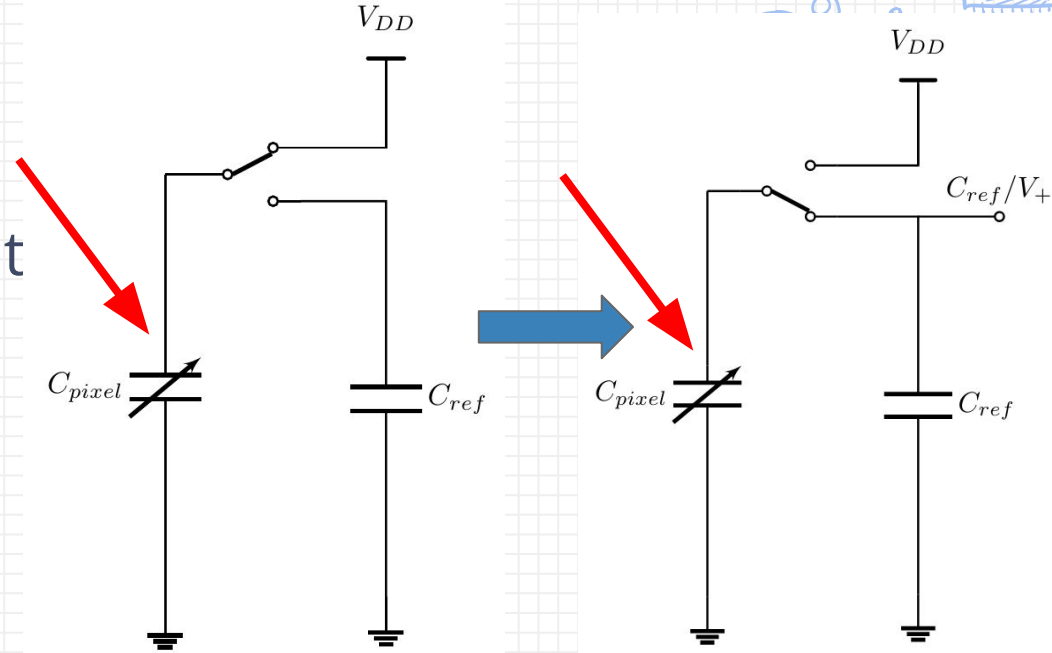


$$Q = CV$$



Poll Time! (cont.)

When the charge is shared across C_{pixel} and C_{ref} , what will happen to the voltage at the positive plate of C_{pixel} ?

- (A) Increase
- (B) **Decrease**

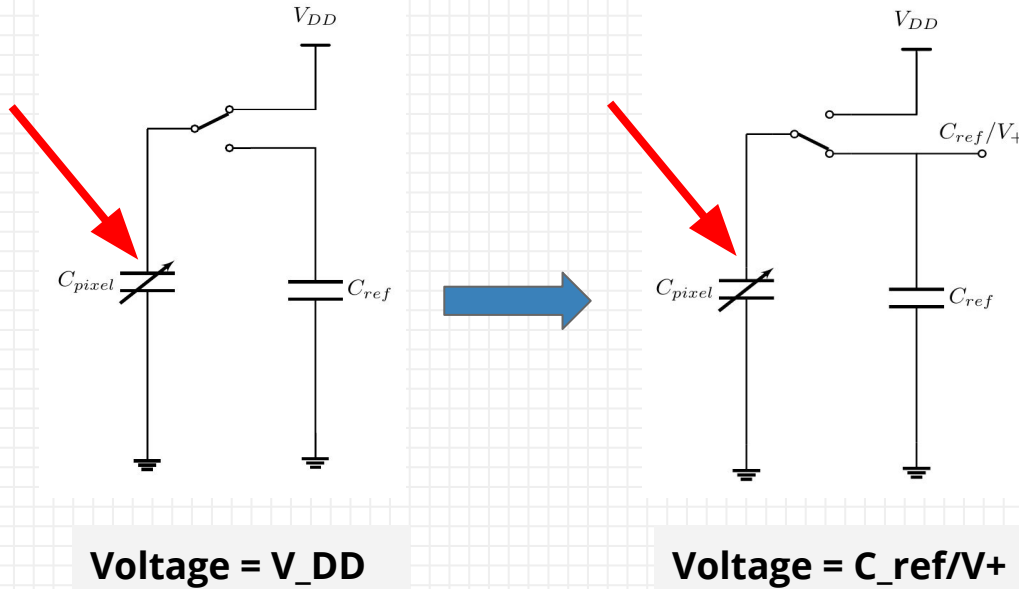

$$Q = C_{pixel} * V_{DD}$$

$$Q = (C_{ref}/V+)(C_{pixel}) + (C_{ref}/V+)(C_{ref})$$

Charge is conserved:


$$C_{pixel} * V_{DD} = (C_{pixel} + C_{ref}) * (C_{ref}/V+)$$

$$(C_{ref}/V+) = \frac{C_{pixel} * V_{DD}}{(C_{pixel} + C_{ref})}$$

$$(C_{ref}/V+) < V_{DD}$$

Measuring Capacitance: Full Cycle

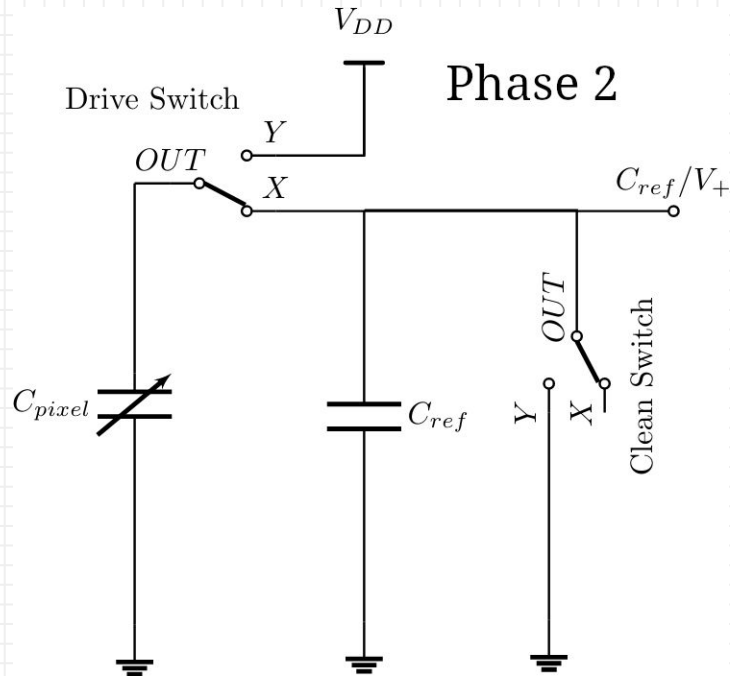
2. Disconnect clean switch from ground to enable charge storing




3. Charge touchscreen (+ finger?)

Applying this equation: $Q = CV$

$$Q_{Phase3} = C_{pixel} * V_{DD}$$

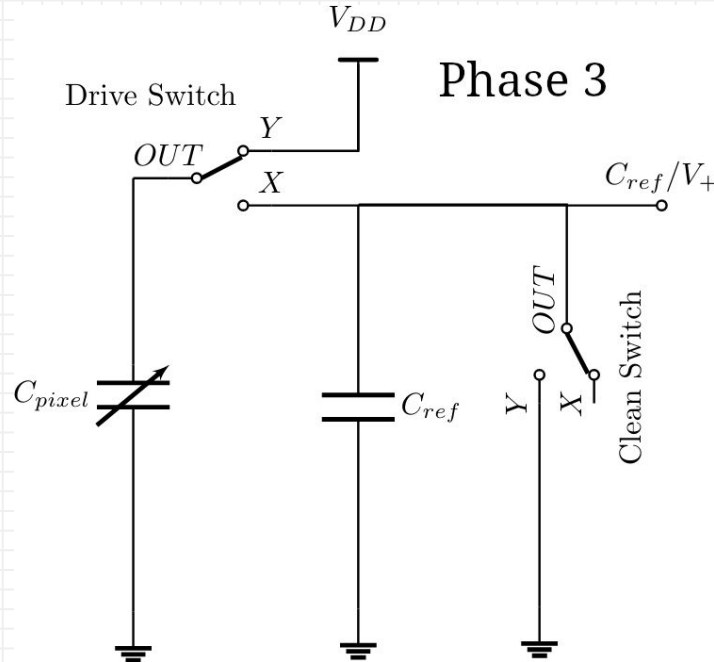

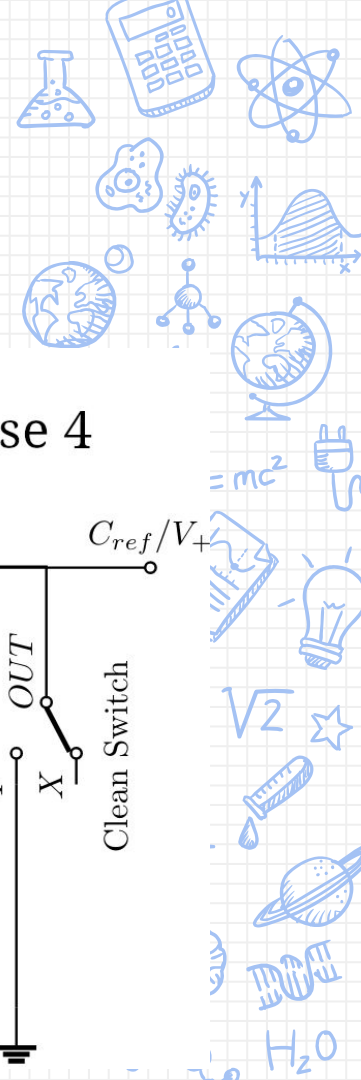

Measuring Capacitance: Full Cycle

4. Share charge between **C_pixel** and **C_ref**


Charge is conserved between phases

$$Q_{Phase3} = Q_{Phase4} = C_{pixel} * V_{DD}$$

$$Q_{Phase4} = (C_{ref}/V+) * (C_{pixel} + C_{ref})$$

$$(C_{ref}/V+) * (C_{pixel} + C_{ref}) = C_{pixel} * V_{DD}$$


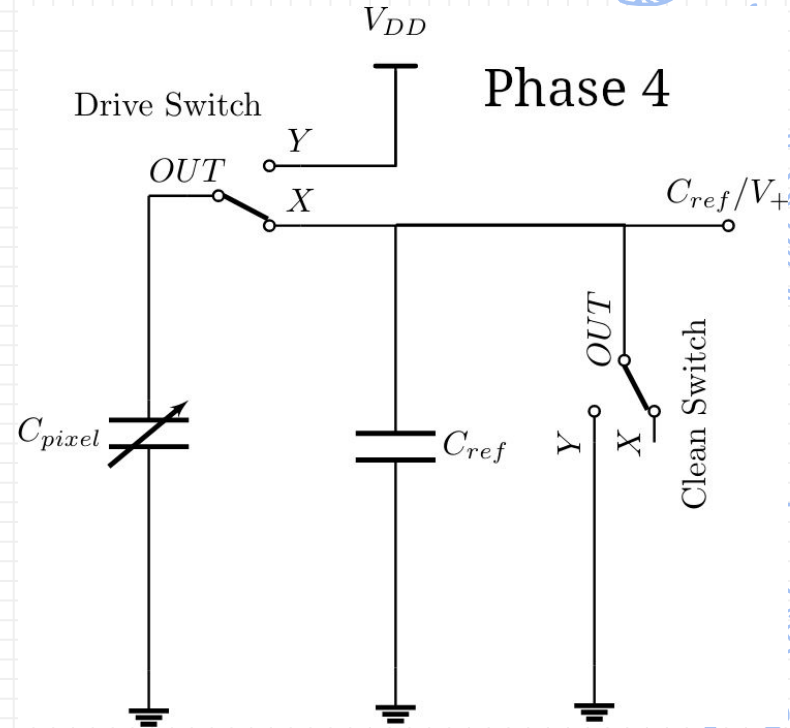
$$(C_{ref}/V+) = \frac{C_{pixel} * V_{DD}}{(C_{pixel} + C_{ref})}$$




Process Comparator

Voltage we are measuring: $(C_{ref}/V+) = \frac{C_{pixel} * V_{DD}}{(C_{pixel} + C_{ref})}$

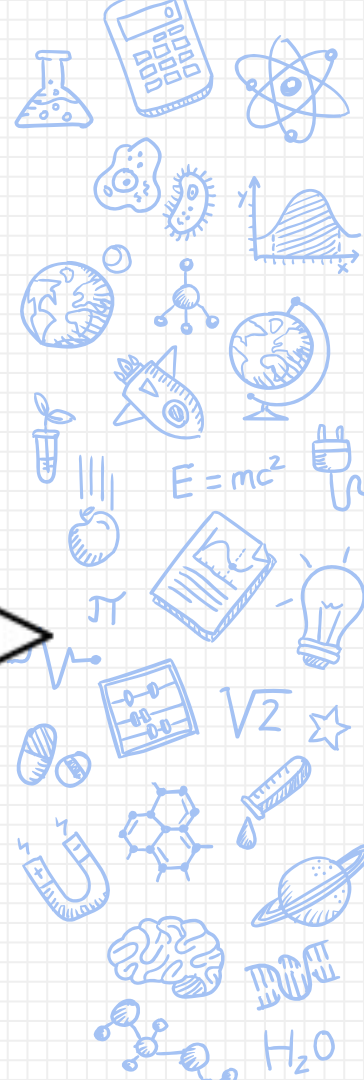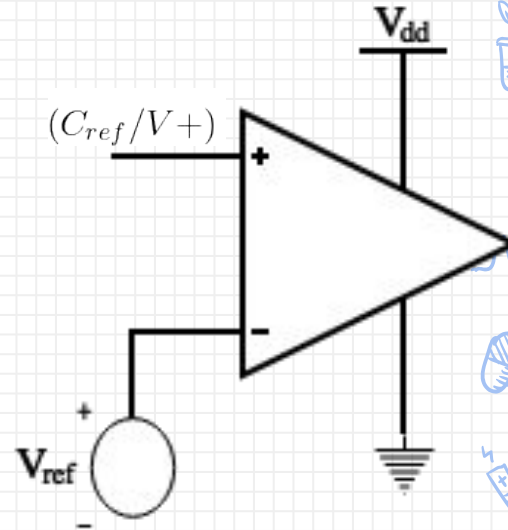- In touch and no-touch cases, the voltage at $C_{ref}/V+$ will be different
- Want to use the process comparator to distinguish between touch and no-touch voltages
- Desired comparator output:
 - **Touch:** V_{DD}
 - **No-touch:** $0V$



Full Circuit - Sense Process Actuate

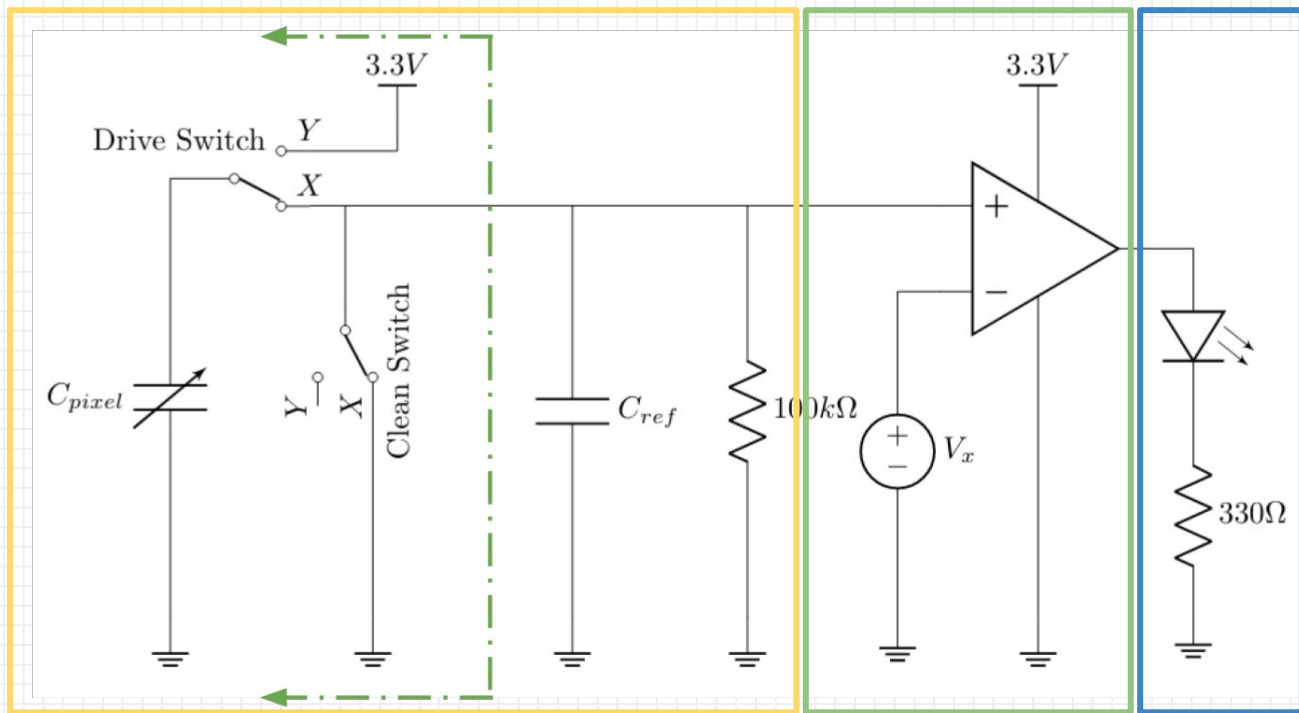

Notes

- ✗ **Unplug MSP before moving circuit components**
- ✗ Op Amp goes across middle of breadboard
- ✗ **Read op-amp pin diagram carefully**
- ✗ Make sure your circuit is grounded and has a common ground
- ✗ **Initial charge sharing diagrams are theoretical--don't start building right away**

