

EECS16ADIS7B


email: moses.wan@berkeley.edu

OH: 11:10 AM - 12 PM PST (HWP)

Learning Objectives

- ① Calculating power using passive sign convention
- ② Ideal voltmeter, ideal ammeter characteristics
- ③ If time (practice): units analysis and common units for circuits

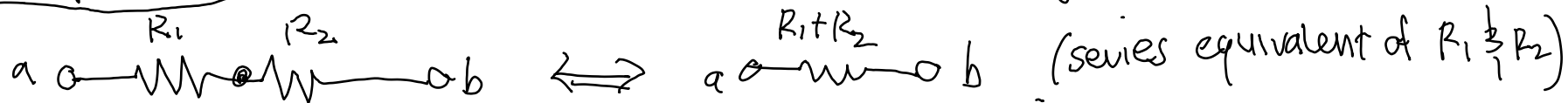Concept needed for HW (wasn't hit in lecture Tuesday)



two resistors connected
at one node, nothing
else on it

When we have this
"simplified" form/
equivalent, the middle node
disappears

// resistors
 R_1 and R_2
are in
series //

Playlist (bit.ly/16ajukebox)

① Glenn Gould Sonata No. 13 E^b
Op. 27 No. 1

② Bach - Little Fugue in Gm

③ Michiru Oshima - Waterlily


EECS 16A Designing Information Devices and Systems I

Fall 2020 Discussion 7B


power of an element $\{w\} = \left[\frac{J}{s} \right]$ joules (energy)
watts
 $P = VI$

1. Passive Sign Convention and Power

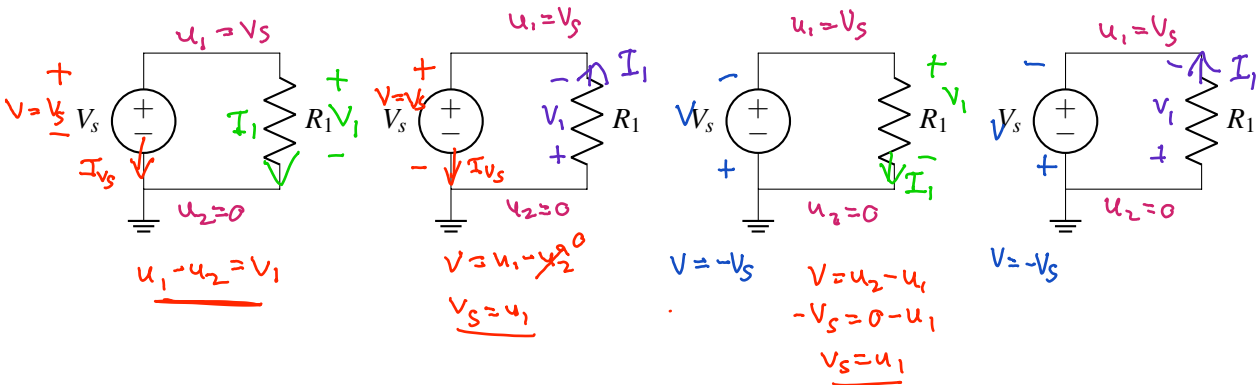- (a) We have made four copies of a circuit below. Following passive sign convention, there are four different possible labelings of current directions and voltage polarities for the circuit. For each copy, label each circuit's voltage source and resistor with current direction and voltage polarity labelings, keeping with passive sign convention.



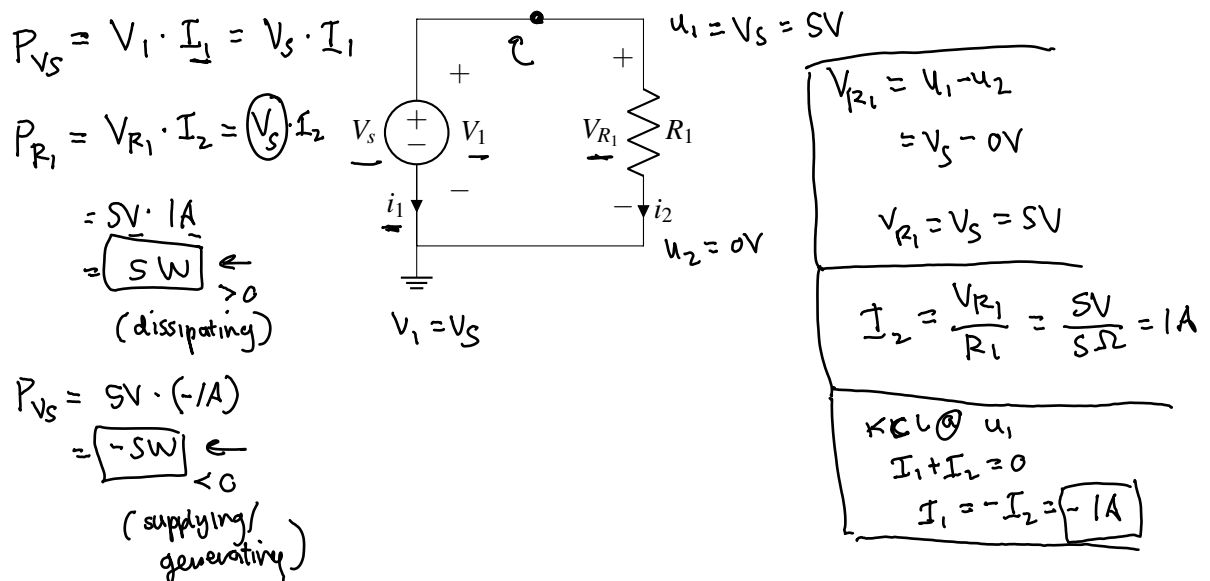- (b) Suppose we consider one of the possible labelings you have found above. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5\text{ V}$ and let $R_1 = 5\Omega$.



- (c) Suppose we choose a second labeling of the circuit as shown below. Calculate the power dissipated or supplied by every element in the circuit. Let $V_s = 5\text{ V}$ and let $R_1 = 5\ \Omega$.



$$\rightarrow V_1 = -V_s = \boxed{-5\text{ V}}$$

$$\begin{aligned} \rightarrow V_{R_1} &= u_1 - u_2 \\ &= V_s - 0\text{ V} \\ &= \boxed{5\text{ V}} \end{aligned}$$

$$I_2 = \frac{V_{R_1}}{R_1} = \frac{5\text{ V}}{5\ \Omega} = \boxed{1\text{ A}}$$

$$\text{KCL @ top} \quad \uparrow I_1 = I_2$$

$$\boxed{I_1 = 1\text{ A}}$$

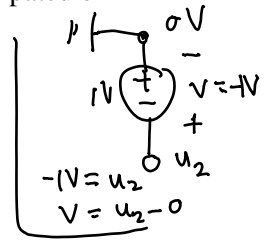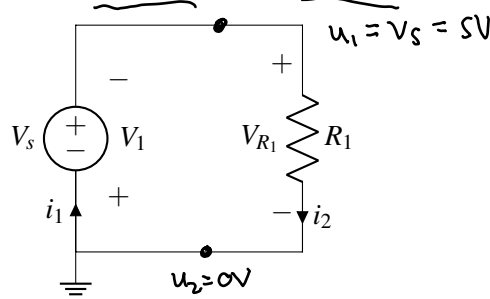

$$P_{V_s} = V_1 I_1 = (-5\text{ V})(1\text{ A}) = \boxed{-5\text{ W}}$$

$$P_{R_1} = V_{R_1} I_2 = 5\text{ V} \cdot 1\text{ A} = \boxed{5\text{ W}}$$

G: Ohm's law for sources?

A: Nope, can't use Ohm's law for voltage sources + current sources.

- (d) Did the values of the element voltages and element currents change with the different labeling? Did the power for each circuit element change? Did the node voltages change? If a quantity didn't change with a difference in labeling, discuss what would have to change for quantity to change.

$\left\{ \begin{array}{l} \rightarrow \text{If we follow PSC} \rightarrow \text{Power will be the same} \\ \rightarrow \text{Node voltages don't change, no matter the labeling} \end{array} \right\}$
 If we change labeling directions \rightarrow element current + element voltage will change value
 Power changes if we change the circuit
 Node voltages change if we change circuit
 \rightarrow moving ground change node voltage

Note: PSC \rightarrow for components that are passive (dissipating/absorbing energy) get positive power
 \rightarrow for components that are active (supplying/generating energy) power \rightarrow negative

2. Volt and ammeter

Consider the following circuit below. We have also included relevant NVA equations below it.

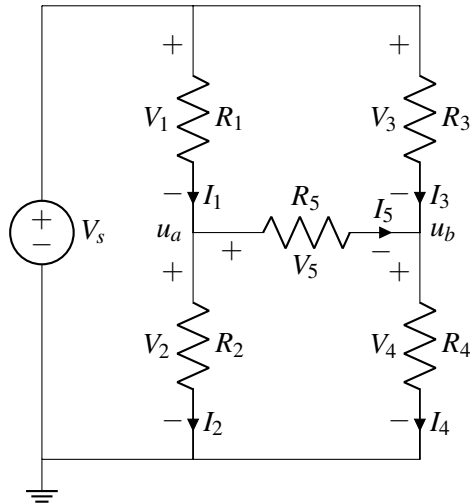


Figure 1: Circuit consisting of a voltage source V_s and five resistors R_1 to R_5 .

$$I_1 = I_2 + I_5$$

$$I_5 + I_3 = I_4$$

KCL

$$I_1 = \frac{V_1}{R_1} = \frac{V_s - u_a}{R_1}$$

$$I_2 = \frac{V_2}{R_2} = \frac{u_a - 0}{R_2}$$

$$I_3 = \frac{V_3}{R_3} = \frac{V_s - u_b}{R_3}$$

$$I_4 = \frac{V_4}{R_4} = \frac{u_b - 0}{R_4}$$

$$I_5 = \frac{V_5}{R_5} = \frac{u_a - u_b}{R_5}$$

Ohm's law in terms of node voltages

$$\frac{V_s - u_a}{R_1} = \frac{u_a - 0}{R_2} + \frac{u_a - u_b}{R_5}$$

$$\frac{u_a - u_b}{R_5} + \frac{V_s - u_b}{R_3} = \frac{u_b - 0}{R_4}$$

Substitute Ohm's into KCL

- (a) The circuit diagram shown in Figure 1 has been redrawn in Figure 2 by adding a voltmeter (letter V in a circle and plus and minus signs indicating direction) to measure voltage $V_{ab} = u_a - u_b$. Assume that the voltmeter is ideal. Are the values of V_{ab} before adding the voltmeter and after adding the voltmeter different? If so, which of the given equations change when doing NVA?



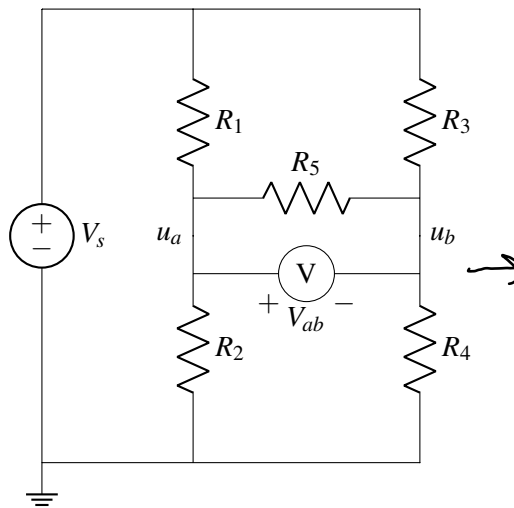


Figure 2: Circuit with voltmeter.

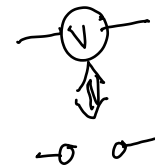
Ideal voltmeter:
behaves like an
open circuit



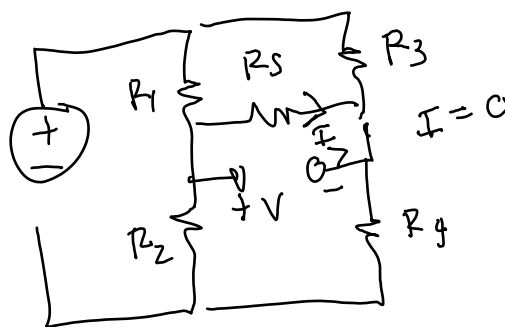No affect,
ckt stays
the same
in terms of
behavior



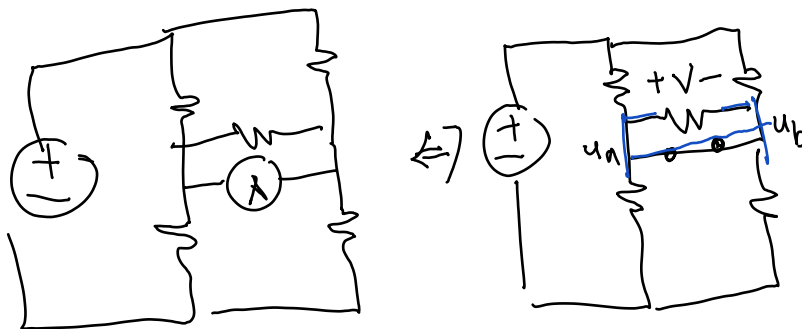- (b) Suppose you accidentally connect an ideal ammeter in part (a) to nodes u_a and u_b instead of an ideal voltmeter. Does the value of V_{ab} with the ammeter connected differ from the value of V_{ab} without the ammeter connected? If so, what equations change when doing NVA?



Q: What is the relationship
between u_a, u_b ?

$$A: u_a = u_b$$

$$V = u_a - u_b = 0V$$

$$I = \frac{V}{R} = \frac{0}{R} = 0A$$


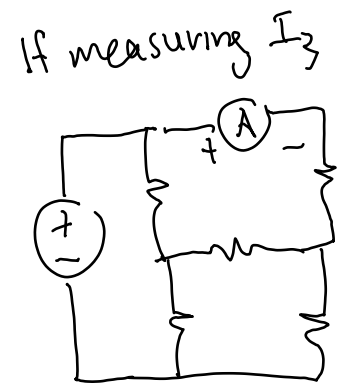
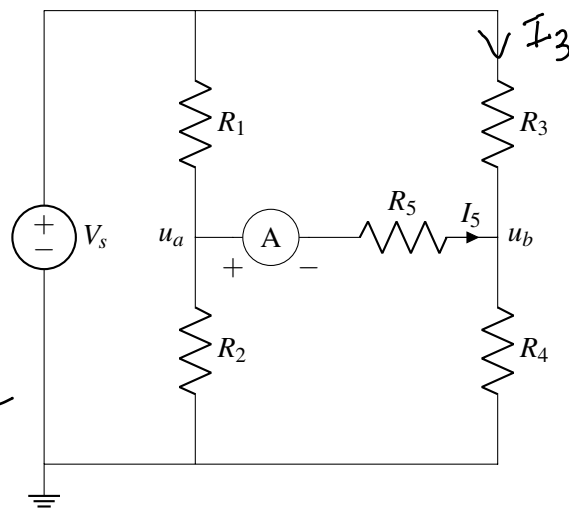




Figure 3: Circuit with ammeter.

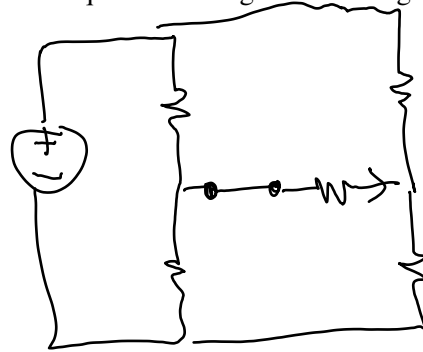- (c) The circuit diagram shown in Figure 1 has been redrawn in Figure 3 by adding an ideal ammeter (letter A in a circle and plus and minus signs indicating direction) in series with resistor R_5 . This will measure the current I_5 through R_5 . Are the values of I_5 before adding the ammeter and after adding the ammeter different? If so, what equations change when doing NVA?



Looks the same as first circuit
 \Rightarrow No change in behavior
 No change in equations

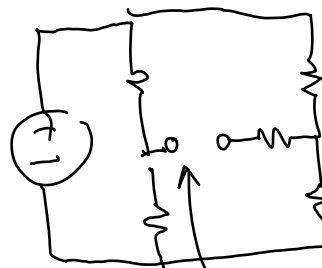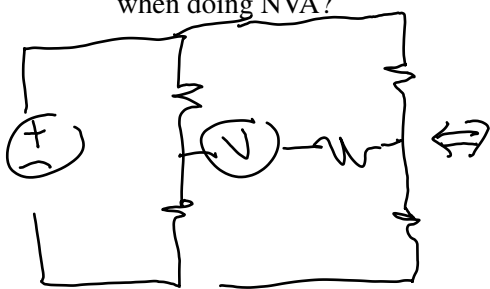- (d) Your friend accidentally connects a voltmeter in part (c) above, rather than an ammeter. Are the values of I_5 before adding the ammeter and after adding the ammeter different? If so, what equations change when doing NVA?



current that flowed before no longer can flow!

Behavior is different

review on how to calculate element voltage from node voltage

$$V = u_{\oplus} - u_{\ominus} = u_a - u_b$$

Key principle: attach voltmeters to same two nodes of voltage you want to measure
 attach ammeters along the same path through which current flows