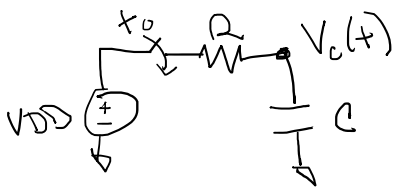


Last time on EE16B...

(Post lecture notes in purple)
(Imp equations boxed in green)

Developed a math model





$$\frac{d}{dt} V_c(t) + \frac{1}{RC} V_c(t) = \frac{V_{DD}}{RC}$$

Diff eq:


$$\frac{d}{dt} x(t) + ax(t) = b \Rightarrow x(t) = b/a + (x_0 - b/a)e^{-at}$$

Model a sq wave through an inv

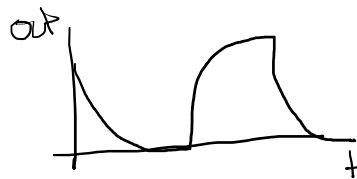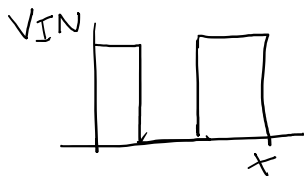

Time constant $\tau = RC$

$$V_c(t) = V_{DD} (1 - e^{-t/RC})$$

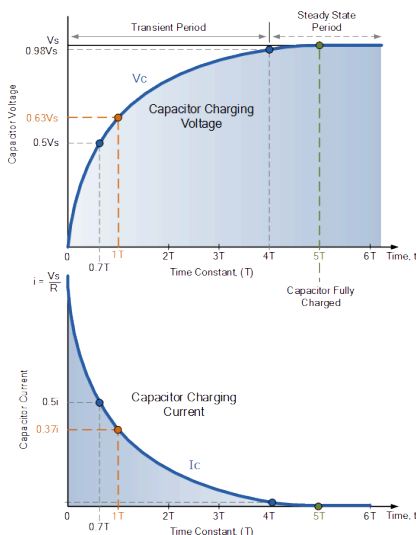

Time Constant	RC Value	Percentage of Maximum
		Voltage
0.5 time constant	$0.5T = 0.5RC$	39.3%
0.7 time constant	$0.7T = 0.7RC$	50.3%
1.0 time constant	$1T = 1RC$	63.2%
2.0 time constants	$2T = 2RC$	86.5%
3.0 time constants	$3T = 3RC$	95.0%
4.0 time constants	$4T = 4RC$	98.2%
5.0 time constants	$5T = 5RC$	99.3%

Looked at
real world applications
(ADCs)

Today -

I. Non-constant inputs to RC


A. Diff Eqn \Rightarrow Model

B. Check w/ constant

C. Exp Inputs

- i. $L \& C$ Impedance
- ii. Steady State
- iii. Euler's Function

Goal I

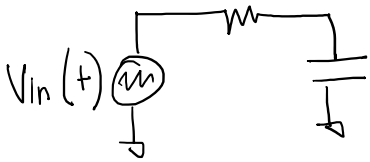

$V_{in}(t) = \text{any time varying function } f(t)$

Prev: $\frac{d}{dt} V_o(t) + \frac{1}{RC} V_o(t) = \frac{V_{in}}{RC}$

Now: $\dots \dots \dots = \frac{V_m(t)}{RC}$

* Math Break *

Goal A. Solve

$$\frac{d}{dt} x(t) + ax(t) = g(t)$$

Last Time

$$\text{soln } x(t) = (x_0 - b/a) e^{-at} + b/a$$

homogenous part
 $\Rightarrow x(t) = x_0 e^{-at}$

This time

$$x(t) = x_h(t) + x_p(t)$$


Several ways to solve eqn:

A) Piecewise Approx

Fall Note "Input"

A) Piecewise Approx

Fall Note "Input"
Pg 8

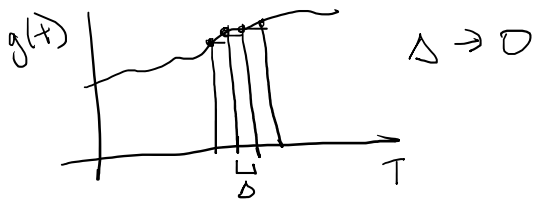

B) Integrating Factor

Consider product rule

$$\frac{d}{dt}(x(t)y(t)) = \frac{dy(t)}{dt}x(t) + \frac{dx(t)}{dt}y(t)$$

$$\left[\frac{d}{dt}x(t) \right] y(t) + \left[\frac{d}{dt}y(t) \right] x(t)$$

$$\frac{d}{dt}x(t)y(t) + a y(t)x(t) = g(t)y(t)$$

Choose $y(t)$ s.t. $\frac{d}{dt}y(t) = a y(t) \Rightarrow y(t) = e^{at}$

$$\underbrace{\frac{d}{dt}x(t)y(t) + \frac{d}{dt}y(t)x(t)}_{\text{product rule}} = g(t)y(t)$$

$$\int \frac{d}{dt}(x(t)y(t)) = \int g(t)y(t)$$

$$x(t)y(t) = \int_{t_0}^t g(\tau)y(\tau)d\tau + C$$

$$x(t)e^{at} = \int_{t_0}^t g(\tau)e^{a\tau}d\tau + C$$

Contains
✓ homogeneous part


$$x(t) = e^{-at} \int_{t_0}^t g(\tau)e^{a\tau}d\tau + Ce^{-at}$$

$$x(0) = x_0 = \int_0^0 g(\tau)e^{a\tau}d\tau + C$$

$$C = x_0$$

$$C = X_C$$

* Math Break Over

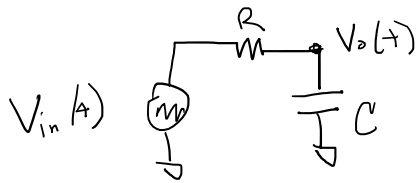

$V_{in}(t)$ see how an RC circuit affects

Circuit

$$\frac{d}{dt} V_o(t) + \frac{1}{RC} V_o(t) = \frac{V_{in}(t)}{RC}$$

$$V_o(t) = e^{-t/RC} \int_{t_0}^t \frac{V_{in}(\tau)}{RC} e^{\tau/RC} d\tau + V_o(t_0) e^{-t/RC}$$

$(\theta \rightarrow \tau \quad \cancel{K \rightarrow C})$

Soln RC circuit

general

$$\frac{d}{dt} x(t) + ax(t) = g(t)$$

$$x(t) = e^{-at} \int_{t_1}^t g(\tau) e^{a\tau} d\tau + X_0 e^{-at}$$

Subgoal B. Check using a const

$$V_{in}(t) = VDD$$

$$V_o(0) = 0$$

$$g(t) = \frac{VDD}{RC}$$

$$V_o(t) = e^{-t/RC} \int_{t_0}^t \frac{VDD}{RC} e^{\tau/RC} d\tau + V_o(t_0) e^{-t/RC}$$

$$= e^{-t/RC} \frac{VDD}{RC} \cdot RC [e^{t/RC} - e^{0/RC}] + 0 e^{-t/RC}$$

$$= VDD (e^{(t-t_0)/RC} - e^{(0-t_0)/RC})$$

$$V_o(t) = VDD - VDD e^{-t/RC}$$

Matches Yesterday!

Sin

$$V_{in}(t) = \sin(t) \quad V_o(0) = X_0$$

$$V_o(t) = e^{-t/RC} \underbrace{\int_{t_0}^t \frac{\sin(\theta)}{RC} e^{\theta/RC} d\theta}_{\text{hard integral}} + V_o(0) e^{-t/RC}$$

Subgoal C. Exp Inputs

Nice things about e^{st} (s is some const)

- eigenfunction

$$- e^{s\theta} \cdot e^{\theta/RC} = e^{\theta(s + \frac{1}{RC})} \text{ easy to intg}$$

- Emily's second favorite function

Try it

$$V_{in}(t) = \tilde{V} e^{st}, \quad \tilde{V} \text{ some const scalar}$$

$\neq V_o(t_0) = V_o(0)$ as initial condition

$$V_o(t) = e^{-t/RC} \int_0^t \frac{\tilde{V}}{RC} e^{\theta(s + \frac{1}{RC})} d\theta + V_o(0) e^{-t/RC}$$

$$= e^{-t/RC} \left[e^{t(s + \frac{1}{RC})} - e^0 \right] \frac{\tilde{V}}{RC} \frac{1}{s + \frac{1}{RC}} + V_o(0) e^{-t/RC}$$

$$V_o(t) = \frac{\tilde{V}}{sRC + 1} e^{st} + \left(V_o(0) - \frac{\tilde{V}}{sRC + 1} \right) e^{-t/RC}$$

$$\tilde{V} e^{st} \rightarrow \boxed{\frac{1}{s}} \rightarrow \lambda \tilde{V} e^{st}$$

True if we could get rid of $e^{-t/RC}$ term

Choose $V_o(0)$ s.t. $(V_o(0) - \frac{\tilde{V}}{sRC+1}) e^{-t/RC} = 0$


$$V_o(0) = \frac{\tilde{V}}{sRC+1}$$

$$V_o(t) = \frac{1}{sRC+1} \tilde{V} e^{st}$$

RC circuit for convenient initial condition


Subgoal: L & C why we care about exp inputs.

Voltage Divider

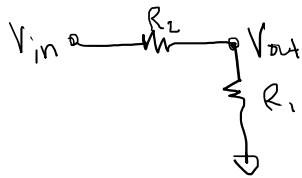

$$V_{out} = V_{in} \frac{R_1}{R_1 + R_2}$$

Eigen function property

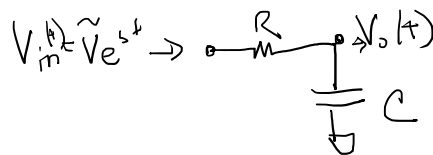


$$V_o(t) = \tilde{V} e^{st} \left(\frac{\frac{1}{sC}}{R + \frac{1}{sC}} \right)$$

e^{st} world

scalars/magnitudes

$$V = \tilde{V} e^{st} \quad I = \tilde{I} e^{st}$$

Capacitor

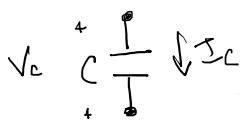

$$I_C = \frac{d}{dt} V_C \cdot C$$

$$\tilde{I} e^{st} = \frac{d}{dt} \tilde{V} e^{st} \cdot C$$


$$\tilde{I} e^{st} = s \tilde{V} e^{st} \cdot C$$

$$\frac{\tilde{V} e^{st}}{\tilde{I} e^{st}} = \frac{1}{sC}$$

$$\frac{\tilde{V}}{\tilde{I}} = \frac{1}{sC}$$



Aside

$$\frac{V}{I} = R$$

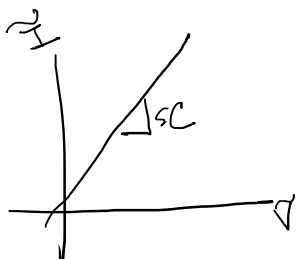

Inductor

Inductor

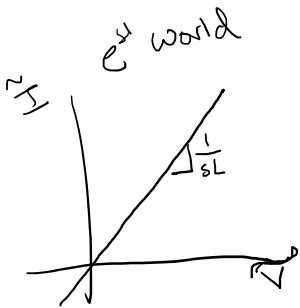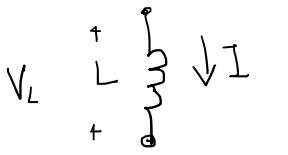

$$V_L = \tilde{V}_L e^{st} \quad I_L = \tilde{I}_L e^{st}$$


$$V_L = \frac{d}{dt} I_L \cdot L$$

$$\tilde{V}_L e^{st} = \frac{d}{dt} \tilde{I}_L e^{st} \cdot L$$

$$\tilde{V}_L e^{st} = s \tilde{I}_L e^{st} \cdot L$$

$$\frac{\tilde{V}_L e^{st}}{\tilde{I}_L e^{st}} = sL$$

Resistor

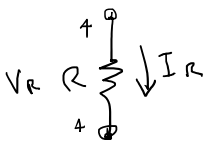


$$V_R = \tilde{V}_R e^{st} \quad I_R = \tilde{I}_R e^{st}$$

$$\tilde{V}_R e^{st} = \tilde{I}_R e^{st} R$$

$$\frac{\tilde{V}_R e^{st}}{\tilde{I}_R e^{st}} = R$$

magnitude divider

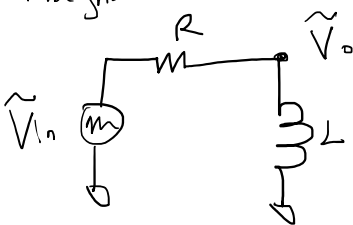

\tilde{V}_x - scalar / magnitude

$$V_x = \tilde{V}_x e^{st} \quad \text{final answer}$$

$$\tilde{V}_R = \tilde{I}_R R = \tilde{V}_{in} - \tilde{V}_o$$

$$\tilde{V}_L = \tilde{I}_L sL = \tilde{V}_o$$

$$\frac{\tilde{V}_{in} - \tilde{V}_o}{R} = \frac{\tilde{V}_o}{sL}$$

$$sL(\tilde{V}_{in} - \tilde{V}_o) = R\tilde{V}_o$$


$$sL\tilde{V}_{in} = sL\tilde{V}_o + R\tilde{V}_o$$

$$\tilde{V}_o = \tilde{V}_{in} \frac{sL}{sL + R}$$

$$\tilde{V}_0 e^{st} = \tilde{V}_{in} e^{st} \frac{sL}{sL+R}$$

$$\tilde{V}_0 = \tilde{V} e^{st} \frac{sL}{sL+R}$$

More complicated

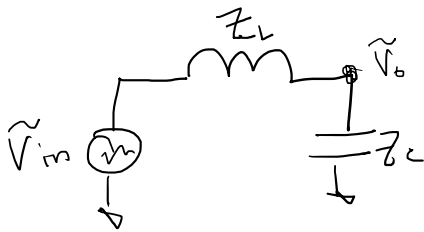

$$\tilde{V}_0 = \tilde{V}_{in} \frac{Z_C}{Z_C + Z_L}$$

$$= \tilde{V}_{in} \frac{\frac{1}{sC}}{\frac{1}{sC} + sL}$$

$$Z_L = sL$$


$$Z_C = \frac{1}{sC}$$

$$Z_R = R$$

Want to be in e^{st} world for L & C

Subsubgoal ii. Steady state

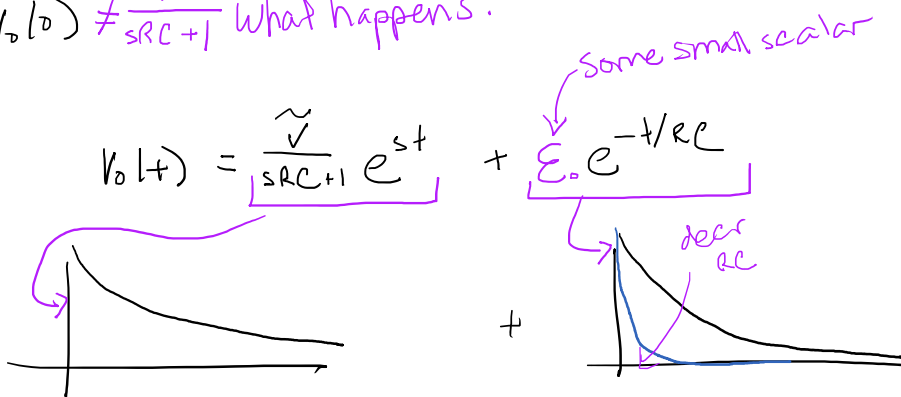$V_0(t) \neq \frac{\tilde{V}}{sRC+1}$ What happens?



choose RC time constant to decay quickly

Would be nice if we could

Choose some s s.t. e^{st} was periodic

$\rightarrow 1/R$ ← The size of the RC time constant doesn't matter if ϵ makes a big difference because a


Would be nice if we could...

Choose some s s.t. e^{st} was periodic



$$e^{-t/RC}$$

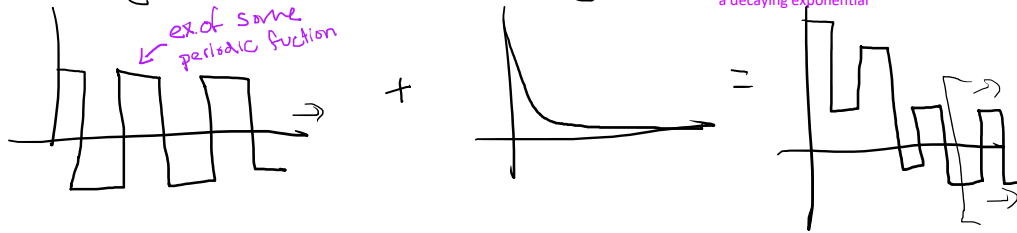The size of the RC time constant doesn't matter if s makes e^{st} periodic, because a periodic function will always outlast a decaying exponential



Steady state:

Wait till $e^{-t/RC}$ is negligible & K is effectively 0


Subsubgoal. iii

Euler's Formula

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$(j = i = \sqrt{-1})$$

Cartesian
& polar like

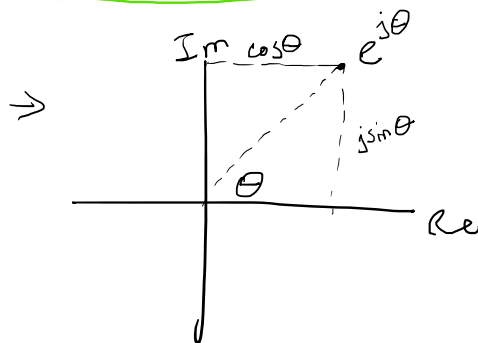

$$\cos \theta = \frac{1}{2} (e^{j\theta} + e^{-j\theta})$$

$$\sin \theta = \frac{1}{2j} (e^{j\theta} - e^{-j\theta})$$