



(Post lecture notes in purple)
(Imp't equations boxed in green)

Used Taylor expansion to prove Euler's Formula



$$e^{j\omega t} = \cos(\omega t) + j\sin(\omega t)$$

conjugate:

$$\overline{a + jb} = a - jb$$

Navigating the complex plane using Phasors

$$re^{j\phi}$$

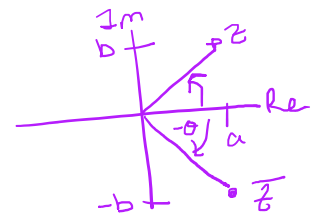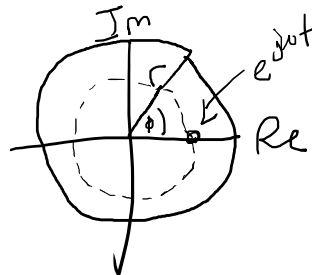

Useful for defining magnitude and phase of our input function $e^{j\omega t}$

$$V_{in}(t) = \underbrace{re^{j\phi}}_{\text{phasor}} \cdot e^{j\omega t}$$

angular freq

$$\omega = 2\pi f \text{ (rad/sec)}$$

Learned useful linear combinations of $e^{j\omega t}$


$$\begin{aligned} r\cos(\omega t + \phi) &= \frac{1}{2} \left(re^{j\phi} e^{j\omega t} + \overline{re^{j\phi} e^{j\omega t}} \right) \\ r\sin(\omega t + \phi) &= \frac{1}{2j} \left(re^{j\phi} e^{j\omega t} - \overline{re^{j\phi} e^{j\omega t}} \right) \end{aligned}$$

Work phasor domain

$$\tilde{V}_{in} \rightarrow \boxed{\text{circuit}} \rightarrow |H(j\omega)| e^{j\phi + j\omega t} \tilde{V}_{in}$$

$$\boxed{Z_R = R \quad Z_L = j\omega L \quad Z_C = \frac{1}{j\omega C}}$$

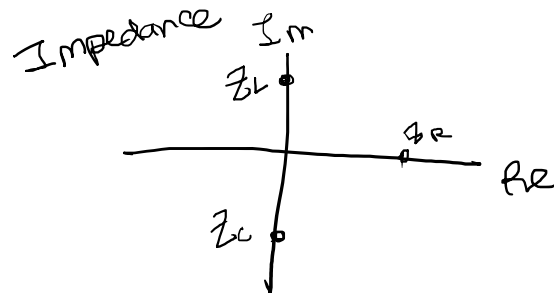Reactance and Resistance of Complex Impedance



Today:

0. Phasor Application Tangent

I. Transfer Function Example


II. Frequency Response

- a. RC circuit example
- b. Passive devices over frequency
 - i. Voltage divider reminder
 - ii. Low Pass Filter
 - iii. High Pass Filter
 - iv. Active Filter



III. Bode Plots

- a. Design and plot a filter
- b. Bode plot rules
- c. Application tangent: Headphone Freq Resp



0. Phasor Application Tangent

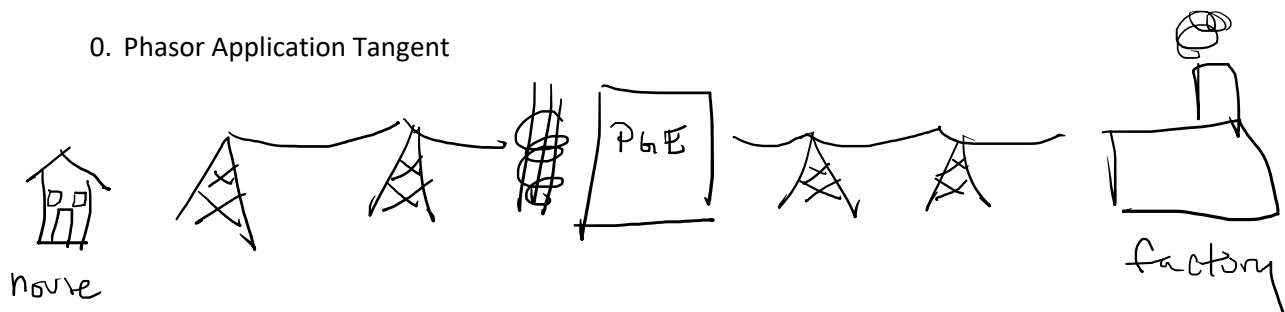

Power to house

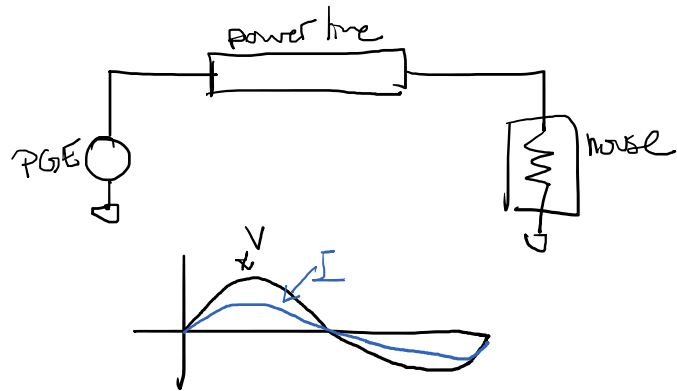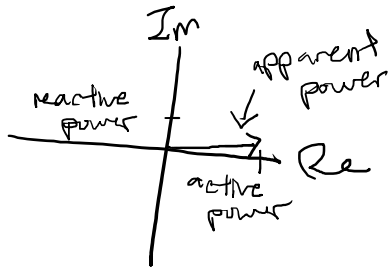


Power to Factory

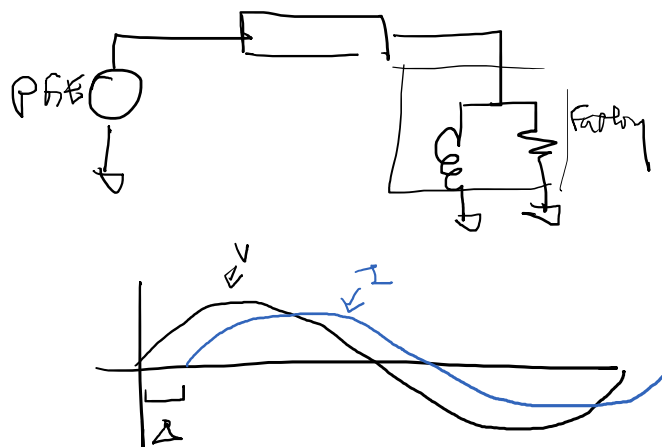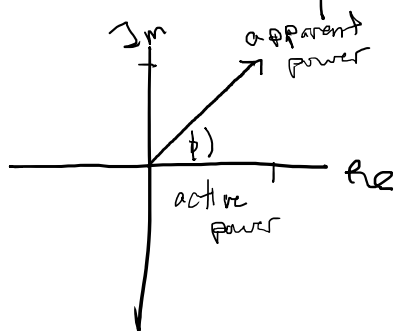


I. Transfer Function Examples

Solve for $H(j\omega)$

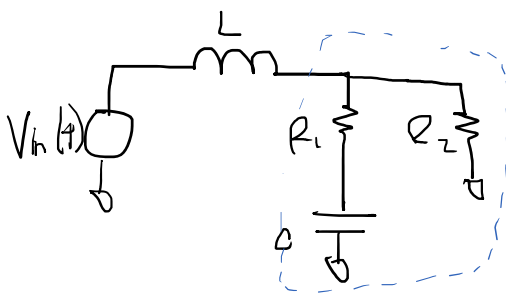

phasor domain

\Rightarrow

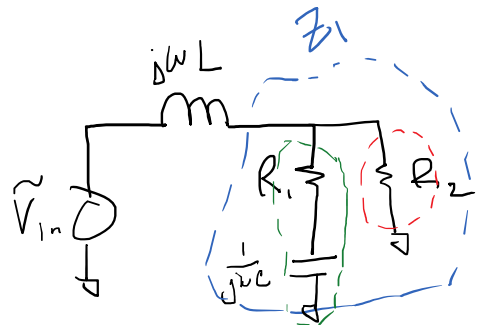


Parallel/ Series Imp Combination
Thevenin and Norton
KVL/KCL
Voltage Divider

$$Z_1 = \left(R_1 + \frac{1}{j\omega C} \right) \parallel R_2$$

$$Z_1 = (R_1 + \frac{1}{j\omega C}) \parallel R_2$$
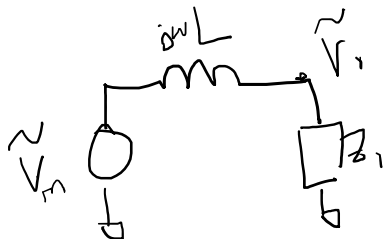
$$= \frac{(R_1 + \frac{1}{j\omega C}) R_2}{(R_1 + \frac{1}{j\omega C}) + R_2}$$



$$\tilde{V}_o = \tilde{V}_in \frac{Z_1}{Z_1 + j\omega L}$$

$$H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_in} = \frac{Z_1}{Z_1 + j\omega L}$$

$$H(j\omega) = |H(j\omega)| e^{j\angle H(j\omega)}$$


Given ω, R_1, R_2, C, L

$$|H(j\omega)| = \text{numpy.absolute}(H(j\omega))$$

$$\angle H(j\omega) = \text{numpy.angle}(H(j\omega))$$

II. Frequency Response

a. RC Circuit Example

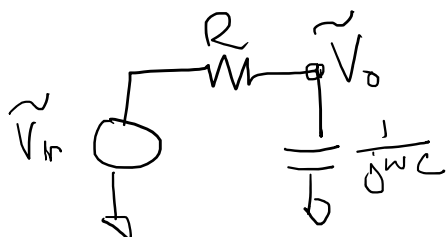


$$H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_in} = \frac{1}{1 + j\omega RC}$$

$$\tilde{V}_o = \tilde{V}_in H(j\omega)$$

Input 1:

$$V_{in} = 1 e^{j\omega t}$$

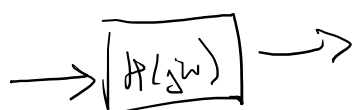

$$\frac{1}{1 + j\omega RC} \cdot 1 \cdot e^{j\omega t}$$

↑
input
pressure

Input 2:

$$V_{in} = \underbrace{\tilde{V} \cos(\omega_1 t)}_{\frac{1}{2}(\tilde{V}e^{j\omega_1 t} + \tilde{V}e^{-j\omega_1 t})} \rightarrow \boxed{H(j\omega)} \rightarrow \frac{1}{2} \left(\frac{1}{1+j\omega_1 RC} \tilde{V} e^{j\omega_1 t} + \frac{1}{1-j\omega_1 RC} \tilde{V} e^{-j\omega_1 t} \right)$$

Input 3

$$V_{in} = \tilde{V} (e^{j\omega_1 t} + e^{j\omega_2 t} + \dots) \rightarrow \boxed{H(j\omega)} \rightarrow \tilde{V} \left(\frac{1}{1+j\omega_1 RC} e^{j\omega_1 t} + \frac{1}{1+j\omega_2 RC} e^{j\omega_2 t} \right)$$

$H(j\omega)$ is freq dependent

\mathcal{L}_x


$$R = 100 \quad C = 1 \times 10^{-6} \quad \omega_1 = 1 \quad \omega_2 = 1 \times 10^9$$

$$H(j\omega_1) = \frac{1}{1 + j(100)(1 \times 10^{-6})} = \frac{1}{1 + j1 \times 10^{-4}} \approx 1$$

$$H(j\omega_2) = \frac{1}{j1 \times 10^5}$$

$$\approx \frac{1}{j1 \times 10^5} \approx \frac{1}{j} 0 = -j0$$
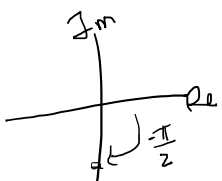
$$V_o(t) = \underbrace{\tilde{V} H(j\omega_1)}_{\sim 1} e^{j\omega_1 t} + \underbrace{\tilde{V} H(j\omega_2)}_{\sim -j0} e^{j\omega_2 t}$$




$$|H(j\omega)| = 1$$

$$\angle H(j\omega) = 0$$

$$|H(j\omega)| = 0$$

$$\angle H(j\omega) = -\frac{\pi}{2}$$

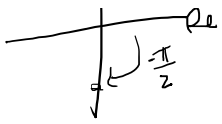

$$\angle H(j\omega) = 0$$

small ω


$$\angle H(j\omega) = -\frac{\pi}{2}$$

Large ω

Low Pass Filter

b. Passive devices over frequency


Resistor

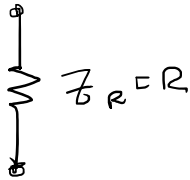

$$Z_R @ (\omega = 0) = R$$

$$Z_R @ (\omega = \infty) = R$$


Capacitor

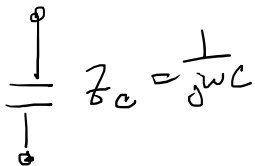

$$Z_C @ (\omega = 0) = \frac{1}{j \cdot 0 \cdot C} = -j\infty \text{ (open)}$$

$$Z_C @ (\omega = \infty) = \frac{1}{j \cdot \infty \cdot C} = -j0 \text{ (short)}$$


Inductor

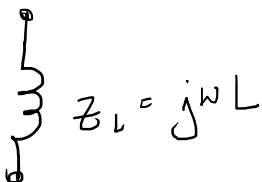

$$Z_L @ (\omega = 0) = j \cdot 0 \cdot L = j0 \text{ (short)}$$

$$Z_L @ (\omega = \infty) = j \cdot \infty \cdot L = j\infty \text{ (open)}$$

i. Voltage divider reminder

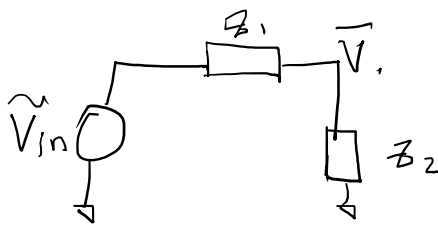


$$\frac{\tilde{V}_{Z_1}}{\tilde{V}_{Z_2}} = \frac{Z_1}{Z_2}$$

\tilde{V}_o large for $Z_2 \gg Z_1$

\tilde{V}_o small for $Z_2 \ll Z_1$

ii. Low Pass Filter

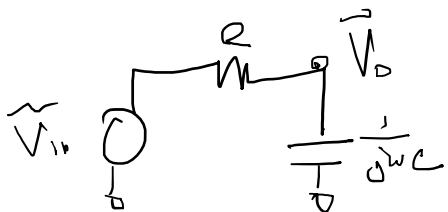


\tilde{V}_o large $\frac{1}{j\omega C} \gg R \leftarrow$ small freq

\tilde{V}_o small $\frac{1}{j\omega C} \ll R \leftarrow$ large freq


Low Pass Filter

iii. High Pass Filter

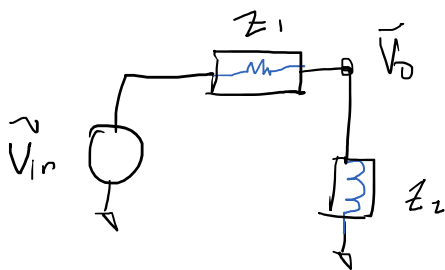

$Z_1 \gg Z_2$ small freq


$Z_1 \ll Z_2$ large freq

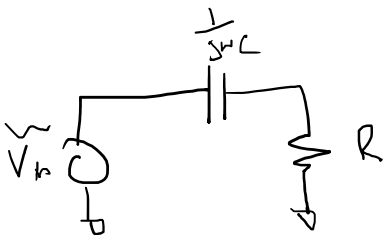

$$\tilde{V}_o = \tilde{V}_in \frac{R}{R + \frac{1}{j\omega C}} \Rightarrow H(j\omega) = \frac{j\omega CR}{1 + j\omega CR}$$

small $\omega \rightarrow 0j$
large $\omega \rightarrow 1$

iv. Active Filter

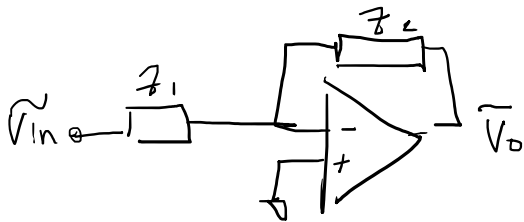

$$A_v = \frac{\tilde{V}_o}{\tilde{V}_{in}} = -\frac{Z_2}{Z_1}$$

$$Z_2 = j\omega L$$

$$Z_1 = R$$

$$Z_2 \gg Z_1$$

large freq

$$Z_2 \ll Z_1$$

small freq

Active High Pass Filter

III. Bode Plots



a. Design and plot a filter

Filter out freq. above human hearing

Low Pass Filter

$$20\text{Hz} - 20\text{kHz} : H(j\omega) \approx 1$$
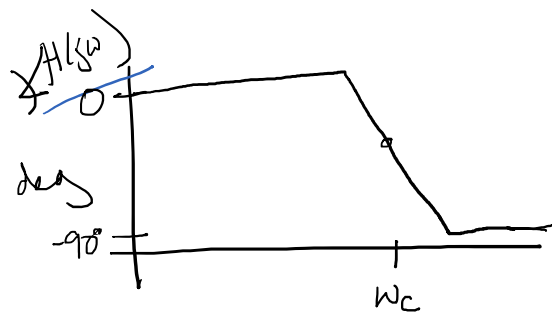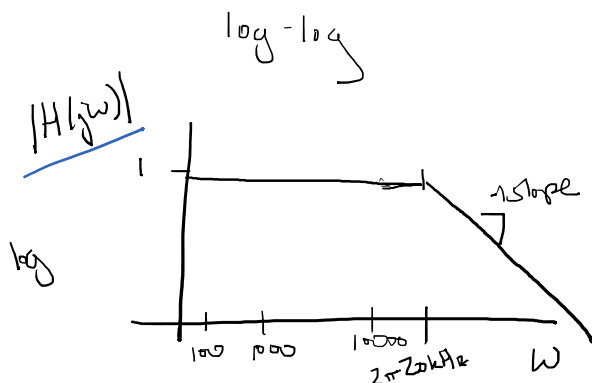
$$> 20\text{kHz} : H(j\omega) \rightarrow -j^0$$



log \rightarrow cutoff freq (ω_c)

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|j\omega RC| = 1$$

$$\omega_c = 2\pi \cdot 20 \text{ kHz}$$



$$\omega_c = \frac{1}{RC} \leftarrow \begin{array}{l} \text{cutoff freq} \\ \text{corner} \\ \text{pole} \end{array}$$

High Pass Filter

$$H(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

\leftarrow grows w/ ω

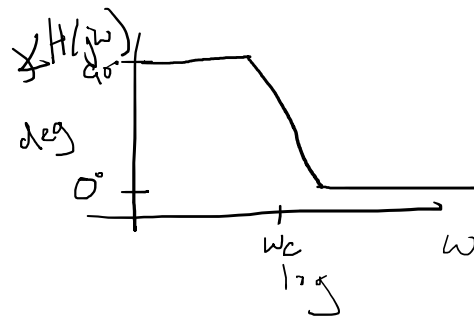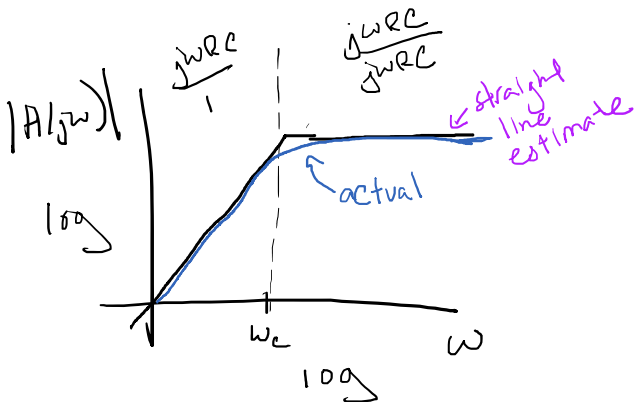
\leftarrow 1 dominates until $\omega = 1/RC$



b. Bode Plot Rules

$$H(j\omega) = \frac{(j\omega)^n (1 + j\omega/\omega_{z1}) (1 + j\omega/\omega_{z2}) \dots \leftarrow \text{zeros} \quad \omega = \omega_{z1}, \omega_{z2}, \dots}{(j\omega)^m (1 + j\omega/\omega_{p1}) (1 + j\omega/\omega_{p2}) \dots \leftarrow \text{poles} \quad \omega = \omega_{p1}, \omega_{p2}, \dots}$$

Factored transfer function

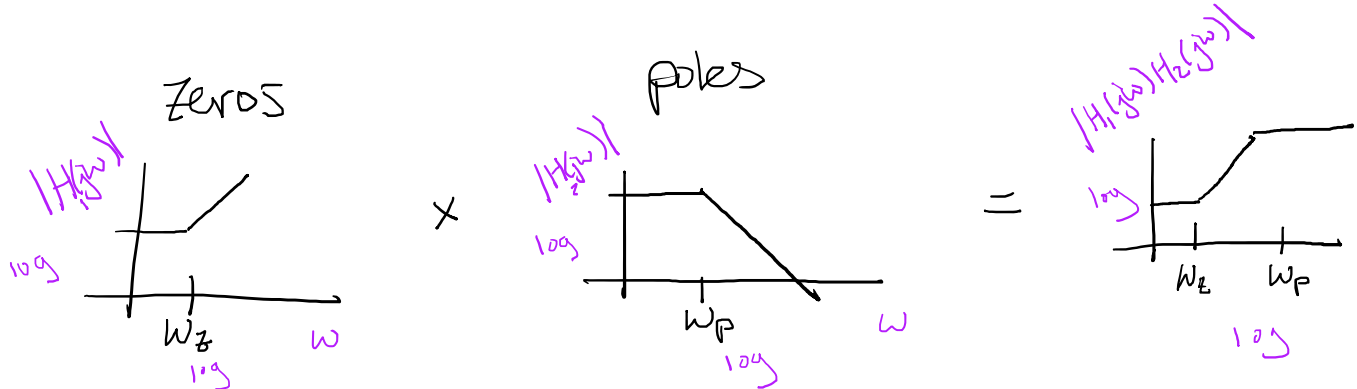

GO TO DISCUSSION FOR MORE BODE PLOT PRACTICE

Factor	Bode Magnitude	Bode Phase
Constant K	$20 \log K$ 0 dB	$\pm 180^\circ$ if $K < 0$ 0° if $K > 0$
Zero @ Origin $(j\omega)^N$	0 dB slope = $20N$ dB/decade	$(90N)^\circ$ 0°
Pole @ Origin $(j\omega)^{-N}$	0 dB slope = $-20N$ dB/decade	0° $(-90N)^\circ$
Simple Zero $(1 + j\omega/\omega_c)^N$	0 dB slope = $20N$ dB/decade	0° $(90N)^\circ$
Simple Pole $\left(\frac{1}{1 + j\omega/\omega_c}\right)^N$	0 dB slope = $-20N$ dB/decade	0° $(-90N)^\circ$
Quadratic Zero $[1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2]^N$	0 dB slope = $40N$ dB/decade	0° $(180N)^\circ$
Quadratic Pole $\frac{1}{[1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2]^N}$	0 dB slope = $-40N$ dB/decade	0° $(-180N)^\circ$