

---

# EECS 16A    Designing Information Devices and Systems I

## Summer 2020    Homework 3A

---

**This homework is due Wednesday, July 15, 2020, at 23:59.**

**Self-grades are due Sunday, July 19, 2020, at 23:59.**

### Submission Format


Your homework submission should consist of a single PDF file that contains all of your answers (any handwritten answers should be scanned).

**Homework Learning Goals:** *The objective of this homework is to introduce Node Voltage Analysis in the context of voltage divider circuits and circuits with more than one independent sources.*

### 1. Voltage divider

In the following parts,  $V_s = 12\text{ V}$ . Choose resistance values such that the current through each element is  $\leq 0.8\text{ A}$ .

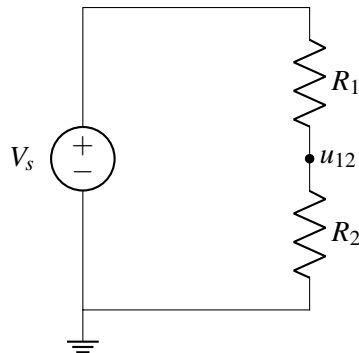
- (a) Select values for  $R_1$  and  $R_2$  in the circuit below such that  $u_{12} = 6\text{ V}$ .




**Solution:** Step 1: Reference Node

We notice that the ground node has already been selected for us in the question.

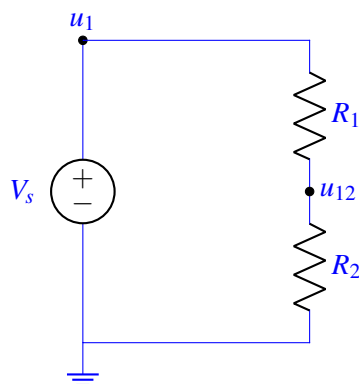Step 2: Label nodes with voltage set by sources



Step 3: Label other nodes

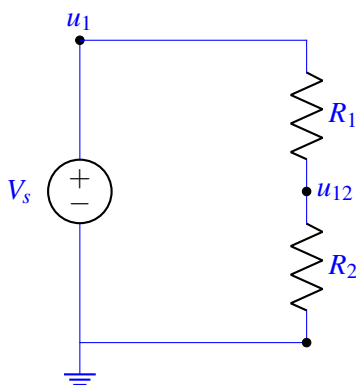

Step 4: Label element voltages and currents.

Let  $V_{R1}$ ,  $V_{R2}$  be the voltage drop across  $R_1$  and  $R_2$  respectively. Let  $I_1$  be the current between the voltage source and  $R_1$ . Let  $I_2$  be the current from  $R_2$  to the voltage source.

Step 5: KCL Equations

From KCL, at  $u_{12}$ ,

$$I_1 = I_2.$$

Step 6: Find element currents

Using Ohm's law, we have that

$$I_1 = \frac{V_{R1}}{R_1}$$

$$I_2 = \frac{V_{R2}}{R_2}$$

Writing the element voltages in terms of the node voltages, we have that  $V_{R1} = V_s - u_{12}$  and  $V_{R2} = u_{12}$ .

Step 7: Substitute element currents into KCL Equations

Substituting back, we obtain  $\frac{V_s - u_{12}}{R_1} = \frac{u_{12}}{R_2}$ . Solving, we find that  $u_{12} = \frac{R_2}{R_1 + R_2} V_s$ . Plugging in  $u_{12} = 6V$  and  $V_s = 12V$ , we see that  $R_1 = R_2$  must be true.

To choose  $R_1$  and  $R_2$  such that the current through each element is  $\leq 1A$ , use KVL to write an expression for  $I_1, I_2$  as a function of  $R_1, R_2$ :

$$V_s - I_1 R_1 - I_2 R_2 = 0, \text{ with } I_1 = I_2 = I_s$$


$$V_s = I_s (R_1 + R_2)$$

$$12V = 0.8A (R_1 + R_2)$$

$$R_1 + R_2 = 15\Omega$$

As  $R_1 + R_2$  must be at least  $15\Omega$ , and  $R_1 = R_2$ , we choose  $R_1 = R_2 = 7.5\Omega$ .

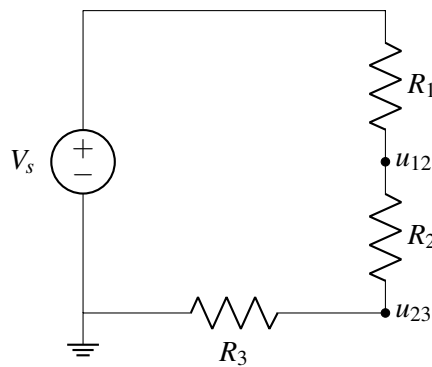(b) Select values for  $R_1, R_2, R_3$  in the circuit below such that  $u_{12} = 6V$  and  $u_{23} = 2V$ .




**Solution:** Let  $V_{R1}, V_{R2}, V_{R3}$  be the voltage drop across  $R_1, R_2, R_3$  respectively. From KCL, we know that the current flowing through each of the elements is the same. Using Ohm's law, this can be rewritten as  $\frac{V_{R1}}{R_1} = \frac{V_{R2}}{R_2} = \frac{V_{R3}}{R_3}$ . Writing the element voltages in terms of the node voltages, we have that  $V_{R1} = V_s - u_{12}$  and  $V_{R2} = u_{12} - u_{23}$  and  $V_{R3} = u_{23}$ . Solving, similarly to the previous subpart, we find that  $u_{12} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} V_s$  and  $u_{23} = \frac{R_3}{R_1 + R_2 + R_3} V_s$ . We found in the previous subpart that the total resistance in our KVL loop must be at least  $15\Omega$  to limit the current to  $\leq 0.8A$ , meaning for this circuit that  $R_1 + R_2 + R_3 \geq 15\Omega$ . Choosing  $R_1 = 7.5\Omega, R_2 = 5\Omega, R_3 = 2.5\Omega$  would give us the desired voltage, and limit the current to  $\leq 0.8A$ , though scaling the resistor values up by the same multiplicative constant would also be a valid solution.

## 2. Circuit Analysis

Using the steps outlined in lecture, analyze the following circuits to calculate the currents through each branch and the voltages at each node. Use the ground node labelled for you. You may use a numerical tool, such as IPython.

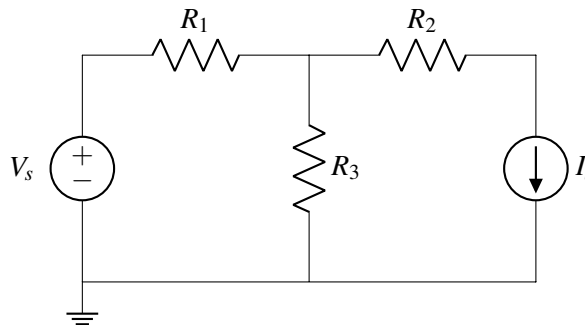
(a)  $V_s = 5V, I_s = 2A, R_1 = R_2 = 2\Omega, R_3 = 4\Omega$



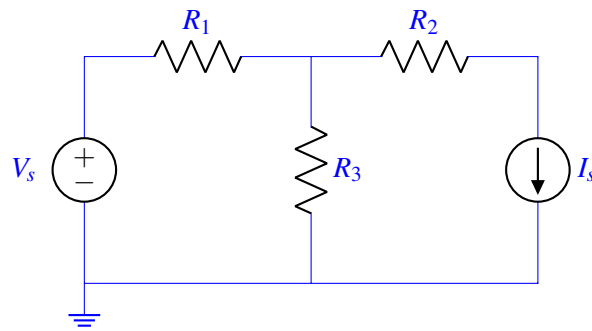**Solution:**


Step 1) Reference node

Select a reference (ground) node. Any node can be chosen for this purpose. In this example, we choose the node at the bottom of the circuit diagram.



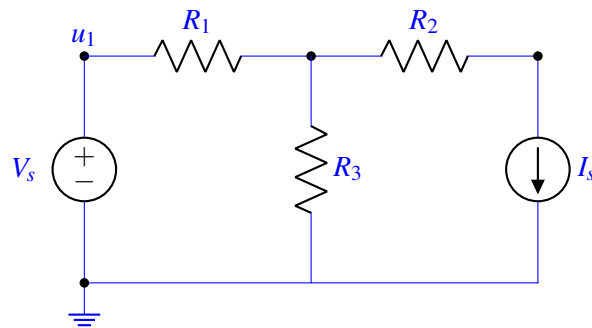
### Step 2) Label Nodes with Voltage set by Sources

Voltage sources set the voltage of the node they are connected to. In the example, there is only one source,  $V_s$ , and we label the corresponding source  $u_1$  (names are arbitrary, but must be unique).


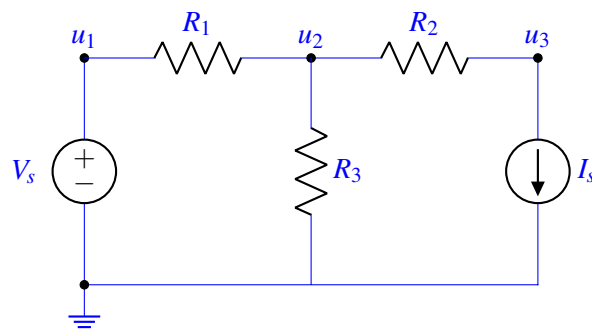
### Step 3) Label Remaining Nodes


Now we label all remaining nodes in the circuit except the reference. In the example there are two,  $u_2$  and  $u_3$ .


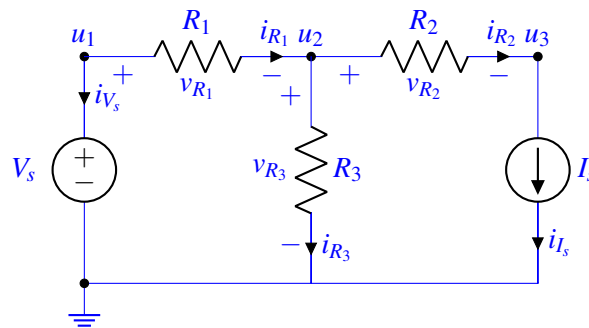
### Step 4) Label Element Voltages and Currents

Next we mark all element voltages and currents.

Start with the current. The direction is arbitrary (top to bottom, bottom to top, it won't matter, but stick with your choice in subsequent steps). Then mark the element voltages following the passive sign convention, i.e. the voltage and current point in the "same" direction.



### Step 5) KCL Equations

Write KCL equations for all nodes with unknown voltage,  $u_2$  and  $u_3$ .

$$\begin{aligned} -i_{R_1} + i_{R_2} + i_{R_3} &= 0 \\ -i_{R_2} + i_{I_s} &= 0 \end{aligned}$$

### Step 6) Element Currents

Find expressions for all element currents in terms of voltage and element characteristics (e.g. Ohm's law) for all circuit elements except voltage sources. In this circuit there are four,  $R_1$ ,  $R_2$ ,  $R_3$  and  $I_s$ .

$$\begin{aligned} i_{I_s} &= I_s \\ i_{R_1} &= \frac{V_{R_1}}{R_1} \\ i_{R_2} &= \frac{V_{R_2}}{R_2} \\ i_{R_3} &= \frac{V_{R_3}}{R_3} \end{aligned}$$

We also have

$$\begin{aligned} u_1 &= V_s \\ i_{I_s} &= I_s \\ i_{R_1} &= \frac{u_1 - u_2}{R_1} \\ i_{R_2} &= \frac{u_2 - u_3}{R_2} \\ i_{R_3} &= \frac{u_2}{R_3} \end{aligned}$$

### Step 7) Substitute Element Currents in KCL Equations

Now we substitute the expressions derived in Step 6 into the KCL equations from Step 5.

$$\begin{aligned}
 -\frac{V_s - u_2}{R_1} + \frac{u_2 - u_3}{R_2} + \frac{u_2}{R_3} &= 0 \\
 -\frac{u_2 - u_3}{R_2} + I_s &= 0
 \end{aligned}$$

Let's make this a bit nicer by grouping the unknowns ( $u_2$  and  $u_3$ ) on the left side and the known terms on the right:

$$\begin{aligned}
 u_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + u_3 \left( -\frac{1}{R_2} \right) &= \frac{V_s}{R_1} \\
 u_2 \left( -\frac{1}{R_2} \right) + u_3 \left( \frac{1}{R_2} \right) &= -I_s
 \end{aligned}$$

Note that we now have 2 equations for 2 unknowns. Thus, we set up the following matrix relation:

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} u_2 \\ u_3 \end{bmatrix} = \begin{bmatrix} \frac{V_s}{R_1} \\ -I_s \end{bmatrix}$$


Finally, we plug in the values we were given into the matrix above and use Gaussian elimination to find the vector of unknowns. We find that:

$$\begin{bmatrix} u_2 \\ u_3 \end{bmatrix} = \begin{bmatrix} 0.667V \\ -3.33V \end{bmatrix}$$


The branch currents can be obtained from the node voltages and element equations. Therefore, we can write:

$$\begin{aligned}
 i_{V_s} &= -2.167A \\
 i_{I_s} &= I_s = 2A \\
 i_{R_1} &= \frac{u_1 - u_2}{R_1} = 2.167A \\
 i_{R_2} &= \frac{u_2 - u_3}{R_2} = 2A \\
 i_{R_3} &= \frac{u_2}{R_3} = 0.167A
 \end{aligned}$$

(b)  $V_s = 5V, R_1 = 1\Omega, R_2 = 2\Omega, R_3 = 3\Omega, R_4 = 4\Omega, R_5 = 5\Omega$

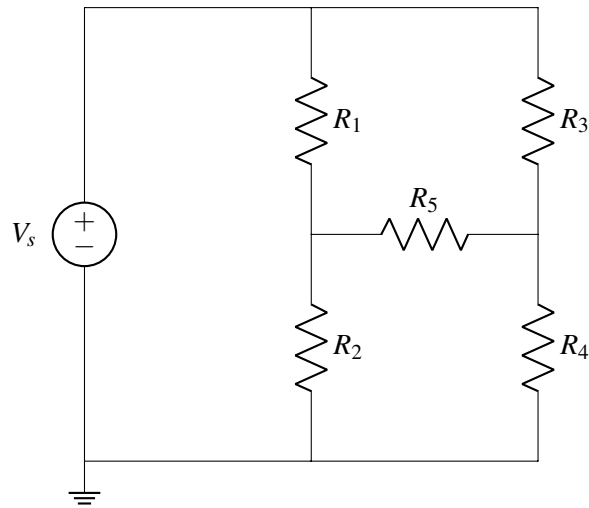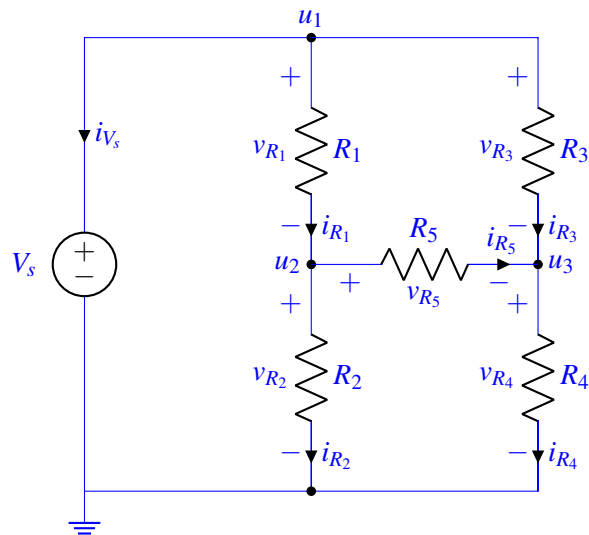**Solution:**

Here, we will skip showing all of the individual steps. Below is the circuit with our choice of ground and current directions.



From the above circuit, we get the following KCL equations:

$$-i_{R_1} + i_{R_2} + i_{R_5} = 0$$

$$-i_{R_3} + i_{R_4} - i_{R_5} = 0$$

Using the  $IV$  relations for each element, we have:

$$\begin{aligned}u_1 - 0 &= V_s \\i_{R_1} &= \frac{u_1 - u_2}{R_1} \\i_{R_2} &= \frac{u_2 - 0}{R_2} \\i_{R_3} &= \frac{u_1 - u_3}{R_3} \\i_{R_4} &= \frac{u_3}{R_4} \\i_{R_5} &= \frac{u_2 - u_3}{R_5}\end{aligned}$$

We also know that  $u_1 = V_s$

Now we substitute these expressions into the KCL equations we previously derived.

$$\begin{aligned}-\frac{V_s - u_2}{R_1} + \frac{u_2 - 0}{R_2} + \frac{u_2 - u_3}{R_5} &= 0 \\-\frac{V_s - u_3}{R_3} + \frac{u_3}{R_4} - \frac{u_2 - u_3}{R_5} &= 0\end{aligned}$$

Let's make this a bit nicer by grouping the unknowns ( $u_2$  and  $u_3$ ) on the left side and the known terms on the right:

$$\begin{aligned}u_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} \right) + u_3 \left( -\frac{1}{R_5} \right) &= \frac{V_s}{R_1} \\u_2 \left( -\frac{1}{R_5} \right) + u_3 \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) &= \frac{V_s}{R_3}\end{aligned}$$

Note that we now have 2 equations for 2 unknowns. Thus, we set up the following matrix relation:

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} & -\frac{1}{R_5} \\ -\frac{1}{R_5} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} u_2 \\ u_3 \end{bmatrix} = \begin{bmatrix} \frac{V_s}{R_1} \\ \frac{V_s}{R_3} \end{bmatrix}$$

Finally, we plug in the values we were given into the matrix above and use Gaussian elimination to find the vector of unknowns.

$$\begin{bmatrix} u_2 \\ u_3 \end{bmatrix} = \begin{bmatrix} 3.29V \\ 2.968V \end{bmatrix}$$

The branch currents can be obtained from the node voltages and element equations. Therefore, we can write:



$$i_{R_1} = \frac{u_1 - u_2}{R_1} = 1.709A$$

$$i_{R_2} = \frac{u_2 - 0}{R_2} = 1.645A$$

$$i_{R_3} = \frac{u_1 - u_3}{R_3} = 0.677A$$

$$i_{R_4} = \frac{u_3}{R_4} = 0.741A$$

$$i_{R_5} = \frac{u_2 - u_3}{R_5} = 0.0644A$$

$$i_{V_s} = i_{R_1} + i_{R_3} = -2.38A$$

### 3. Homework Process and Study Group

Who else did you work with on this homework? List names and student ID's. (In case of homework party, you can also just describe the group.) How did you work on this homework?

**Solution:**

I worked on this homework with...

I first worked by myself for 2 hours, but got stuck on problem 5, so I went to office hours on...

Then I went to homework party for a few hours, where I finished the homework.