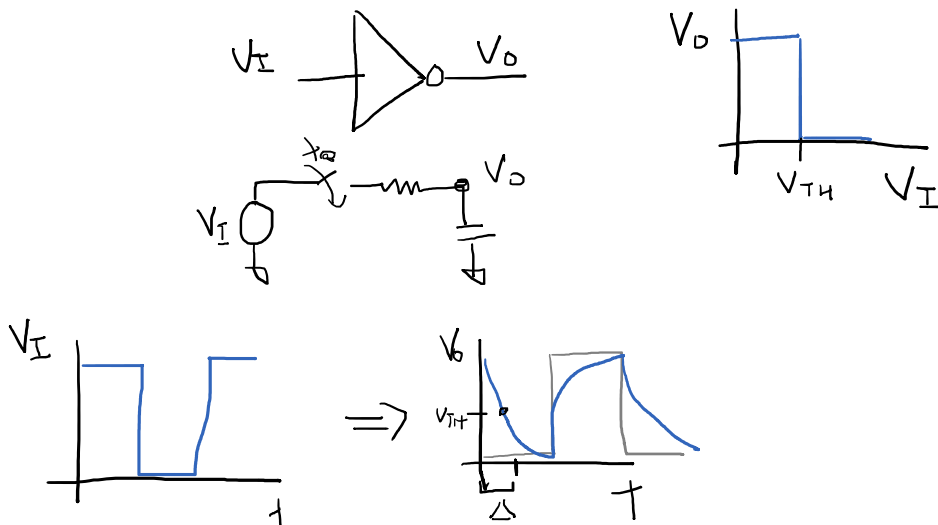


Circuits Module in Review...

I. Modeling Circuits with Differential Equations

a. First order differential equations with constant inputs

- i. Used transistors and inverters as an application of transients (capacitors charging and discharging to 0)



ii. Solved differential equation


$$\frac{d}{dt}x(t) + ax(t) = b$$

$$x(t) = b/a + (x_0 - b/a)e^{-at}$$

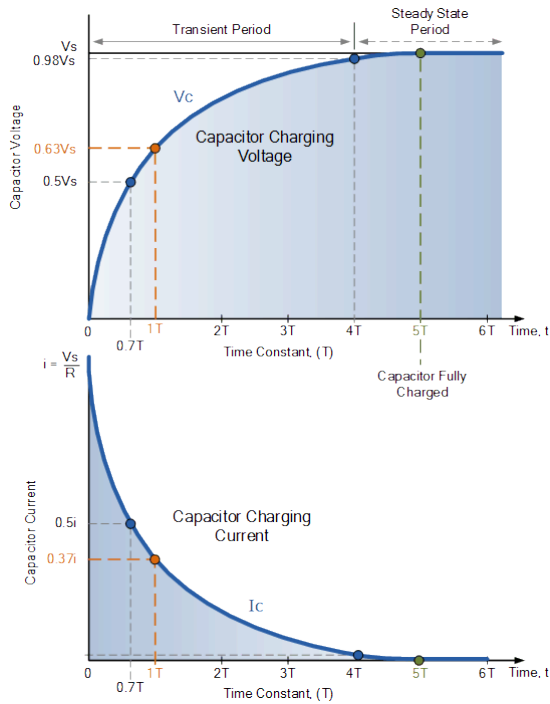- iii. Plugged in circuit values and looked at time constant τ to solve for delay Δ through an inverter

$$\text{charge} : V_o(t) = V_{DD} (1 - e^{-t/\tau}) \quad , \tau = RC$$

$$\text{discharge} : V_o(t) = V_{DD} e^{-t/\tau}$$



Time Constant	RC Value	Percentage of Maximum
		Voltage
0.5 time constant	$0.5T = 0.5RC$	39.3%
0.7 time constant	$0.7T = 0.7RC$	50.3%
1.0 time constant	$1T = 1RC$	63.2%
2.0 time constants	$2T = 2RC$	86.5%
3.0 time constants	$3T = 3RC$	95.0%
4.0 time constants	$4T = 4RC$	98.2%
5.0 time constants	$5T = 5RC$	99.3%

b. First order differential equations with time varying inputs

i. Solved differential equation

$$\frac{d}{dt} x(t) + ax(t) = g(t)$$

$$x(t) = e^{-at} \int_{t_0}^t g(\tau) e^{a\tau} d\tau + x_0 e^{-at}$$

ii. Plugged in circuit values and choose $g(t) = \tilde{V} e^{st}$ for eigenfunction properties with derivative operator

$$\frac{d}{dt} e^{st} = s e^{st}$$

$$V_o(t) = \underbrace{\frac{\tilde{V}_i}{1+sRC}}_{\text{Steady State}} e^{st} + \underbrace{\left(V_d(0) - \frac{\tilde{V}_i}{1+sRC} \right)}_{\text{Transient}} e^{-t/RC}$$

iii. Choose $s=j\omega$ to make e^{st} term periodic (as per Euler's Formula)

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t) \quad (\text{proved using Taylor Expansion})$$

If we wait long enough in RC time constants, the $e^{-t/RC}$ term will decay, leaving a

If we wait long enough in RC time constants, the $e^{-t/RC}$ term will decay, leaving a periodic steady state of just the $e^{j\omega t}$ term

II. Phasor Domain

a. Defined interesting input signals in $e^{j\omega t}$ basis

$$r \cos(\omega t + \phi) = \frac{1}{2} (\tilde{V} e^{j\omega t} + \overline{\tilde{V} e^{j\omega t}}) \quad , \quad \tilde{V} = r e^{j\phi}$$

$$r \sin(\omega t + \phi) = \frac{1}{2j} (\tilde{V} e^{j\omega t} - \overline{\tilde{V} e^{j\omega t}})$$

$$\text{Music/bio sensor/wireless signal} = r_1 \cos(\omega_1 t + \phi_1) + r_2 \cos(\omega_2 t + \phi_2) + \dots$$

b. Navigating Complex Plane with Phasors

Phasor is a complex number

$$r e^{j\phi} \quad , \quad \text{magnitude } r \quad \& \quad \text{angle } \phi$$

Used to scale or rotate another phasor or function of time


$$r e^{j\phi} \cdot q e^{j\theta} \quad \quad \quad r e^{j\phi} \cdot e^{j\omega t}$$

c. Used Phasor Domain to write complex impedances for inductors and capacitors

$$Z_R = R$$

$$Z_L = j\omega L$$


$$Z_C = \frac{1}{j\omega C}$$

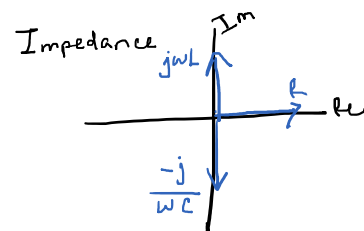

d. Used the frequency dependent impedances Z_L and Z_C to make first order frequency filters

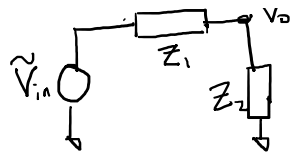i. Examined voltage divider transfer function



$$\begin{array}{c} \tilde{V}_{in} \text{ --- } [Z_1] \text{ --- } \tilde{V}_o \\ \quad \quad \quad \uparrow \\ \quad \quad \quad Z_2 \end{array} \quad H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_{in}} = \frac{Z_2}{Z_1 + Z_2}$$



$$H(j\omega) = \frac{\tilde{V}_o}{\tilde{V}_{in}} = \frac{Z_1}{Z_1 + Z_2}$$


ii. Plotted magnitude $|H(j\omega)|$ and angle $\angle H(j\omega)$ with bode plots
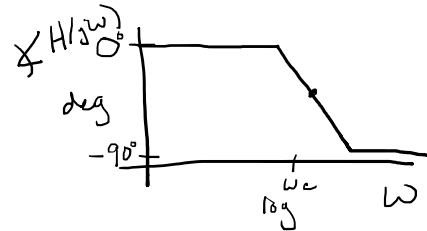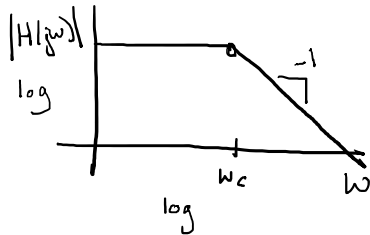
$$\text{Ex. } H(j\omega) = \frac{1}{1 + j\omega RC}$$




e. Made second order filters to filter interferers and noise better

i. Second order lowpass

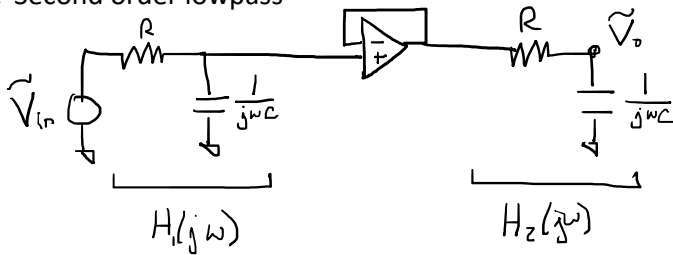


$$H(j\omega) = H_1(j\omega) H_2(j\omega) = \frac{1}{(1 + j\omega RC)^2}$$

ii. Second order bandpass

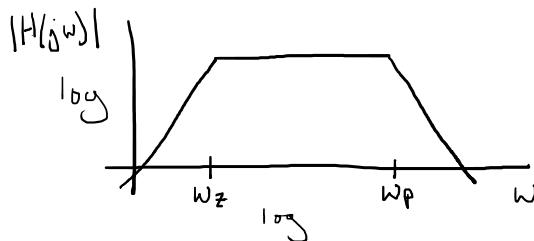

$$H(j\omega) = \frac{j\omega/\omega_z}{(1 + j\omega/\omega_c)} \cdot \frac{1}{(1 + j\omega/\omega_p)}$$

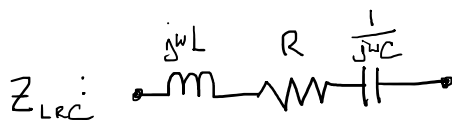F. Cancelled Imaginary Impedances at the Resonant Frequency



$$Z_{LRC} = R + j(\omega L - \frac{1}{\omega C})$$

$$Z_{LRC} \text{ Purely real at } \omega_r L = \frac{1}{\omega_r C}$$

$$\omega^2 = \frac{1}{LC}$$

Today


- I. Representing more function in e^{jwt} basis
- II. Back to diff eqns
 - a. Second order in time domain
 - b. Diagonal matrices
 - c. Diagonalization with eigen decomposition
 - d. Stability and eigenvalues

I. Representing more function in e^{jwt} basis


Use linear combinations of e^{jwt} to represent cosines,
sines, music, wireless communication

Square wave?


```
y = sin(t);
```

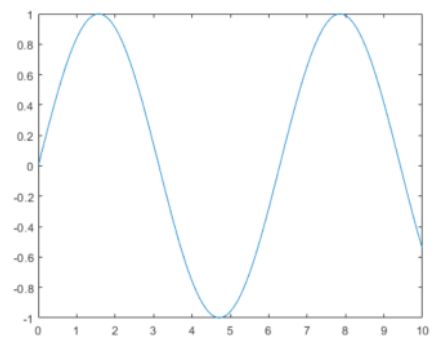

$$y = \sin(t) + \sin(3*t)/3;$$

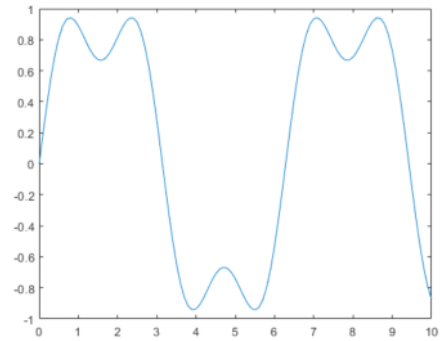
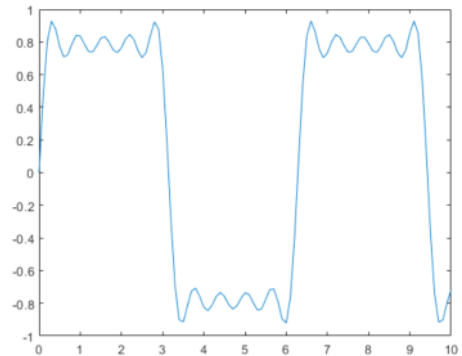
$$y = \sin(t) + \sin(3*t)/3 + \sin(5*t)/5 + \sin(7*t)/7 + \sin(9*t)/9;$$



Much like a Taylor Series, can represent sq wave, but I need infinite sines to do it



Could put a sq wave into phasor domain and look at the effect transfer function




Would need infinite sines to do this



Phasor domain is not always the best way to examine functions like a sq wave

II. Back to Differential Equations

A. Second order in time domain

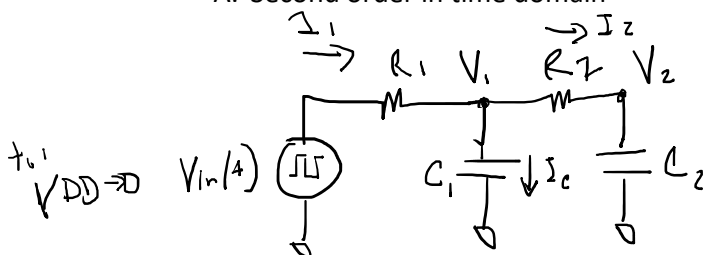

$$I_1 = I_C + I_2$$

$$I_1 = \frac{V_{in} - V_1}{R_1}$$

$$I_2 = \frac{V_1 - V_2}{R_2}$$

$$V'_m(0) = 0$$

$$V_z(0) = V_1(0) = V_{DD}$$

$$\frac{1}{R_z} = \frac{dV_z}{dt} C_z$$

$$I_C = \frac{d}{dt} V_1 C_1$$

$$\frac{d}{dt} V_1 = \frac{I_1}{C_1} - \frac{I_z}{C_1} = \frac{V_{DD} - V_1}{R_1 C_1} - \frac{V_1 - V_z}{R_z C_1}$$

$$\left[\begin{array}{l} \frac{d}{dt} V_1 = \frac{V_z}{R_z C_1} - V_1 \left(\frac{1}{R_1 C_1} + \frac{1}{R_z C_1} \right) \\ \frac{d}{dt} V_z = \frac{V_1}{R_z C_z} - \frac{V_z}{R_z C_z} \end{array} \right.$$

second order
diff eqn

matrix
representation


$$\left(\frac{d}{dt} \right)^2 x(t) + a \frac{d}{dt} x(t) + b x(t) = c$$

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_z \end{bmatrix} = \begin{bmatrix} A \end{bmatrix} \begin{bmatrix} V_1 \\ V_z \end{bmatrix}$$

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_z \end{bmatrix} = \begin{bmatrix} -\left(\frac{1}{R_1 C_1} + \frac{1}{R_z C_1} \right) & \frac{1}{R_z C_1} \\ \frac{1}{R_z C_z} & -\frac{1}{R_z C_z} \end{bmatrix} \begin{bmatrix} V_1 \\ V_z \end{bmatrix}$$

$$\frac{d}{dt} \vec{x} = A \vec{x} \quad \leftarrow e^{ct} \text{ somewhere involved}$$

B. Diagonal A example

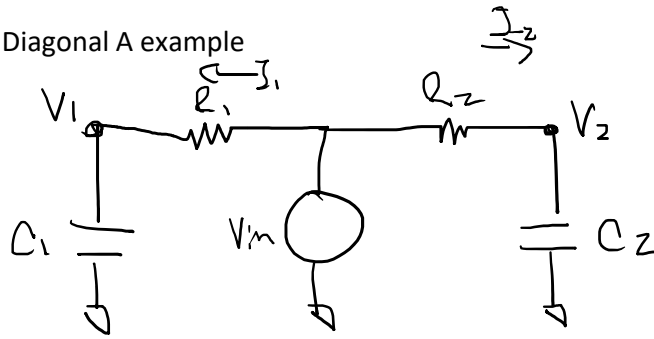

$$V_{in}: VDD \rightarrow 0$$

$$V_{in}(0) = 0$$

$$V_2(0) = V_1(0) = VDD$$

$$\frac{V_{in} - V_1}{R_1} = I_1 = \frac{d}{dt} V_1 C_1$$

$$\frac{d}{dt} V_1 = \frac{-V_1}{R_1 C_1}$$

$$\frac{V_{in} - V_2}{R_2} = I_2 = \frac{d}{dt} V_2 C_2$$

\Rightarrow

$$\frac{d}{dt} V_2 = \frac{-V_2}{R_2 C_2}$$

$$\frac{d}{dt} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{-1}{R_1 C_1} & 0 \\ 0 & \frac{-1}{R_2 C_2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$V_1(t) = C_1 e^{\lambda_1 t} \quad \lambda_1 = \frac{-1}{R_1 C_1}$$

$$V_2(t) = C_2 e^{\lambda_2 t} \quad \lambda_2 = \frac{-1}{R_2 C_2}$$

Want: apply some transform to our matrices

$$\begin{array}{ccc} \vec{x} & \xrightarrow{A} & A\vec{x} \\ \downarrow B & & \uparrow B^{-1} \end{array}$$

$$\begin{matrix} \mathcal{B} \\ \downarrow \\ \vec{x} \end{matrix} \xrightarrow{D} \begin{matrix} \vec{x}' \\ \uparrow \\ \mathcal{B}' \end{matrix}$$

convenient basis
where D is diagonal

C. Diagonalization with Eigendecomposition

Eigenvalues & Eigenvectors

$$A\vec{v}_n = \lambda_n \vec{v}_n$$

A has eigenvalues $\lambda_1, \lambda_2, \dots, \lambda_n$

and eigenvectors $\vec{v}_1, \vec{v}_2, \dots, \vec{v}_n$

$$\begin{matrix} \downarrow & \downarrow & & \downarrow \\ \begin{bmatrix} x_{11} \\ x_{12} \\ \vdots \\ x_{1k} \end{bmatrix}, & \begin{bmatrix} x_{21} \\ x_{22} \\ \vdots \\ x_{2k} \end{bmatrix}, & \dots & \begin{bmatrix} x_{k1} \\ x_{k2} \\ \vdots \\ x_{kk} \end{bmatrix} \end{matrix}$$

Create a matrix V of eigenvectors

$$V = [\vec{v}_1 \ \vec{v}_2 \ \dots \ \vec{v}_n]$$
~~$$= [\vec{x}_1 \ \vec{x}_2 \ \dots \ \vec{x}_k]$$~~

$$= \begin{bmatrix} x_{11} & x_{21} & \dots & x_{k1} \\ x_{12} & x_{22} & \dots & x_{k2} \\ \vdots & \vdots & \ddots & \vdots \\ x_{1k} & x_{2k} & \dots & x_{kk} \end{bmatrix}$$

$$\begin{aligned} AV &= A[\vec{v}_1 \ \vec{v}_2 \ \dots \ \vec{v}_n] \\ &= [A\vec{v}_1 \ A\vec{v}_2 \ \dots \ A\vec{v}_n] \end{aligned}$$

$$= [\lambda_1 \vec{v}_1 \quad \lambda_2 \vec{v}_2 \quad \dots \quad \lambda_n \vec{v}_n]$$

$$= \begin{bmatrix} \lambda_1 x_{11} & \lambda_2 x_{21} & \dots & \lambda_k x_{k1} \\ \lambda_1 x_{12} & \lambda_2 x_{22} & \dots & \lambda_k x_{k2} \\ \vdots & \vdots & \ddots & \vdots \\ \lambda_1 x_{1k} & \lambda_2 x_{2k} & \dots & \lambda_k x_{kk} \end{bmatrix}$$

$$= \begin{bmatrix} x_{11} & x_{21} & \dots & x_{k1} \\ x_{12} & x_{22} & \dots & x_{k2} \\ \vdots & \vdots & \ddots & \vdots \\ x_{1k} & x_{2k} & \dots & x_{kk} \end{bmatrix} \begin{bmatrix} \lambda_1 & 0 & \dots & 0 \\ 0 & \lambda_2 & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & \lambda_k \end{bmatrix}$$

$$AV = V\Lambda$$

$$\begin{array}{ccc} \vec{x} & \xrightarrow{\quad} & A\vec{x} \\ \downarrow V & & \uparrow V \\ \tilde{\vec{x}} & \xrightarrow{\Lambda} & \Lambda\tilde{\vec{x}} \end{array}$$

$$\frac{d}{dt} \vec{x} = A\vec{x}$$

$$\left[\frac{d}{dt} \tilde{\vec{x}} = \Lambda \tilde{\vec{x}} \right]$$

$$\tilde{\vec{x}} = V^{-1} \vec{x}, \quad \vec{x} = V \tilde{\vec{x}}$$

In our convenient domain

$$\frac{d}{dt} \tilde{\vec{x}} = \Lambda \tilde{\vec{x}} \Rightarrow \tilde{\vec{x}} = \begin{bmatrix} c_1 e^{\lambda_1 t} \\ c_2 e^{\lambda_2 t} \\ \vdots \\ c_n e^{\lambda_n t} \end{bmatrix} \quad \begin{array}{l} \text{solve for constants} \\ c_1, c_2, \dots, c_n \\ \text{with initial conditions} \\ \tilde{\vec{x}}(0) = V^{-1} \vec{x}(0) \end{array}$$

$$\vec{x} = V \tilde{\vec{x}}$$




$$\vec{x} = \begin{bmatrix} c'_1 e^{\lambda_1 t} + c'_2 e^{\lambda_2 t} + \dots + c'_n e^{\lambda_n t} \\ c'_1 e^{\lambda_1 t} + \dots + c'_n e^{\lambda_n t} \\ \vdots \\ c'_1 e^{\lambda_1 t} + \dots + c'_n e^{\lambda_n t} \end{bmatrix}$$

$$\begin{bmatrix} C_1' e^{a_1 t} + \dots \\ C_n' e^{a_n t} + \dots \end{bmatrix}$$

could solve for constants here


D. Stability and Eigen Values

i. look at Ce^{at} for various a

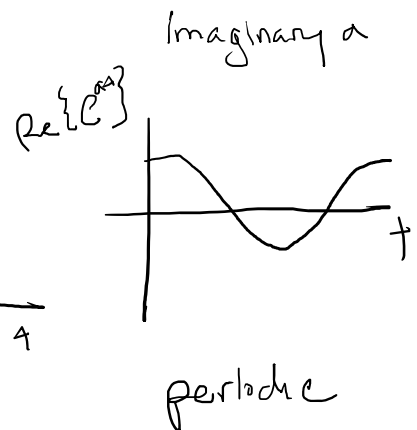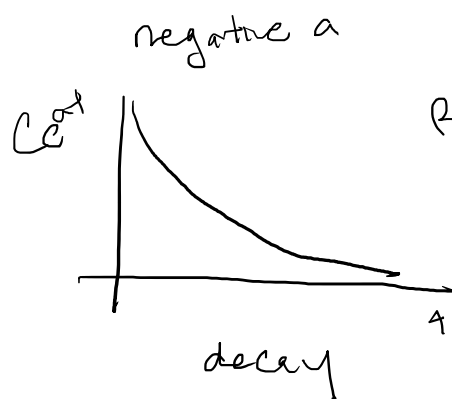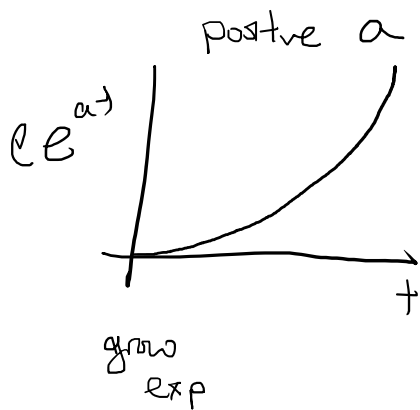

Look at eigenvalues of matrix A and know if x is going to grow, decay, or oscillate

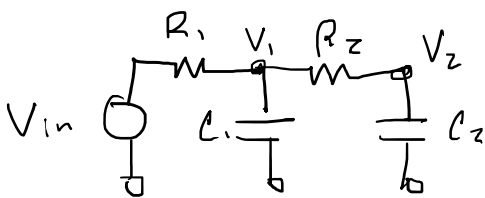ii. Solve for eigenvalues of our second order RC



$$A = \begin{bmatrix} -\left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1}\right) & \frac{1}{R_2 C_1} \\ \frac{1}{R_2 C_1} & -\frac{1}{R_2 C_2} \end{bmatrix}$$

Choose R & C

$$A = \begin{bmatrix} -5 & 2 \\ 2 & -2 \end{bmatrix}$$

Solve for the roots of the characteristic eqn

$$A\vec{v}_i = \lambda_i \vec{v}_i$$

$$(A - \lambda_i I) \vec{v}_i = 0$$


→ $\det(A - \lambda I)$ find the roots

$$\begin{aligned} \det \begin{pmatrix} \lambda + 5 & 2 \\ 2 & \lambda + 2 \end{pmatrix} &= (\lambda + 5)(\lambda + 2) - 4 \\ &= \lambda^2 + 7\lambda + 6 \\ &= (\lambda + 6)(\lambda + 1) \end{aligned}$$

$$\text{roots, } \lambda_{1,2} = -6, -1$$

$$\text{Expect } \vec{x} = \begin{bmatrix} c_0' e^{-6t} + c_1 e^{-t} \\ c_2 e^{-6t} + c_3 e^{-t} \end{bmatrix} \leftarrow \text{Voltages will decay}$$


iii. Eigenvalues for LC

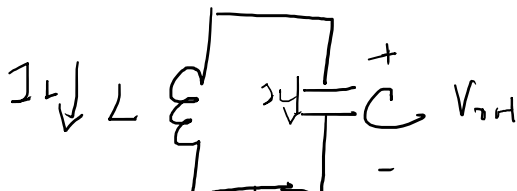

$$I_L = -I_C$$

$$V_L = V_C = V_{\text{out}}$$

$$-d - 1$$

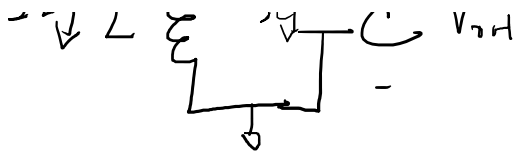

$$\begin{cases} V_L - V_C = V_{out} \\ \frac{d}{dt} I_L L = V_{out} \\ \frac{d}{dt} V_{out} C = -I_L \end{cases}$$

$$\frac{d}{dt} \begin{bmatrix} V_{out} \\ I_L \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix}}_A \begin{bmatrix} V_{out} \\ I_L \end{bmatrix}$$


$$\det(A) = \begin{vmatrix} -\lambda & -\frac{1}{C} \\ \frac{1}{L} & -\lambda \end{vmatrix} = \lambda^2 + \frac{1}{LC} \leftarrow \text{solve for the roots}$$

$$\lambda_{1,2} = 0 \pm j \frac{1}{\sqrt{LC}} \leftarrow \text{imaginary roots}$$

$$\vec{x} = \begin{bmatrix} V_{out} \\ I_L \end{bmatrix} \leftarrow \text{oscillate}$$


-LC tank, used to make oscillator

iii. Eigenvalues of LCR

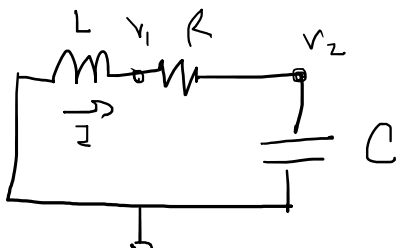

$$\textcircled{1} V_1 - V_2 = RI$$

$$\frac{d}{dt} (V_2 - 0) C = I$$

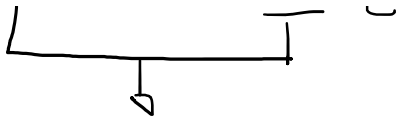

$$\frac{d}{dt} (V_2 - 0) L = L$$

$$(0 - V_1) = \frac{d}{dt} I L$$

\uparrow
①

$$\frac{d}{dt} V_2 = \frac{1}{C} I$$

$$\frac{d}{dt} I = \frac{-R I - V_2}{L}$$

$$\frac{d}{dt} \begin{bmatrix} V_2 \\ I \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix}}_A \begin{bmatrix} V_2 \\ I \end{bmatrix}$$

$$\det \left(\begin{bmatrix} -\lambda & \frac{1}{C} \\ \frac{1}{L} & -\frac{R}{L} - \lambda \end{bmatrix} \right) = \lambda^2 + \frac{R}{L} \lambda + \frac{1}{LC}$$

$$\text{roots} \rightarrow \lambda_{1,2} = -\frac{1}{2} \frac{R}{L} \pm \sqrt{\left(\frac{1}{2} \frac{R}{L}\right)^2 - \frac{1}{LC}}$$

potential for
imaginary values

Case 1.

$$\left(\frac{1}{2} \frac{R}{L}\right)^2 = \frac{1}{LC} \Rightarrow \lambda_{1,2} = -\frac{1}{2} \frac{R}{L} \leftarrow \text{decay}$$

Case 2.

$$\left(\frac{1}{2} \frac{R}{L}\right)^2 > \frac{1}{LC} \Rightarrow \lambda_{1,2} = \text{distinct real valued} \leftarrow \text{decay or grow}$$

Case 3.

$$\left(\frac{1}{2} \frac{R}{L}\right)^2 < \frac{1}{LC} \Rightarrow \lambda_{1,2} = \underbrace{-\frac{1}{2} \frac{R}{L}}_{\text{real}} \pm j \underbrace{\sqrt{\frac{1}{LC} - \left(\frac{1}{2} \frac{R}{L}\right)^2}}_{\text{imaginary}}$$

decay & oscillation

ringing

