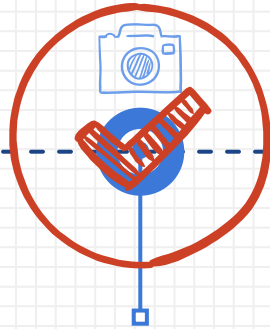


EECS16A Touchscreen 1

TA, ASE, ASE, ASE



Semester Outline



Imaging
Module



Touchscreen
Module



APS
Module

- Breadboarding
- Build multiple functional circuits
- Learn how to use Multimeter

Poll time!

Review of breadboarding practices from Imaging 1.

1. Which of the following are good breadboarding practices

- a. Check the resistor value by its color bands
- b. Plug in component legs in different rows
- c. Use black and red wires for the rails

2. For which of the following components does polarity matter?

Resistor

LED

Capacitor

Ambient Light Sensor



Poll time!

Review of breadboarding practices from Imaging 1.

1. Which of the following are good breadboarding practices

- a. Check the resistor value by its color bands
- b. Plug in component legs in different rows
- c. Use black and red wires for the rails

2. For which of the following components does polarity matter?

Resistor

LED


Capacitor

Ambient Light Sensor




Tinkercad

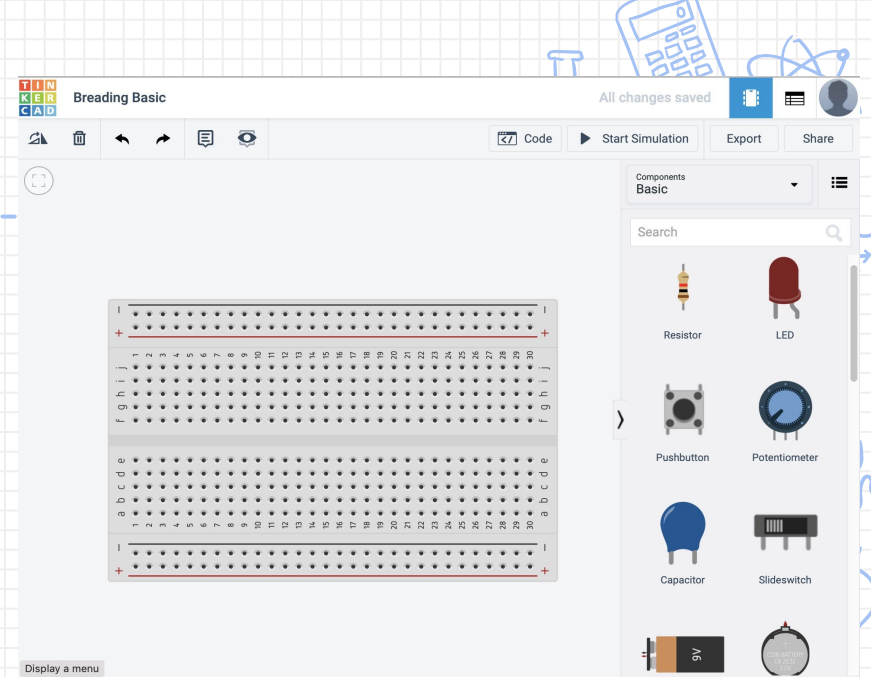- Circuit design prototyping software
 - Primary circuit software in this course
 - Useful for many different electrical projects
- Ran online using an Autodesk account




Launchpad Review

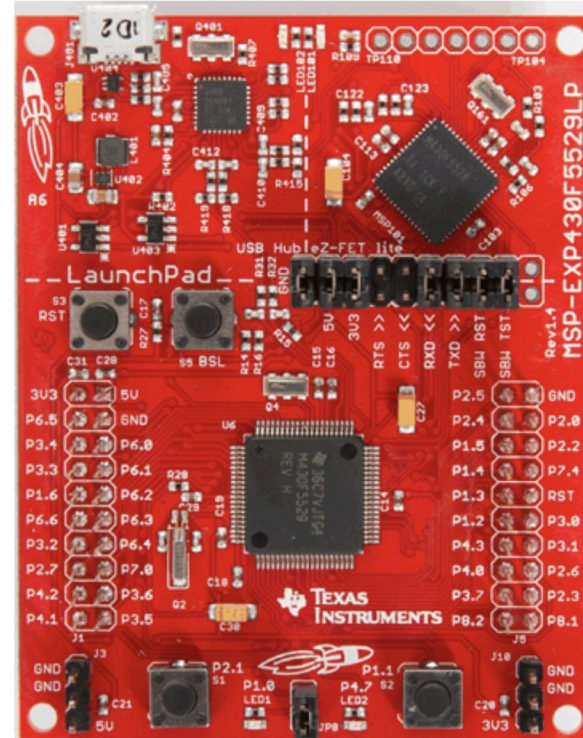
- Micro-Controller
- Power Supply
- Voltmeter



Multimeter (Circuit Debugger)

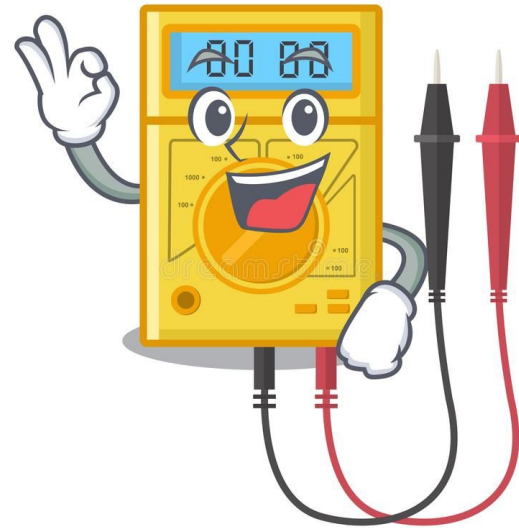- Voltmeter
 - Infinite resistance
 - Connect in parallel with component
- Ammeter
 - Very low resistance
 - Act as a wire in the circuit
 - Connect in series with component
- Ohmmeter
 - Remove resistor from circuit before use
 - Connect in parallel with resistor






diode



diode



current


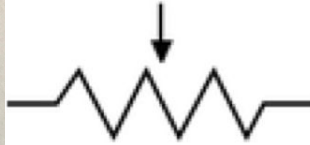




Operational Amplifier (OpAmp)

741



Operational
Amplifier

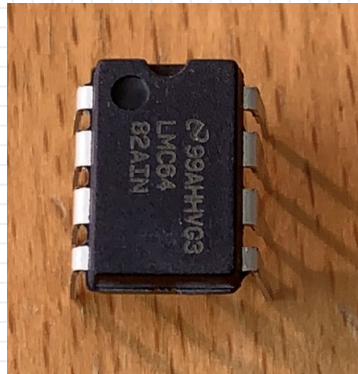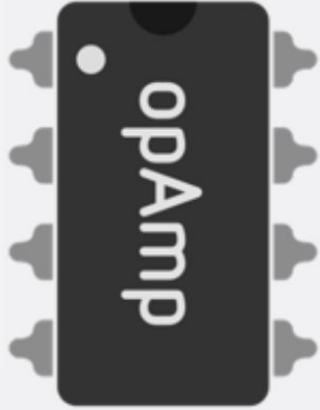


The 741 Operational Amplifier

Fig.2

Pinout

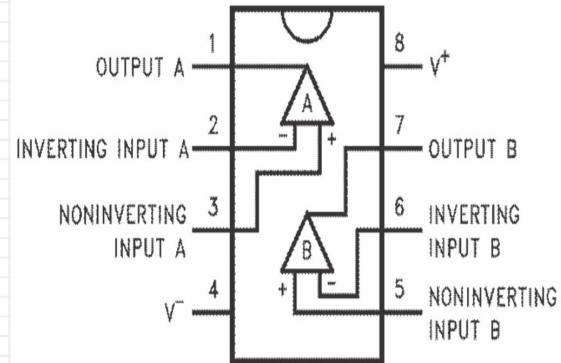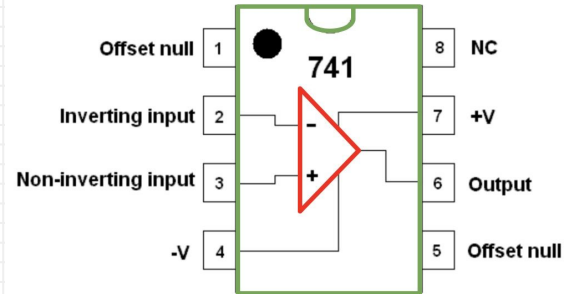

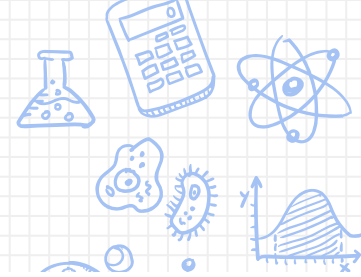

Voltage Divider Circuit

What is the voltage value u_2 at Node 2?


$$I_y = I_z = V_s / (R_1 + R_2) \text{ (Ohm's Law)}$$


$$u_2 - u_0 = R_2 * I_z$$

$$u_2 - 0 = R_2 * V_s / (R_1 + R_2)$$

$$u_2 = V_s * R_2 / (R_1 + R_2)$$

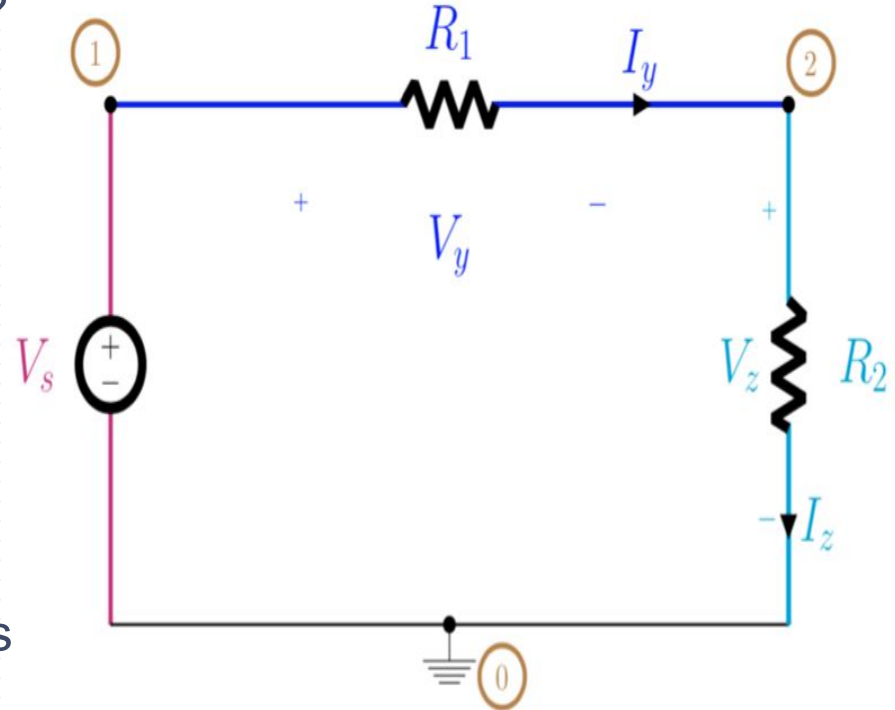What is the voltage value u_2 if R_1 equals to R_2 ?



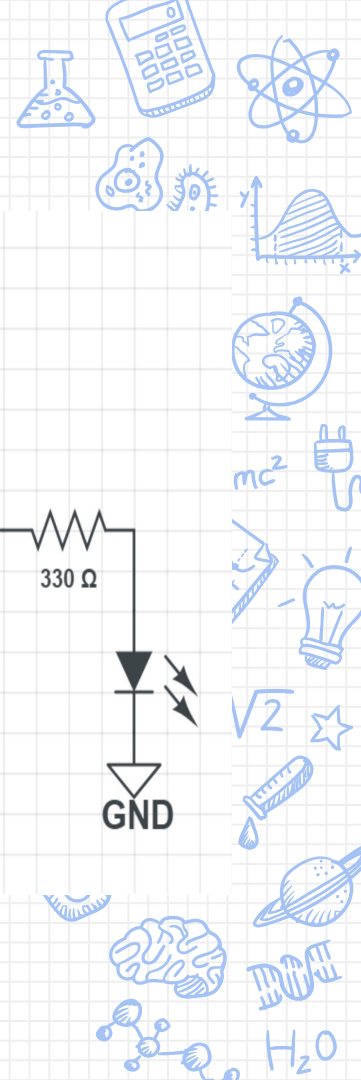

Mystery Circuit


- Voltage Divider Circuit

- Find it in this circuit?


- Potentiometer Circuit

- Find it in this circuit?

Fig. 1

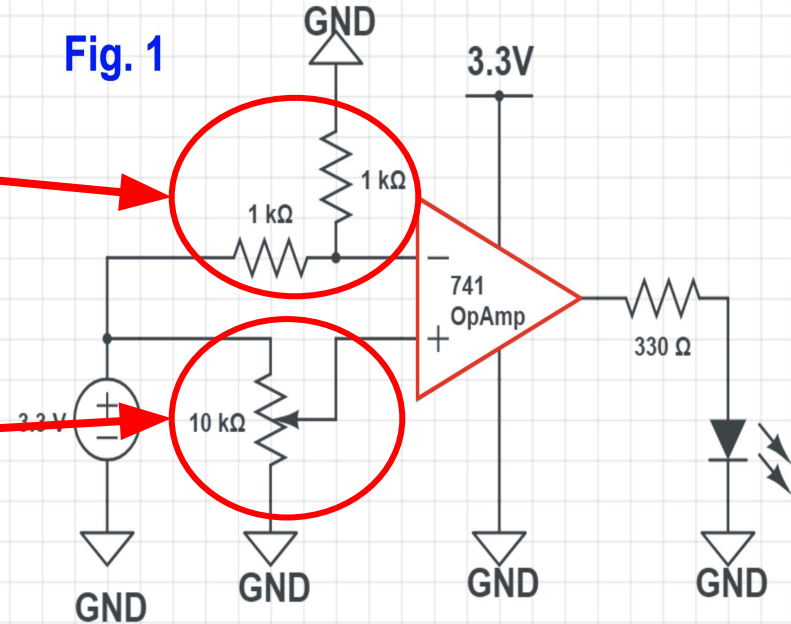


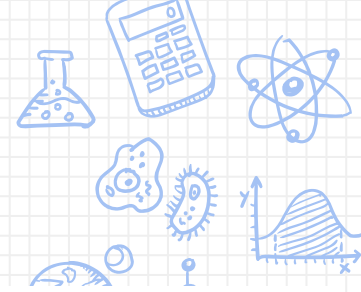
- A breadboarding exercise - not meant to test circuit analysis knowledge



Series and Parallel Resistors

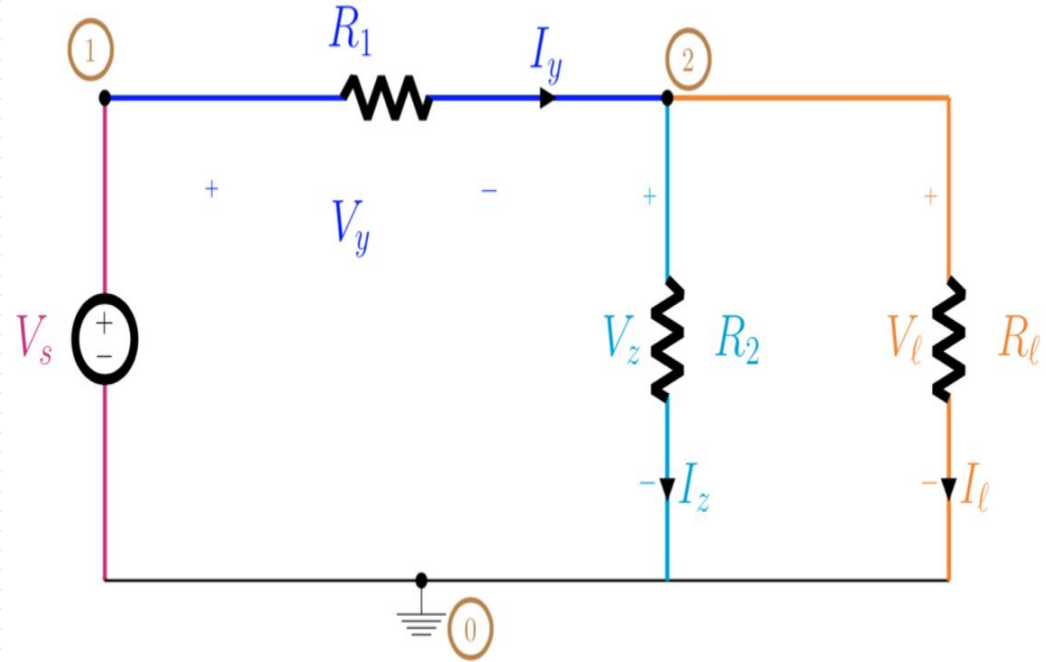- What is the relationship between R_2 and R_l ?
- What about R_l with R_2 and R_l ?



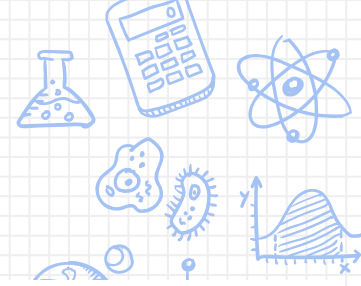


Series and Parallel Resistors

Resistor Equation:

$$R = (\rho * L) / A$$

When in parallel what parameter changes? How does this affect overall resistance, (ie: R_{eq})

What about in series?

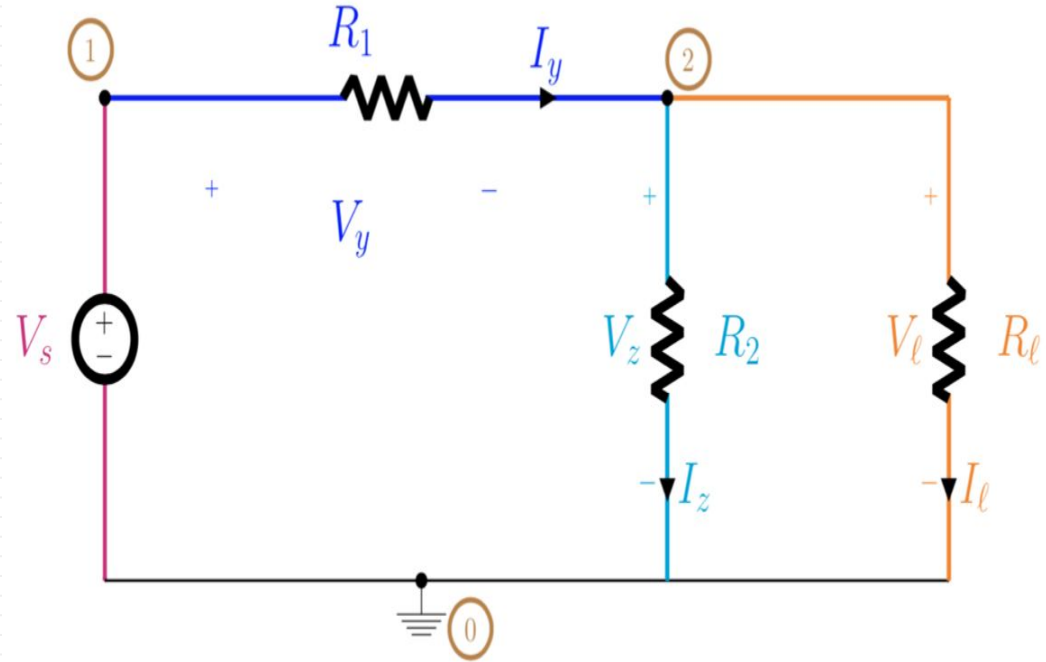

Lab Structure

- Tasks are labelled **Software** or **Hardware** else **Software** in the title
- For students with hardware:
 - Some TinkerCAD tasks
 - Some hardware tasks
- For students without hardware:
 - Do the TinkerCAD versions of all tasks
 - Watch videos and work with group members to see hardware setup
- Optional Task 4 at the end of the notebook to try building more circuits



- Go through the TinkerCAD tutorial (if you haven't already)
- Try to debug your circuit by yourself before you ask the TAs
 - However, don't spend too long, after 5 minutes or so queue for help
- Task 3c: MSP acts as single point voltmeter