

Last time on EE16B.....

(Post lecture notes in purple)

(Imp equations boxed in green)

Transfer function will represent the magnitude and phase alteration, which are fully known given all values of passive devices (R, L, C) and the frequency  $\omega$


$$H(j\omega) = |H(j\omega)| e^{j\angle H(j\omega)}$$

Frequency Response

examine  $H(j\omega)$  over freq  $\omega = 0 \rightarrow \infty$

Filters


Low Pass Filters

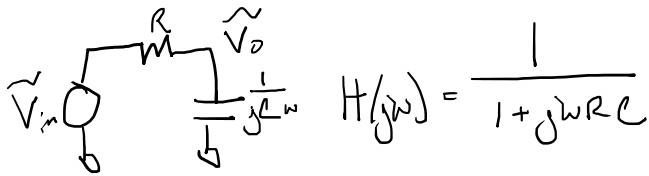

$$H(j0) \rightarrow \frac{1}{1} = 1$$

$$H(j\infty) \rightarrow \frac{1}{j\infty} = -j0$$

High Pass Filters

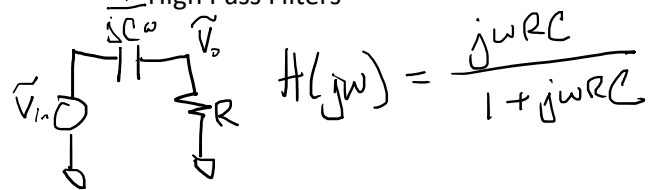

$$H(j0) \rightarrow \frac{j0}{1} = j0$$

$$H(j\infty) \rightarrow \frac{j\infty}{j\infty} = 1$$

Impedance over Frequency

$$\underline{\omega = 0}$$

$$|Z_R| = R$$

$$|Z_C| = \infty \leftarrow \text{open}$$

$$\underline{\omega = \infty}$$

$$|Z_R| = R$$

$$|Z_C| = 0 \leftarrow \text{short}$$


$$|Z_c| = \infty \leftarrow \text{open}$$

$$|Z_c| = 0 \leftarrow \text{short}$$

$$|Z_c| = 0 \leftarrow \text{short}$$

$$|Z_c| = \infty \leftarrow \text{open}$$


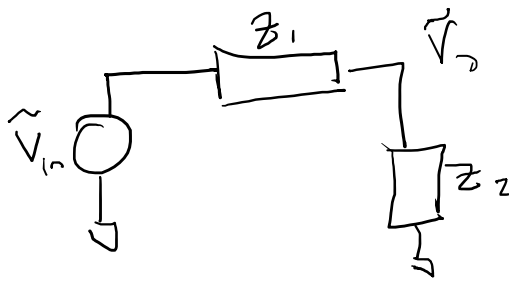
Predict filter type given a voltage divider shape





$$\frac{\tilde{V}_{Z1}}{\tilde{V}_{Z2}} = \frac{Z_1}{Z_2} \quad (\tilde{V}_o = \tilde{V}_{Z2})$$

Plot Frequency Response with Bode Plots

LowPass

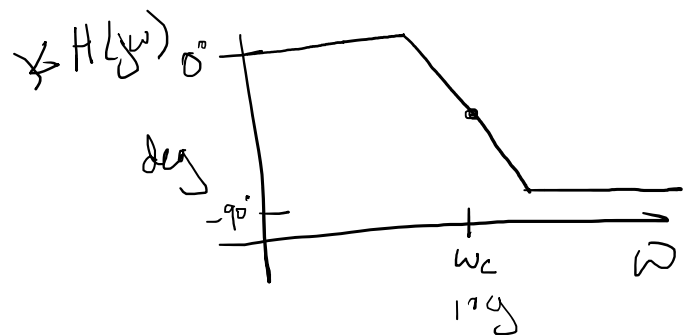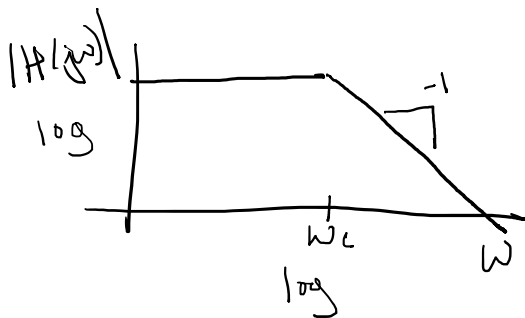

High Pass

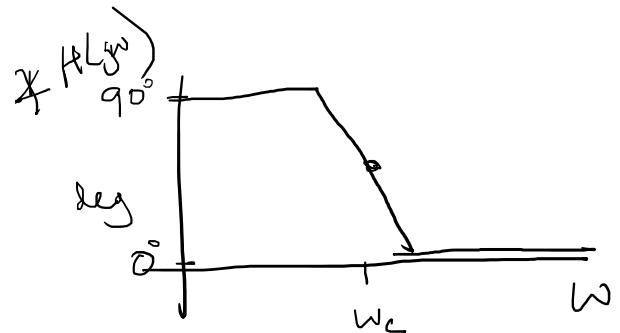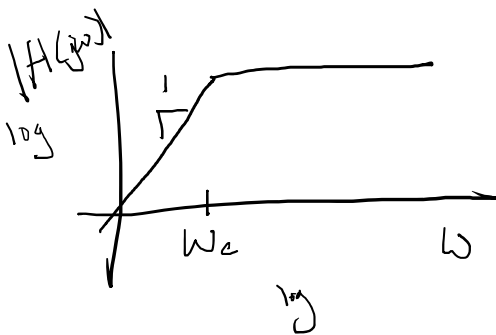

General Factored  $H(j\omega)$




$$H(j\omega) = \frac{(j\omega/\omega_1)(1 + j\omega/\omega_2)}{(1 + j\omega/\omega_1)(1 + j\omega/\omega_3)(1 + j\omega/\omega_3)} \quad \leftarrow \text{zeros} \quad \leftarrow \text{poles}$$


## I. Second Order Filters
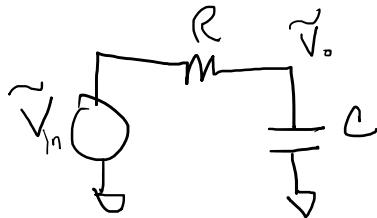
### a. Filtering an Interferer with a First Order Filter

$$V_{in} = \tilde{V}_{in} \left( \overset{\text{signal}}{e^{j\omega_s t}} + \overset{\text{noise}}{e^{j\omega_n t}} \right) \quad \omega_s < \omega_n$$


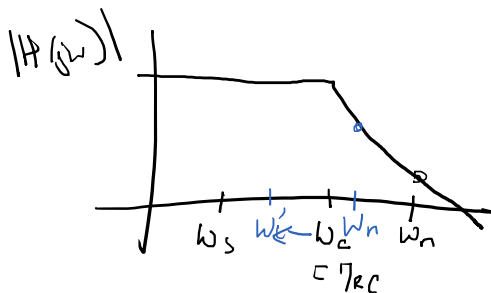
$$H(j\omega) = \frac{1}{1 + j\omega RC} \quad \leftarrow \text{single pole} \quad \omega_p = 1/RC$$




$$\omega_n = 100 \omega_c$$

$$H(j\omega_n) = \frac{1}{1 + j\omega_n/\omega_c} = \frac{1}{1 + j100\omega_c/\omega_c} = \frac{1}{1 + j100}$$

$$\approx \frac{1}{j100} = \frac{-j}{100}$$

$$|H(j\omega_n)| \approx \frac{1}{100} \quad \angle H(j\omega_n) \approx -\frac{\pi}{2}$$

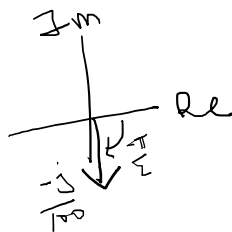

What if noise frequency is lower (closer to our desired signal frequency)

$$\omega_n = 10 \omega_c$$


$$|H(j\omega_n)| \approx \frac{1}{10}$$

$$\angle H(j\omega_n) \approx -\frac{\pi}{2}$$

$$|H(j\omega)| \approx \frac{1}{10}$$

$$\angle H(j\omega) \approx -\frac{\pi}{2}$$


## b. Second Order Filter

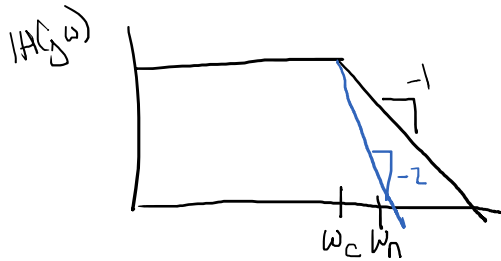

Design a filter with two poles at  $\omega_c$

$$H(j\omega) = \frac{1}{(1 + j\omega/\omega_c)(1 + j\omega/\omega_c)}$$
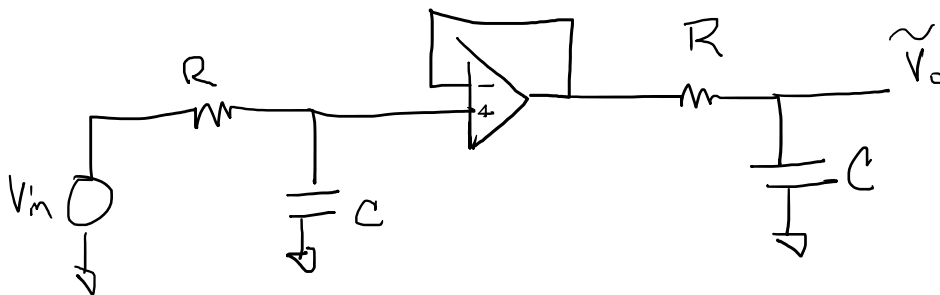
$$\tilde{V}_i \rightarrow [H(j\omega)] \xrightarrow{H(j\omega) \tilde{V}_i} [H(j\omega)] \rightarrow H(j\omega) \cdot H(j\omega) \tilde{V}_i$$




$$H_{\text{tot}}(j\omega) = \frac{1}{1 + j\omega/\omega_c} \cdot \frac{1}{1 + j\omega/\omega_c}$$

$$\omega_n = 10\omega_c$$

$$H_{\text{tot}}(j\omega) = \frac{1}{1 + j^{10}\omega_c/\omega_c} \cdot \frac{1}{1 + j^{10}\omega_c/\omega_c} = \frac{1}{1 + j^{10}} \cdot \frac{1}{1 + j^{10}}$$

$$\approx \frac{1}{j^{10}} \cdot \frac{1}{j^{10}} = \frac{-j}{10} \cdot \frac{-j}{10} = \frac{-1}{100}$$



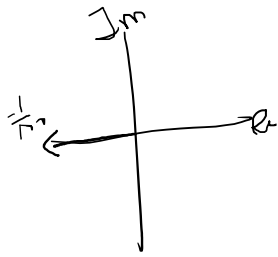
$$\approx \frac{1}{j10} \cdot \frac{1}{j10} = \frac{-j}{10} \cdot \frac{-j}{10} = \frac{-1}{100}$$



$$|H(j\omega)| \approx \frac{1}{100}$$

$$\angle H(j\omega) \approx \pi$$

### C. Second Order Bandpass Filter

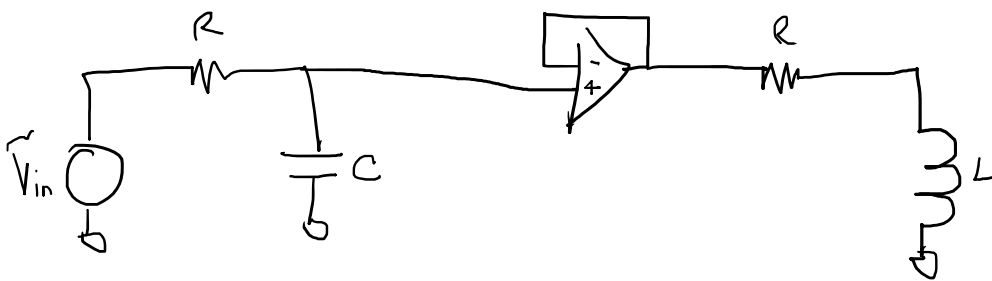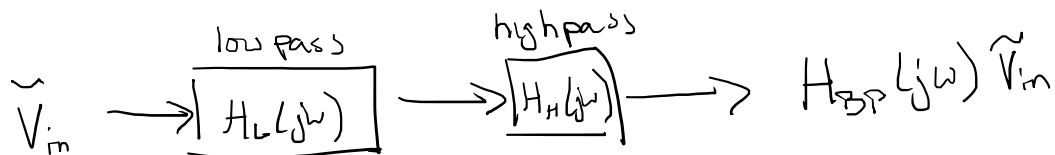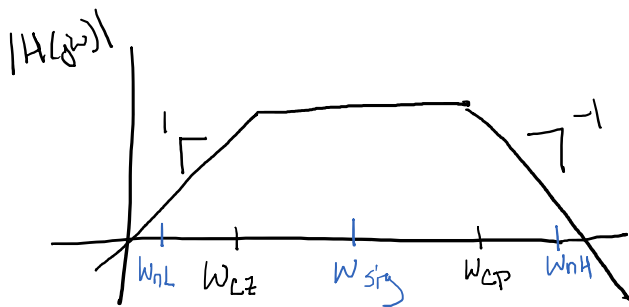


$$H_L(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$H_H(j\omega) = \frac{j\omega L}{R + j\omega L} \cdot \frac{1}{R}$$

$$H_{BP}(j\omega) = H_L(j\omega) \cdot H_H(j\omega) = \frac{1}{(1 + j\omega R C)} \cdot \frac{j\omega \frac{L}{R}}{(1 + j\omega \frac{L}{R})}$$


$$H_{BP}(j\omega) = H_L(j\omega) \cdot H_H(j\omega) = \overline{(1 + j\omega RC)} \cdot \overline{(1 + j\omega \frac{L}{R})}$$
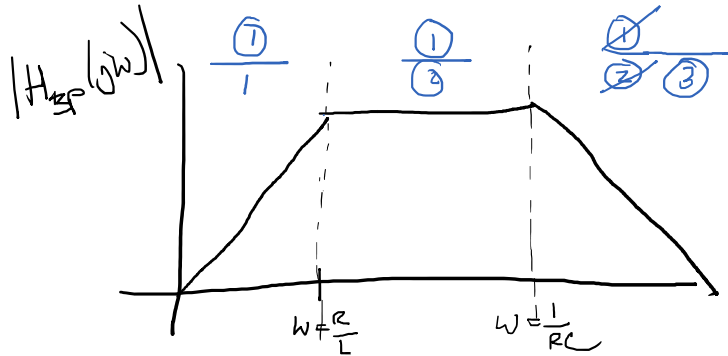
$$= \frac{j\omega \frac{L}{R} \textcircled{1}}{\textcircled{3}(1 + j\omega RC) \textcircled{2}(1 + j\omega \frac{L}{R})}$$



## II. Resonance

### a. Complex Impedance Practice

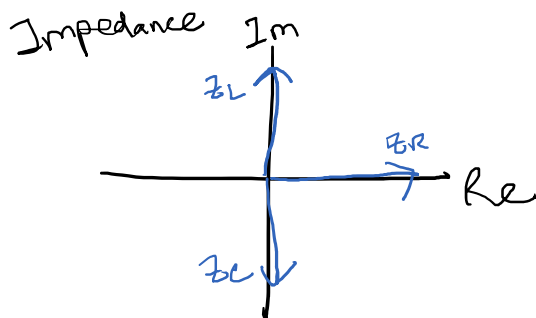


$$Z_R = R$$


$$Z_C = \frac{1}{j\omega C}$$


$$Z_L = j\omega L$$

Combinations


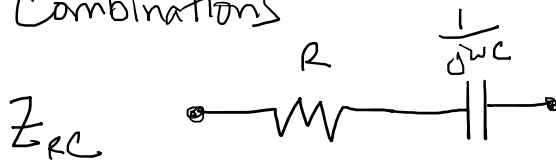


$$Z_{RC} = R + \frac{1}{j\omega C}$$

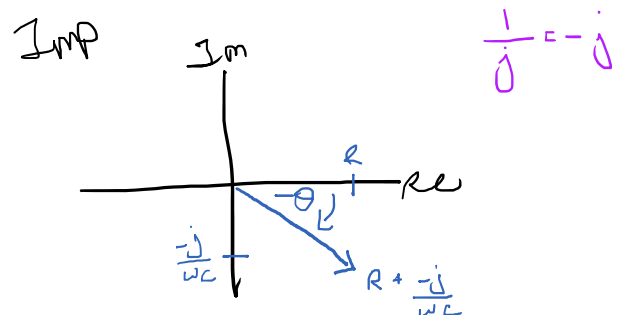


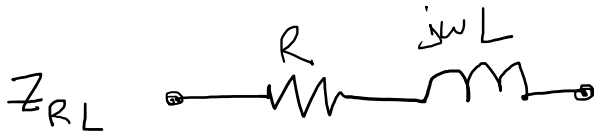

$$Z_{RL} = R + j\omega L$$

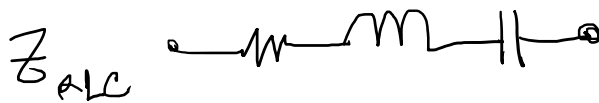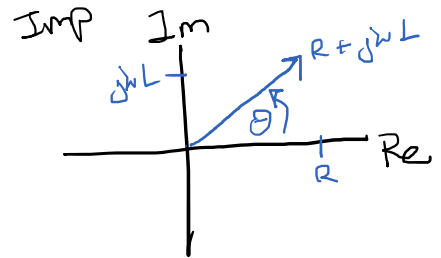
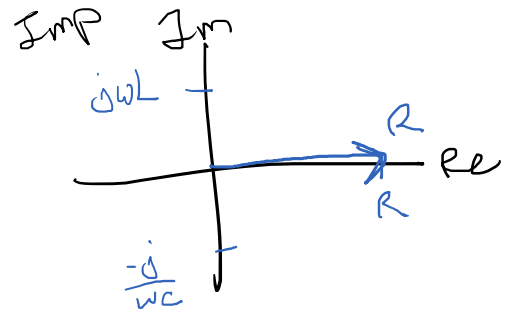
$$\begin{aligned} Z_{RLC} &= R + j\omega L + \frac{-j}{\omega C} \\ &= R + j\left(\omega L - \frac{1}{\omega C}\right) \end{aligned}$$




Could choose L and C s.t. for some  $\omega_r$  impedance is purely real

b. Resonant frequency

$$\omega_r \quad \text{where} \quad \omega_r L - \frac{1}{\omega_r C} = 0$$

Return to Power Grid

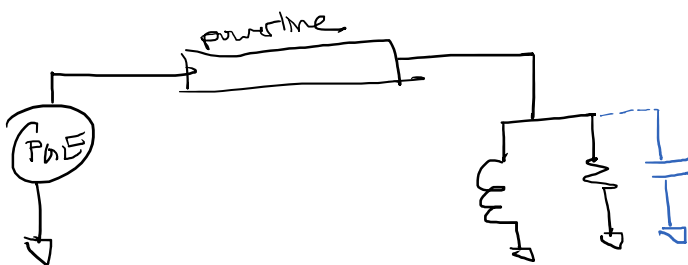


$$\omega_{\text{wall power}} = 60 \cdot 2\pi \text{ (rad/sec)}$$

$$L = 1 \text{ H}$$

$$\omega_r L = \frac{1}{\omega_r C}$$

$$\omega_r^2 = \frac{1}{LC}$$




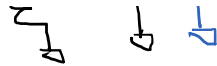

$$\omega_r^2 = \frac{1}{LC}$$

$$C = \frac{1}{(\omega_r 2\pi)^2 L}$$

c. Resonant bandpass filter

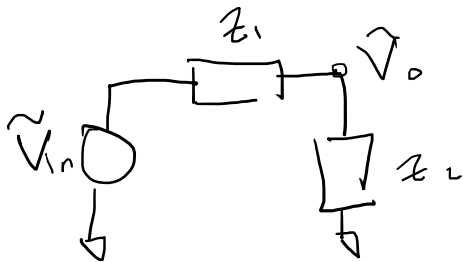

$$H(j\omega) = \frac{V_o}{V_{in}} = \frac{Z_2}{Z_2 + Z_1}$$

$\omega \neq \omega_r \Rightarrow H(j\omega) = 0$


$\omega = \omega_r \Rightarrow H(j\omega) = 1$

$\omega_r$





$$H(j\omega) = \frac{R}{R + (j\omega L + \frac{1}{j\omega C})}$$

dominates @  $\omega \to \infty$

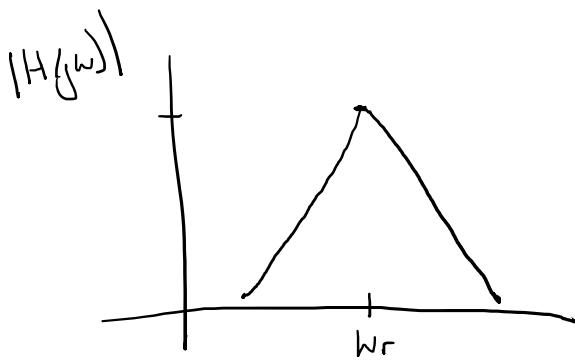


d. Application Tangent: Radio Stations

Radio Receiver

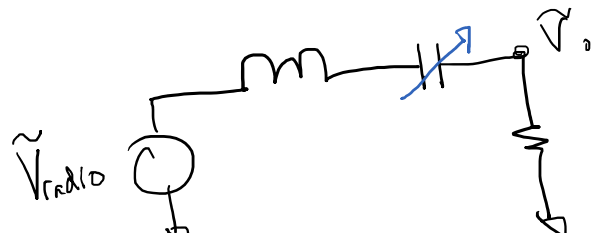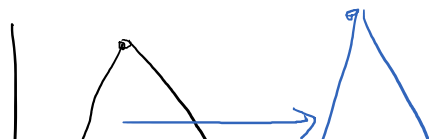

Radio  
Receiver  
Filter

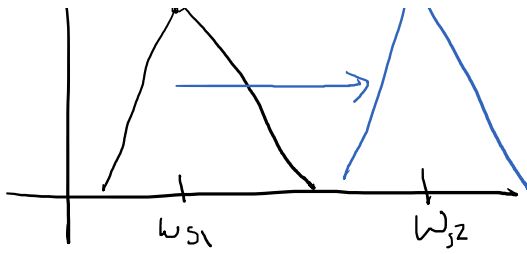

$\tilde{V}_{radio}$  



$$\omega_r^2 = \frac{1}{LC_{\text{variable}}}$$