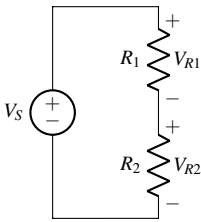
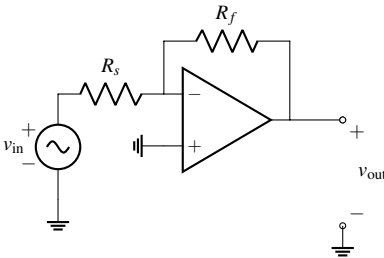
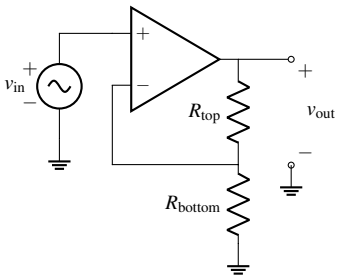
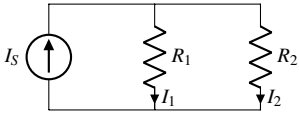
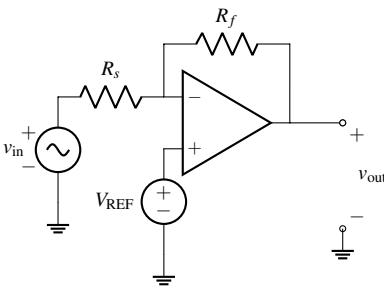
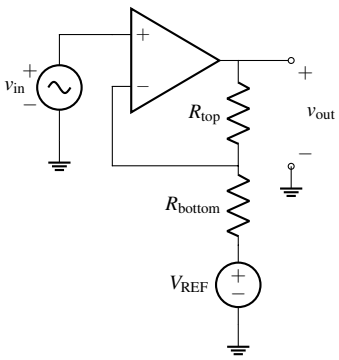
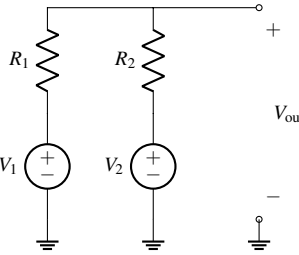
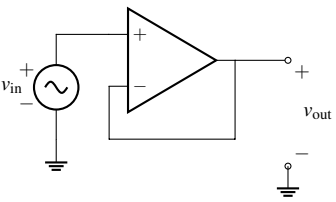


CSM 16A  
Fall 2020

Designing Information Devices and Systems I

Week 10

**Reference: Op-Amp Example Circuits**


<p><b>Voltage Divider</b></p>  $V_{R2} = V_S \left( \frac{R_2}{R_1 + R_2} \right)$	<p><b>Inverting Amplifier</b></p>  $v_{out} = v_{in} \left( -\frac{R_f}{R_s} \right)$	<p><b>Noninverting Amplifier</b></p>  $v_{out} = v_{in} \left( 1 + \frac{R_{top}}{R_{bottom}} \right)$
<p><b>Current Divider</b></p>  $I_1 = I_S \left( \frac{R_2}{R_1 + R_2} \right)$	<p><b>Inverting Amplifier with Reference</b></p>  $v_{out} = v_{in} \left( -\frac{R_f}{R_s} \right) + V_{REF} \left( \frac{R_f}{R_s} + 1 \right)$	<p><b>Noninverting Amplifier with Reference</b></p>  $v_{out} = v_{in} \left( 1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left( \frac{R_{top}}{R_{bottom}} \right)$
<p><b>Voltage Summer</b></p>  $V_{out} = V_1 \left( \frac{R_2}{R_1 + R_2} \right) + V_2 \left( \frac{R_1}{R_1 + R_2} \right)$	<p><b>Unity Gain Buffer</b></p>  $v_{out} = v_{in}$	

## 1. Voltage Summers

**Learning Goal:** This problem uses basic circuit analysis techniques to find the response of a summer circuit.

**Relevant Notes:** [Note 19](#) goes different op-amp circuit topology and corresponding derivations.

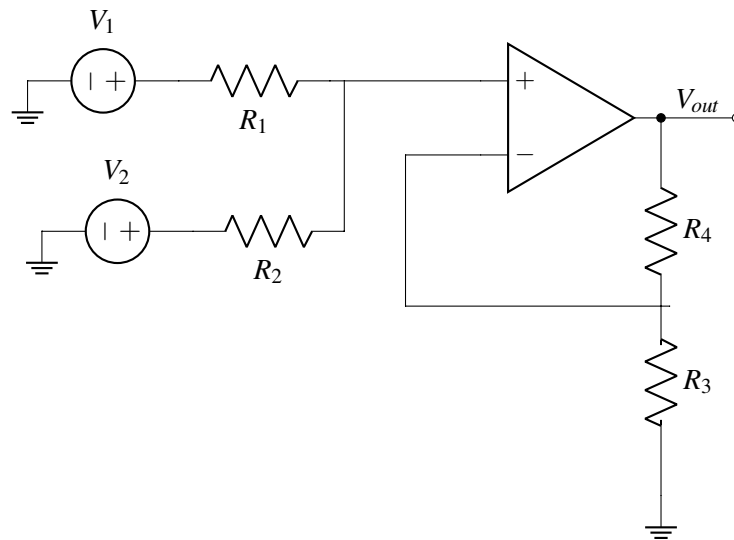- (a) Calculate  $V_{out}$  in terms of  $V_1$  and  $V_2$ . Assume that  $R_1 = R_2$ . Use superposition.



- (b) What values should we select for  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$  such that  $V_{out} = V_1 + 2V_2$ ?

## 2. Multi-stage Amplifier

**Learning Goal:** The objective of this problem is to understand how multiple stages of op-amp circuits can be used to achieve a specific circuit gain.

**Relevant Notes:** [Note 19 Section 19.5](#) goes over inverting and non-inverting amplifiers.

- (a) What is the range of values that we can scale  $V_{in}$  by when using a non-inverting op amp? (What are possible values for the gain?)

- (b) What is the range of values that we can scale  $V_{in}$  by when using an inverting op amp? (What are the possible values for the gain?)
- (c) Can you design a single inverting/ non-inverting amplifier with circuit gain  $G = 0.5$ ? If not, what range of gain values is not reachable using a single inverting op amp or a single non-inverting op amp?
- (d) How would you construct a circuit using inverting/ non-inverting amplifiers so that the overall circuit gain is  $G = 0.5$ ?


### 3. Op Amps as Buffers

**Learning Goal:** This problem helps understand the operating principle of an op-amp buffer and how it helps with loading.

**Relevant Notes:** [Note 19 Section 19.7](#) goes different op-amp circuit topology and corresponding derivations.

Now we will revisit a problem that you might have seen before, with our new knowledge of op-amps. We have access to a circuit inside a 'black box' as shown below, with two terminal coming out of it.

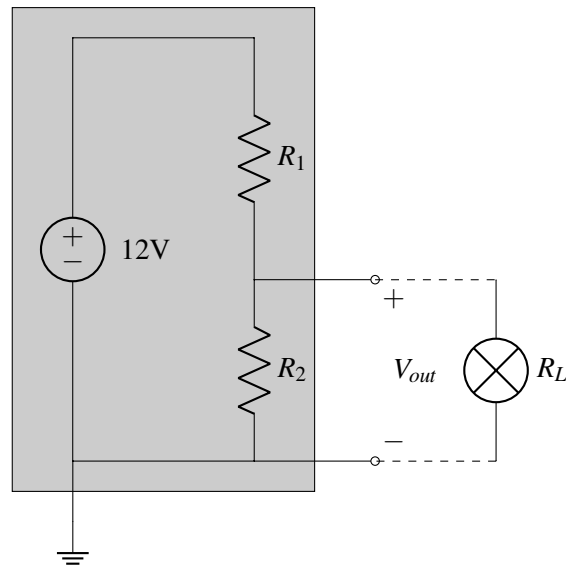- (a) We need a voltage of 6V power a light bulb with resistance  $R_L$ . Design  $R_1$  and  $R_2$  inside the black box so that the voltage across  $R_2$  is exactly equal to this required voltage **when the bulb is not connected**; i.e.  $V_{R_2} = V_{out} = 6V$ .



(b) Now let us connect the bulb  $R_L$  across  $R_2$ . What is the voltage across  $R_1$ ,  $R_2$  and  $R_L$  when the bulb is connected when  $R_L = R_2$ ? Use the values of  $R_1$  and  $R_2$  from the last part. Will the light bulb turn on? What happens if  $R_L = 2R_2$ ?

(c) Using your knowledge of op-amps, how could you resolve this issue of  $V_{out}$  changing based on the value of  $R_L$ ? Think about how you might use an op-amp buffer.