



**Sanity check question:** What challenge does the relatively small size of the audible spectrum create? Remember, the word “cutoff” in the phrase “cutoff frequency” is somewhat of a misnomer; the cutoff frequency indicates the point at which the signal power is attenuated by half, not the point at which it is fully eliminated. **Hint:** Think about separation in frequency domain.

Note: Acoustic waves are *not* electromagnetic (EM) waves: sound waves are mechanical and therefore need a medium through which to propagate. While EM waves do not need a medium<sup>1</sup>: they can propagate through the vacuum of space.

You will be targeting the bass, midrange, and treble (aka “high mids”-“high freqs”) sections depicted in Figure 2 above, which we define as follows:

Bass	0-500 Hz
Midrange	1000-5,000 Hz
Treble	6,000-20,000 Hz

Ultimately, these frequency ranges are **guidelines**: the goal of this lab is to independently light up your LEDs (with little to no overlap — two LEDs should ideally not light up at the same pure frequency, and “dead zones” where none of the LEDs light up should be minimal/imperceptible) and generate sound with the piezo speaker on TinkerCAD.

## Part 1: Piezoelectric speaker

A piezo or piezoelectric speaker is a loudspeaker that uses the piezoelectric effect for generating sound. The mechanical motion is created by applying a voltage to a piezoelectric material, and this motion is typically converted into audible sound using diaphragms and resonators.

As shown in Figure 3(a), the heart of each piezoelectric speaker is a ceramic disc that interacts when it feels a certain voltage difference. An increase of the peak-to-peak voltage  $V_{pp}$ , will result in a larger piezo deformation and larger sound output. Piezoelectric speakers have a complex electronic equivalent circuit [Figure 3(b)] but mainly they can be seen as a capacitive load with values between  $nF$  to  $\mu F$  (e.g.  $1.5\mu F$ ). For simplicity, we will treat the piezoelectric speaker as a resistor during calculation in this lab.

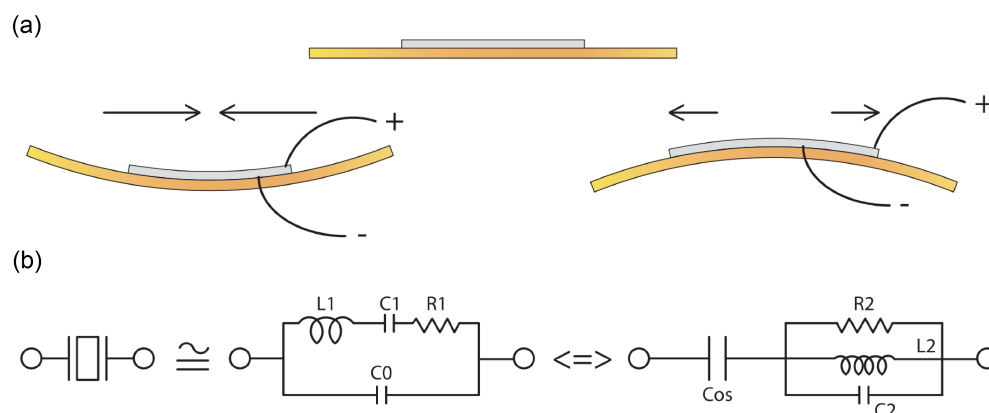


Figure 3: (a) Piezo interacting with voltage variations, (b) Equivalent circuit of Piezo.

<sup>1</sup>This bothered early scientists, so they came up with the concept of the [aether](#) (subsequently decommissioned in 1897).

## Part 2: A Bass-ic Color Organ

Now we are ready to begin building the color organ circuit! The finished product will look something like this:

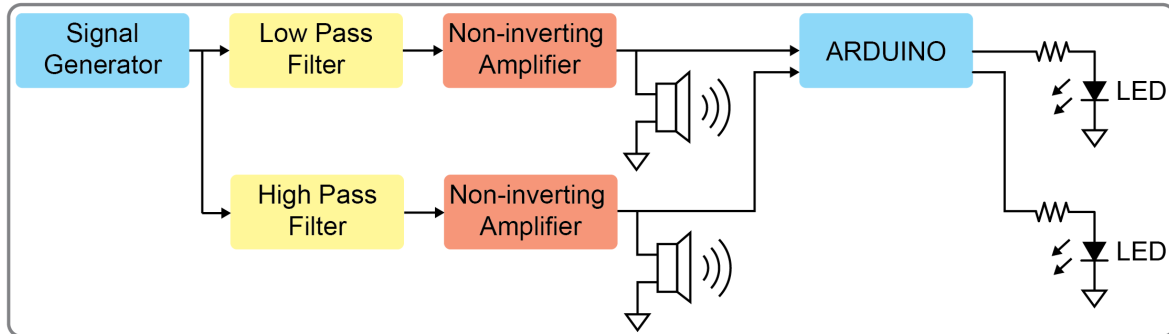


Figure 4: High-level overview of completed color organ.

This is a significantly larger circuit than the circuits you have built in previous labs, so **be sure to plan ahead when constructing your circuit, and keep your circuit clean!**

### Generalizing the first-order filter

The general first-order (or **bilinear**, since it is linear in both the numerator and denominator) transfer function is as follows (recall,  $s = j\omega$ ):

$$H(s) = \frac{a_1 s + a_0}{s + \omega_0}$$

*Think: What is the gain at  $s = \infty$ ? What about at  $s = 0$ ? The gain at  $s = 0$  is the DC gain, and the gain at  $s = \infty$  is the high frequency gain. In this case, the high-frequency gain approaches  $a_1$ , and the DC gain is  $a_0/\omega_0$ . The coefficients  $a_0$  and  $a_1$  determine what kind of filter we have. As an exercise, think of the relationships among the numerator coefficients that realize the different kinds of filters.*

The first filter you will build in this lab will be a first-order low-pass RC filter to isolate the bass frequencies, as detailed in the lab ipynb. It would be also helpful to take a look at [Part 4](#) of this note to familiarize yourself with the derivation of low-pass RC filters.

Now, you're ready to build your filter! Go to the ipython notebook and complete Part 1.

## Part 3: A Treble-some Color Organ

Next, we will build a first-order high-pass RC filter to isolate the treble frequencies. The derivation of high-pass RC filters can also be found in [Part 4](#).

**Sanity check question:** Does placing the filters in parallel affect their respective cutoff frequencies? Think: is the signal you're trying to process a current signal or a voltage signal?

Go to the ipython notebook and complete Part 2.


**Sanity check question:** Why do we use sinusoid waveform with 0V DC offset? Hint: The input to our filters, which is generated by the signal generator, has both a sinusoidal/fluctuating component with a frequency and a DC offset component. What does a low-pass filter do to each component? What about a high-pass filter?

## Part 4: Derivation of first-order RC filters

### Building Filters


#### Lowpass Filter

##### Circuit Schematic

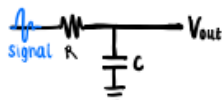

Think: the "gate" C is lower.

##### Low Pass Frequency Response

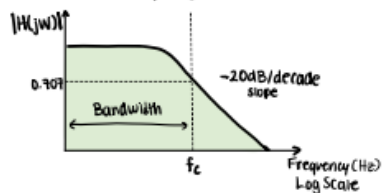

$$\hat{V}_{out} = \hat{V}_{in} \cdot \frac{Z_C}{Z_R + Z_C} = \hat{V}_{in} \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \hat{V}_{in} \frac{1}{j\omega RC + 1}$$

$$\frac{V_{out}}{V_{in}} = H(j\omega) \text{ and cutoff frequency is at half power, where } \frac{|\hat{V}_{out}|}{|\hat{V}_{in}|} = \frac{1}{\sqrt{2}} = 0.707.$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(j\omega RC)^2 + 1}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$2 = 1 + (\omega RC)^2$$

$$1 = \omega RC$$

$$\omega = \frac{1}{RC} \quad \text{angular cutoff frequency}$$


$$f_c = \frac{1}{2\pi RC} \quad \text{cutoff frequency}$$

Conceptually: as  $\omega \rightarrow \infty$ ,  $|H(j\omega)| \rightarrow 0$   
 as  $\omega \rightarrow 0$ ,  $|H(j\omega)| \rightarrow 1$

Everything that is less than  $f_c$  gets through. Note that out cutoff isn't clean & perfect because the attenuation is gradual.


#### High Pass Filter

##### Circuit Schematic

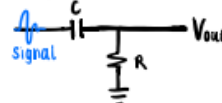

Think: the "gate" C is higher.

##### High Pass Frequency Response

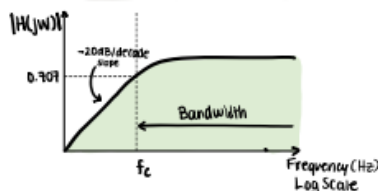

$$\hat{V}_{out} = \hat{V}_{in} \cdot \frac{Z_R}{Z_R + Z_C} = \hat{V}_{in} \frac{R}{\frac{1}{j\omega C} + R}$$

$$|H(j\omega)| = \frac{|\hat{V}_{out}|}{|\hat{V}_{in}|} = \frac{1}{\sqrt{2}} = \frac{\sqrt{R^2}}{\sqrt{(\frac{1}{\omega C})^2 + R^2}}$$

$$\frac{1}{2} = \frac{R^2}{(\frac{1}{\omega C})^2 + R^2}$$

$$(\frac{1}{\omega C})^2 + R^2 = 2R^2$$

$$(\frac{1}{\omega C})^2 = R^2$$

$$\omega = \frac{1}{RC} \quad \text{angular cutoff frequency}$$

$$f_c = \frac{1}{2\pi RC} \quad \text{cutoff frequency}$$

Conceptually: as  $\omega \rightarrow \infty$ ,  $|H(j\omega)| \rightarrow 1$   
 as  $\omega \rightarrow 0$ ,  $|H(j\omega)| \rightarrow 0$

Everything higher than  $f_c$  gets through.


**Thought:** What happens to DC Voltage in a high pass filter?

↳ It gets destroyed,  $\omega = 0$ !

**Thought:** How can we make attenuation faster?

↳ Multiple filters cascaded. Our transfer functions multiply, making the drop-off faster.

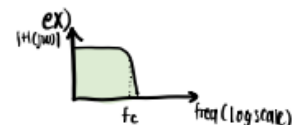↳ make sure to place a unity gain buffer in between to prevent loading



## References

Horowitz, P. and Hill, W. (2015). *The Art of Electronics*. 3rd ed. Cambridge: Cambridge University Press, ch 1.  
Sedra, A. and Smith, K. (2015). *Microelectronic Circuits*. 7th ed. New York: Oxford University Press, ch 17.

*Written by Mia Mirkovic (2019).*

*Edited by Kourosh Hakhamaneshi (2020). Version 2.0, 2020.*

*Edited by Steven Lu, Bozhi Yin (2021). Version 3.0, 2021.*

*Edited by Bozhi Yin (2022). Version 4.0, 2021.*