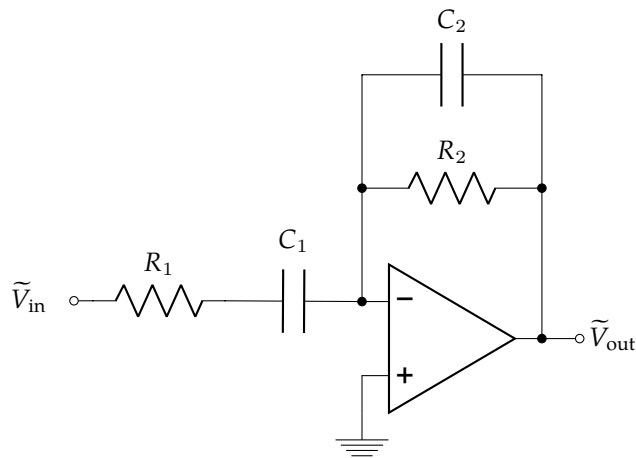


## 1 Differentiator Circuit


Consider the following circuit



1. What is the transfer function  $H(j\omega)$ ?
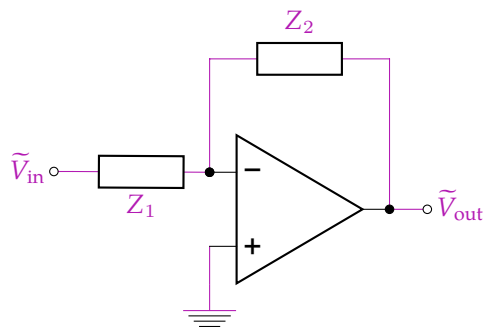
### Answer

This is a non-inverting amplifier with impedances  $Z_1 = R_1 + \frac{1}{j\omega C_1}$  and  $Z_2 = R_2 \parallel \frac{1}{j\omega C_2}$



Therefore, the transfer function will be  $H(j\omega) = -\frac{z_2}{z_1}$ .

$$H(j\omega) = -\frac{Z_2}{Z_1} = -\frac{j\omega R_2 C_1}{(1 + j\omega R_2 C_2)(1 + j\omega R_1 C_1)}$$

## 2 Parallel RLC


Consider the circuit shown below.

1. Right after the switches change state (i.e., at  $t = 0$ ), what is the value of  $i_L$ ?


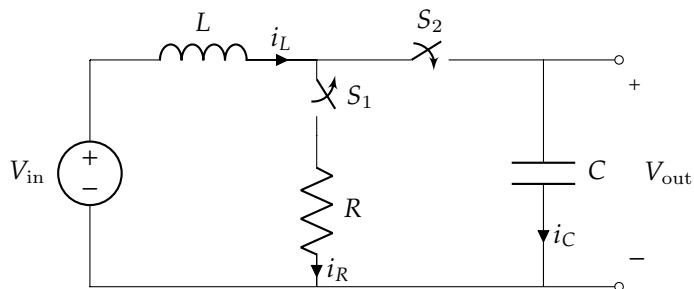
### Answer

$$V_L = L \frac{di_L}{dt} = 0, i_c = C \frac{dV_{out}}{dt} = 0 \implies V_{out} = V_{in}, i_L = i_R, \text{ so } i_L(0^-) = \frac{V_{in}}{R}.$$

Right after switches change state, the inductor current cannot change instantaneously (since this could require infinite voltage across it), so  $i_L(0^+) = \frac{V_{in}}{R}$ .



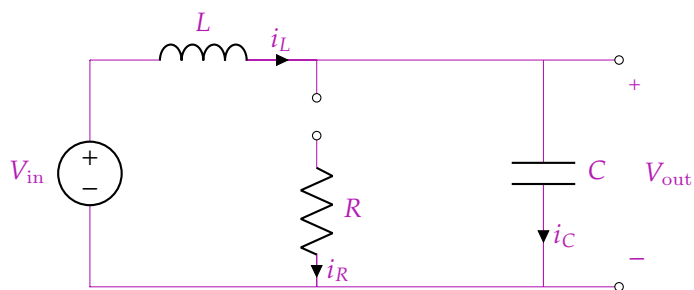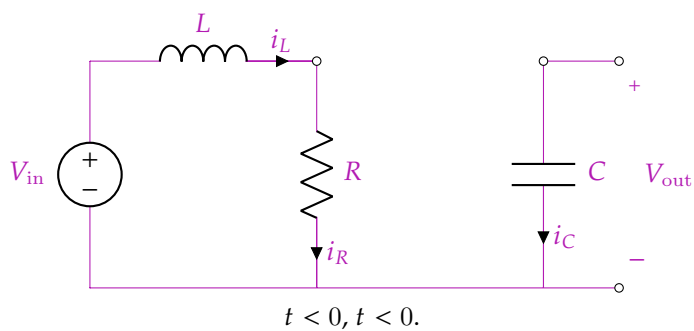At  $t < 0$ ,  $S_1$  is on (short-circuited), and  $S_2$  is off (open-circuited).  
 At  $t \geq 0$ ,  $S_1$  is off (open-circuited), and  $S_2$  is on (short-circuited).



At  $t < 0$ ,  $S_1$  is on (short-circuited), and  $S_2$  is off (open-circuited).  
 At  $t \geq 0$ ,  $S_1$  is off (open-circuited), and  $S_2$  is on (short-circuited).

2. Choosing the state variables as  $\vec{x}(t) = \begin{bmatrix} V_{\text{out}}(t) \\ i_L(t) \end{bmatrix}$ , derive the  $\mathbf{A}$  matrix that captures the behavior of this circuit for  $t \geq 0$  with the matrix differential equation  $\frac{d\vec{x}(t)}{dt} = \mathbf{A}\vec{x}(t) + \vec{b}$ , where  $\vec{b}$  is a vector of constants.

**Answer**

$$\begin{aligned}
V &= L \frac{di_L}{dt} \\
V_{\text{in}} - V_{\text{out}} &= L \frac{di_L}{dt} \\
\frac{di_L}{dt} &= -\frac{V_{\text{out}}}{L} + \frac{V_{\text{in}}}{L} \\
i_C &= i_L = C \frac{dV_{\text{out}}}{dt} \\
\frac{dV_{\text{out}}}{dt} &= \frac{1}{C} i_L \\
\frac{d}{dt} \begin{bmatrix} V_{\text{out}} \\ i_L \end{bmatrix} &= \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} V_{\text{out}} \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{V_{\text{in}}}{L} \end{bmatrix} \\
\mathbf{A} &= \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & 0 \end{bmatrix}, \quad \mathbf{b} = \begin{bmatrix} 0 \\ \frac{V_{\text{in}}}{L} \end{bmatrix}
\end{aligned}$$

3. Assuming that  $V_{\text{out}}(0) = 0$  V, derive an expression for  $V_{\text{out}}(t)$  for  $t \geq 0$ .

**Answer**

We perform a change of variables, so that  $\hat{V}_{\text{out}}(t) = V_{\text{out}} - V_{\text{in}}$ . The  $\mathbf{A}$  matrix will not change, but the  $\vec{b}$  vector goes to zero.

$$\begin{aligned}
\det(\mathbf{A} - \lambda \mathbf{I}) &= 0 \\
\lambda^2 + \frac{1}{LC} &= 0 \\
\lambda &= \pm j \frac{1}{\sqrt{LC}}
\end{aligned}$$

At this point, there are two possible solutions.

**Method 1:**

$$\begin{aligned}
\hat{V}_{\text{out}}(t) &= k_1 \cos\left(\frac{t}{\sqrt{LC}}\right) + k_2 \sin\left(\frac{t}{\sqrt{LC}}\right) \\
V_{\text{out}}(t) &= k_1 \cos\left(\frac{t}{\sqrt{LC}}\right) + k_2 \sin\left(\frac{t}{\sqrt{LC}}\right) + V_{\text{in}} \\
V_{\text{out}}(0) = 0 &= k_1 \cos(0) + k_2 \sin(0) + V_{\text{in}} \\
k_1 &= -V_{\text{in}} \\
i_L(0) = \frac{V_{\text{in}}}{R} &= C \frac{dV_{\text{out}}}{dt}(0) \\
\frac{V_{\text{in}}}{RC} &= -\frac{k_1}{\sqrt{LC}} \sin(0) + \frac{k_2}{\sqrt{LC}} \cos(0) \\
k_2 &= \frac{\sqrt{L/C}}{R} V_{\text{in}} \\
V_{\text{out}} &= V_{\text{in}} \left( 1 - \cos\left(\frac{t}{\sqrt{LC}}\right) + \frac{\sqrt{L/C}}{R} \sin\left(\frac{t}{\sqrt{LC}}\right) \right)
\end{aligned}$$

**Method 2:**

$$\begin{aligned}
\hat{V}_{\text{out}}(t) &= k_1 e^{j\frac{1}{\sqrt{LC}}t} + k_2 e^{-j\frac{1}{\sqrt{LC}}t} \\
V_{\text{out}}(t) &= k_1 e^{j\frac{1}{\sqrt{LC}}t} + k_2 e^{-j\frac{1}{\sqrt{LC}}t} + V_{\text{in}} \\
V_{\text{out}}(0) = 0 &= k_1 e^0 + k_2 e^0 + V_{\text{in}} \\
k_1 + k_2 &= -V_{\text{in}} \\
i_L(0) = \frac{V_{\text{in}}}{R} &= C \frac{dV_{\text{out}}}{dt}(0) \\
\frac{V_{\text{in}}}{RC} &= j \frac{k_1}{\sqrt{LC}} - j \frac{k_2}{\sqrt{LC}} \\
k_1 - k_2 &= -j \frac{\sqrt{L/C}}{R} V_{\text{in}} \\
k_1 = -V_{\text{in}} \left( \frac{1}{2} + j \frac{\sqrt{L/C}}{2R} \right), k_2 &= -V_{\text{in}} \left( \frac{1}{2} - j \frac{\sqrt{L/C}}{2R} \right) \\
V_{\text{out}}(t) &= V_{\text{in}} \left( -\left( \frac{1}{2} + j \frac{\sqrt{L/C}}{2R} \right) e^{j\frac{1}{\sqrt{LC}}t} - \left( \frac{1}{2} - j \frac{\sqrt{L/C}}{2R} \right) e^{-j\frac{1}{\sqrt{LC}}t} + 1 \right)
\end{aligned}$$

At this point, let  $\frac{1}{2} + j \frac{\sqrt{L/C}}{2R} = a + bj$ ,  $e^{j\frac{1}{\sqrt{LC}}t} = \cos\left(\frac{1}{\sqrt{LC}}t\right) + j \sin\left(\frac{1}{\sqrt{LC}}t\right) = c + dj \implies$   
 $e^{-j\frac{1}{\sqrt{LC}}t} = \cos\left(-\frac{1}{\sqrt{LC}}t\right) + j \sin\left(-\frac{1}{\sqrt{LC}}t\right) = \cos\left(\frac{1}{\sqrt{LC}}t\right) - j \sin\left(\frac{1}{\sqrt{LC}}t\right) = c - dj$

$$\begin{aligned}
V_{\text{out}}(t) &= V_{\text{in}} \left( -\left( \frac{1}{2} + j \frac{\sqrt{L/C}}{2R} \right) e^{j\frac{1}{\sqrt{LC}}t} - \left( \frac{1}{2} - j \frac{\sqrt{L/C}}{2R} \right) e^{-j\frac{1}{\sqrt{LC}}t} + 1 \right) \\
&= V_{\text{in}}(1 - (a + bj)(c + dj) - (a - bj)(c - dj)) \\
&= V_{\text{in}}(1 - ac + bd - (ad + bc)j - ac + bd + (ad + bc)j) \\
&= V_{\text{in}}(1 - 2ac + 2bd) \\
&= V_{\text{in}}\left(1 - 2\frac{1}{2}\cos\left(\frac{1}{\sqrt{LC}}t\right) + 2\frac{\sqrt{L/C}}{2R}\sin\left(\frac{1}{\sqrt{LC}}t\right)\right) \\
&= V_{\text{in}}\left(1 - \cos\left(\frac{1}{\sqrt{LC}}t\right) + \frac{\sqrt{L/C}}{R}\sin\left(\frac{1}{\sqrt{LC}}t\right)\right)
\end{aligned}$$

### 3 Diagonalizability and Invertibility

- Given an example of a matrix  $A$ , or prove that no such example can exist.
  - Can be diagonalized and is invertible.
  - Cannot be diagonalized but is invertible.
  - Can be diagonalized but is non-invertible.
  - Cannot be diagonalized and is non-invertible.

#### Answer

•

$$A = \begin{bmatrix} 2 & 0 \\ 0 & -3 \end{bmatrix}$$

•

$$A = \begin{bmatrix} 2 & 1 \\ 0 & 2 \end{bmatrix}$$

•

$$A = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

•

$$A = \begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix}$$

### 4 Eigenvalue Decomposition and Singular Value Decomposition

We define Eigenvalue Decomposition as follows:

If a matrix  $A \in \mathbb{R}^{n \times n}$  has  $n$  linearly independent eigenvectors  $\vec{p}_1, \dots, \vec{p}_n$  with eigenvalues  $\lambda_1, \dots, \lambda_n$ , then we can write:

$$A = P\Lambda P^{-1}$$

Where columns of  $P$  consist of  $\vec{p}_1, \dots, \vec{p}_n$ , and  $\Lambda$  is a diagonal matrix with diagonal entries  $\lambda_1, \dots, \lambda_n$ .

Consider a matrix  $A \in \mathbb{S}^n$ , that is,  $A = A^T \in \mathbb{R}^{n \times n}$ . This is a symmetric matrix and has orthogonal eigenvectors. Therefore its eigenvalue decomposition can be written as,

$$A = P\Lambda P^T$$

- First, assume  $\lambda_i \geq 0, \forall i$ . Find the SVD of  $A$ .

#### Answer

Observe that,

$$A^T A = P\Lambda^2 P^T$$

This means that,

$$\sigma_i = \lambda_i \text{ and } V = P$$

We have,

$$Av_i = \lambda_i v_i = \sigma_i v_i$$

Plugging into our SVD condition  $Av_i = \sigma_i u_i$ :

$$\sigma_i v_i = \sigma_i u_i$$

This means that,

$$U = V = P$$

Therefore, in this case, the eigenvalue decomposition is the same as the singular value decompositions.

2. Let one particular eigenvalue  $\lambda_j$  be negative, with the associated eigenvector being  $p_j$ . Succinctly,

$$Ap_j = \lambda_j p_j \text{ with } \lambda_j < 0$$

We are still assuming that,

$$A = P\Lambda P^T$$

- a) What is the singular value  $\sigma_j$  associated to  $\lambda_j$ ?
- b) What is the relationship between the left singular vector  $u_j$ , the right singular vector  $v_j$  and the eigenvector  $p_j$ ?

### Answer

a)

$$\sigma_j = |\lambda_j|$$

b) Either,

$$u_j = p_j \text{ and } v_j = -p_j$$

or,

$$u_j = -p_j \text{ and } v_j = p_j$$

This is because the diagonal entries of  $\Sigma$  MUST be non-negative.